



Chapter 4

Fundamentals of Logic

4.1



The Binary Concept

Binary refers to the idea that many things can be thought of as existing in only one of two states.



The binary states
are **1** and **0**



The 1 and 0 can represent:

ON or OFF


Open or Closed

True or False

High or Low


A logic gate is a circuit with several inputs but only one output that is activated by particular combinations of input conditions.

Logical AND

 

The **high beam light** can be turned on only when the light switch **AND** the high beam switch are closed.

Logical OR

 

The **dome light** will be turned on whenever the passenger door switch **OR** the driver door switch is activated.


4.2



AND, OR, and NOT Functions

The *AND* Function

 An **AND gate** is a device with two or more inputs and one output.







AND truth table

Inputs		Output
<i>A</i>	<i>B</i>	<i>Y</i>
0	0	0
0	1	0
1	0	0
1	1	1

The AND gate output is **1** only if all inputs are **1**.

The AND Function

  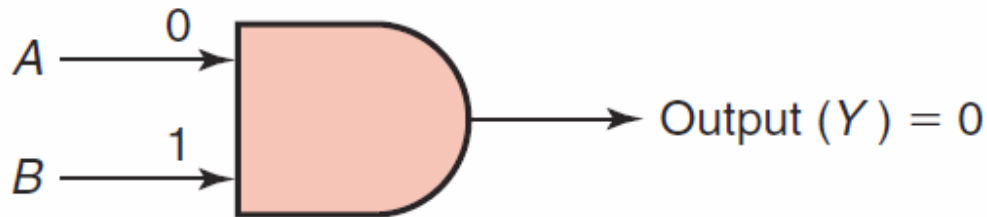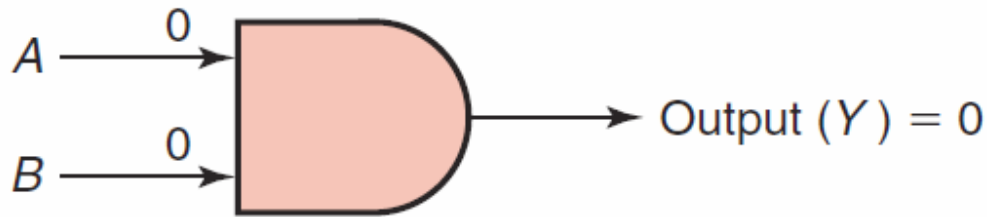


Truth table

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

- If **all** inputs are **1**, the output will be **1**.
- If **any** input is **0**, the output will be **0**.

The AND Function

 The AND logic gate operates similarly to control devices connected in **series** — — — — —




The light will be **on** only when both switch A **and** switch B are **closed**.

Truth table


SW-A		SW-B		Light	
Open	(0)	Open	(0)	Off	(0)
Open	(0)	Closed	(1)	Off	(0)
Closed	(1)	Open	(0)	Off	(0)
Closed	(1)	Closed	(1)	On	(1)

Logic representation

 

The OR Function

 An **OR gate** can have any number of inputs but only one output.







OR truth table

Inputs		Output
<i>A</i>	<i>B</i>	<i>Y</i>
0	0	0
0	1	1
1	0	1
1	1	1

The OR gate output is **1** if **one or** more inputs are **1**.


The OR Function

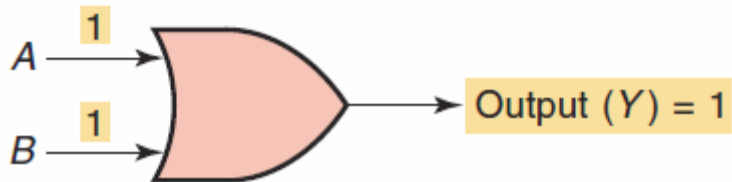   

Truth table		
Inputs		Output
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

- If **one or more** inputs are **1**, the output is **1**.
- If **all** inputs are **0**, the output will be **0**.

The OR Function

 


The OR logic gate operates similarly to control devices connected in **parallel**.

The light will be **on** if switch A **or** switch B or both are **closed**.

Truth table


SW-A		SW-B		Light	
Open	(0)	Open	(0)	Off	(0)
Open	(0)	Closed	(1)	On	(1)
Closed	(1)	Open	(0)	On	(1)
Closed	(1)	Closed	(1)	On	(1)

Logic representation

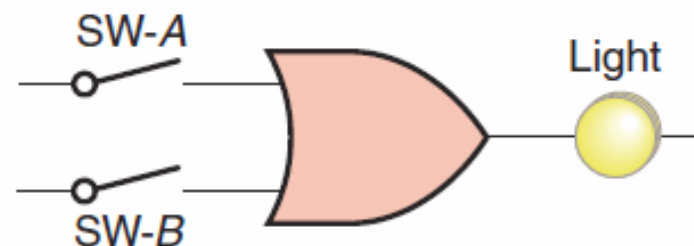

The *NOT* Function

 The **NOT** function can have **only one** input.



NOT truth table

A	NOT A
0	1
1	0


The NOT **output** is **1** if the **input** is **0**.

The **output** is **0** if the input is **1**.

The *NOT* Function


The **circle** indicates that an **inversion** of the logical function has taken place.

 The **bar** across the top of the letter, indicates an **inverted** output.



The result of the NOT operation is always the **inverse** of the input, and the NOT function is, therefore, called an **inverter**.

The *NOT* Function

 


The NOT function can be performed on a contact input simply by using a **normally closed** instead of a normally open contact.

Truth table


Pushbutton		Light	
Not pressed	(0)	On	(1)
Pressed	(1)	Off	(0)

Logic representation

 


The *NOT* Function

 NOT function used in **conjunction** with an AND gate on a low pressure indicator circuit.




Truth table		
Pressure switch	Power	Pressure indicator
0	1	1
1	1	0

 


The *NAND* Function

 An AND gate with an inverted output is called a **NAND** gate.




NAND truth table		
Inputs		Output
A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

 — The NAND gate has the **opposite** outputs to the AND gate.





The *NOR* Function

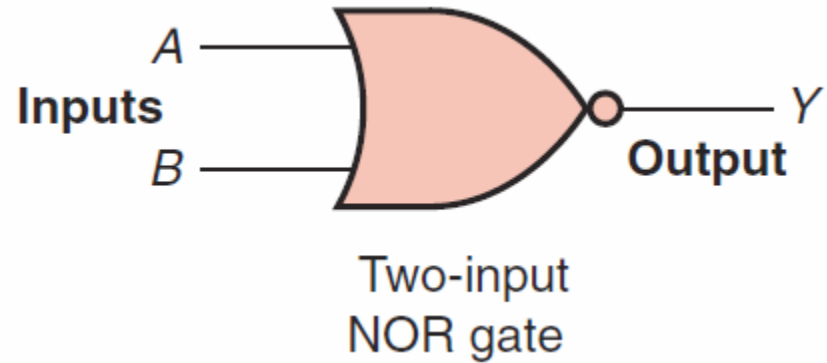A OR gate with an inverted output is called a **NOR** gate.



NOR truth table		
Inputs		Output
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

 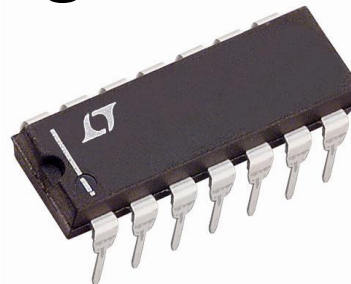← — The NOR gate has the **opposite** outputs to the OR gate.




The Exclusive-OR (XOR) Function

Truth table

Inputs		Output
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

The output of the **XOR** gate is **HIGH (1)** only when **one input or the other** is HIGH, but **not both**.

 The exclusive-OR gate is commonly used for the **comparison** of two binary numbers.




 4.3



Boolean Algebra



The mathematical study of the binary number system and logic is called *Boolean algebra*.



Boolean algebra is used to write combinations of logic statements that are used to solve PLC programming problems.




Typical Boolean Instructions or Statements

Instructions are based on the basic Boolean operators of **AND**, **OR**, and **NOT**



 
 
Boolean Instruction and Function	Graphic Symbol
Or (OR) Logically ORs a normally open contact in parallel with another contact in a rung.	
Or Not (OR NOT) Logically ORs a normally closed contact in parallel with another contact in a rung.	
And (AND) Logically ANDs a normally open contact in series with another contact in a rung.	
And Not (AND NOT) Logically ANDs a normally closed contact in series with another contact in a rung.	

Even though these instructions are programmed in a list format they **implement** the same logic as **relay ladder logic**.





Boolean algebra as related to AND, OR, and NOT functions.

   Logic symbol	Logic statement	Boolean equation	Boolean notations
	Y is 1 if A and B are 1	$Y = A \cdot B$ or $Y = AB$	Symbol Meaning • and + or - not ◦ invert = result in
	Y is 1 if A or B is 1	$Y = A + B$	
	Y is 1 if A is 0 Y is 0 if A is 1	$Y = \overline{A}$	

    Logic operators used form *logical statements*.



 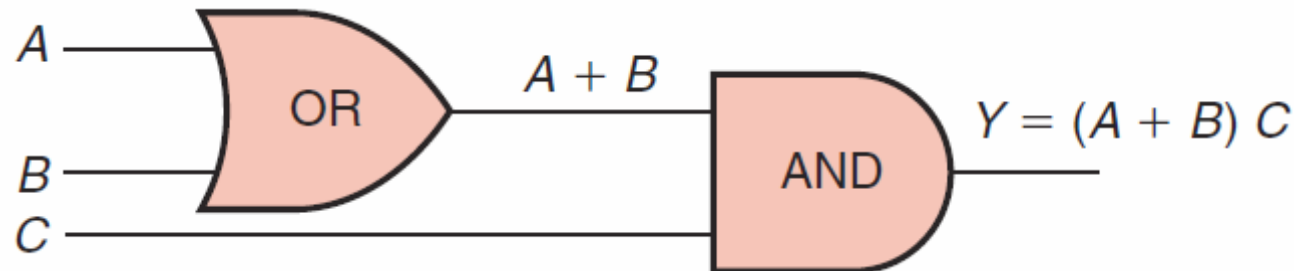  **Logic
operators
used to
form
Boolean
equations.**



Some laws of Boolean algebra are similar to those of ordinary algebra.

COMMUTATIVE LAW

$$A + B = B + A$$

$$A \cdot B = B \cdot A$$

ASSOCIATIVE LAW

$$(A + B) + C = A + (B + C)$$

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

**This law holds true only
in Boolean algebra**



DISTRIBUTIVE LAW

$$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$$

$$A + (B \cdot C) = (A + B) \cdot (A + C)$$

4.4




Developing Logic Gate Circuits from Boolean Expressions

Logic gate circuit developed from the Boolean expression $Y = AB + C$.

Gates required:

1 - **AND** gate with input A and B

 1 - **OR** gate with input C and output from previous **AND** gate




Logic gate circuit developed from the Boolean expression $Y = A (BC + D)$.

Gates required:

1 - **AND** gate with input B and C

1 - **OR** gate with inputs BC and D

 1 - **AND** gate with inputs A and the output from the OR gate




 4.5




Producing the Boolean Equation for a Given Logic Gate Circuit

Determining the logic circuit Boolean equation



- The output of the OR gate is $A + B$
- The output of the inverter is $\overline{D}$
- Based on the input combination applied to the AND gate the Boolean equation for the circuit is $Y = C \overline{D} (A + B)$

 Determining the logic circuit Boolean equation



- The output of AND gate 1 is $\bar{A}B$
- The output of AND gate 2 is $A\bar{B}$
- Based on the combination of inputs applied to the OR gate the Boolean equation for the circuit is

$$Y = \bar{A}B + A\bar{B}$$

4.6




Hardwired Logic versus Programmed Logic

The term *hardwired logic* refers to logic control functions that are determined by the way devices are electrically interconnected.


Hardwired logic is **fixed** and changeable only by altering the way devices are electrically interconnected.

Hardwired motor control program.

 


Programmable control is based on the basic logic functions, which are programmable and easily changed.

 PLC **programmed** motor control program.




Simulated PLC motor control program.

Ladder Logic Program

 

I/O

 The most common PLC programming language is *ladder logic* .




A ladder logic program consists of several **rungs**, each of which controls an output.


Each rung is a combination of **input** conditions (symbols) connected from left to right, with the symbol that represents the **output** at the far right.

Relationship between the relay ladder *schematic*, the ladder logic *program*, and the equivalent logic *gate circuit*.


Relay schematic

 

Ladder logic program

 



Gate logic

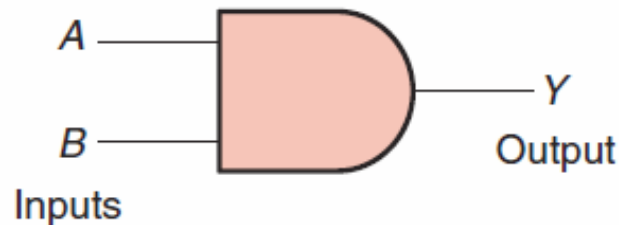

Boolean equation: $AB = Y$


Two limit switches connected in **series** and used to control a solenoid valve.

  Program simulation of two switches in series used to control an output.



Boolean equation: $AB = Y$


Program

 


I/O

Two limit switches connected in *parallel* and used to control a solenoid valve.


Relay schematic

 

Ladder logic program

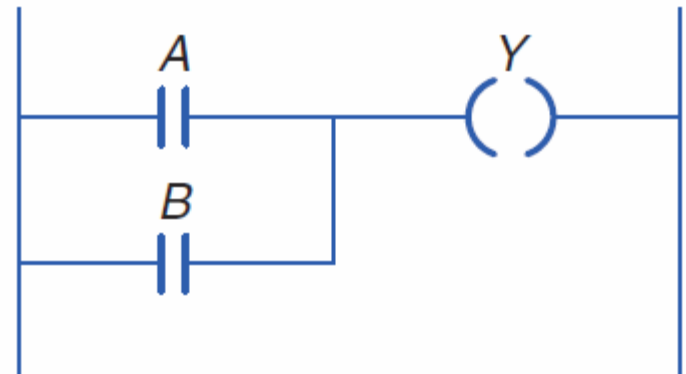


Gate logic

 


$$\text{Boolean equation: } A + B = Y$$

Program simulation of two switches in parallel used to control an output.

Relay schematic

 


Gate logic

 

$$\text{Boolean equation: } A + B = Y$$


Program

 


I/O

Two limit switches connected in *parallel* with each other and in *series* with a pressure switch to control a pilot light.


Relay schematic

 

Ladder logic program

 


Gate logic

 


$$\text{Boolean equation: } (A + B)C = Y$$

Program simulation of two switches in parallel and this pair in series with a switch used to an output.

Relay schematic

 


Gate logic

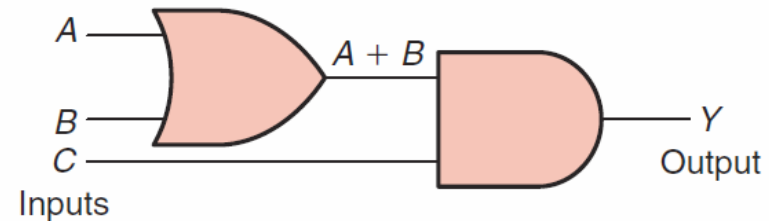

$$\text{Boolean equation: } (A + B)C = Y$$


Program

 


I/O

Two limit switches connected in *parallel* with each other and in *series* with two sets of flow switches (in *parallel*), and used to control a pilot light.


Relay schematic

 



Ladder logic program

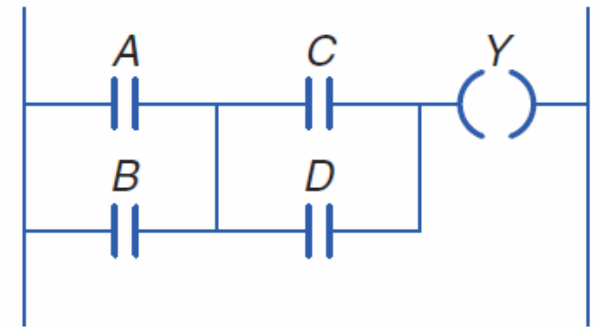

Gate logic

 


  Program simulation of two switches in parallel and in series with a second pair of switches in parallel.



Boolean equation: $(A + B) (C + D) = Y$


Program

 


I/O

Two limit switches connected in *series* with each other and in *parallel* with a third limit switch, and used to control a warning horn.


Relay schematic

 

Ladder logic program

 


Gate logic

 


$$\text{Boolean equation: } (AB) + C = Y$$

Program simulation of two switches in series and in parallel with a third switch.

Relay schematic

 


Gate logic

 

$$\text{Boolean equation: } (AB) + C = Y$$


Program

 


I/O

Two limit switches connected in *series* with each other and in *parallel* with two other limit switches (in *series*), and used to control a pilot light.


Relay schematic

 

Ladder logic program

 


Gate logic

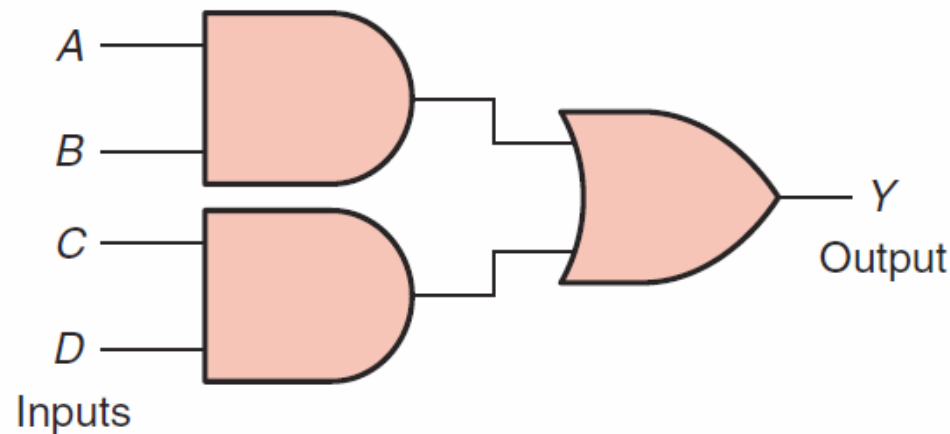


$$\text{Boolean equation: } (AB) + (CD) = Y$$

Program simulation of two switches in series and in parallel with a second pair in series.

Relay schematic

 


Gate logic

 

$$\text{Boolean equation: } (AB) + (CD) = Y$$


Program

 


I/O

One limit switch connected in series with a *normally closed pushbutton* and used to control a solenoid valve.


Relay schematic

 

Ladder logic program

 


Gate logic

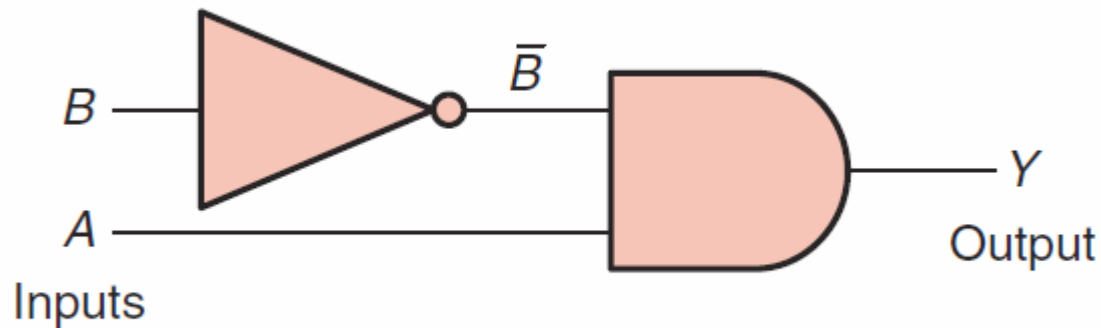


Boolean equation: $A\bar{B} = Y$

Program simulation of one switch connected in series with a normally closed pushbutton.

Relay schematic

 


Gate logic

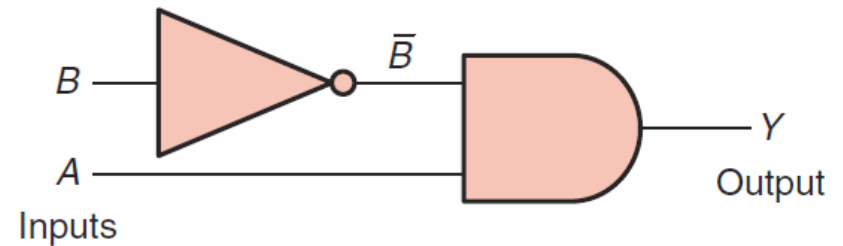

$$\text{Boolean equation: } A\bar{B} = Y$$


Program

 


I/O

The output lamp of this circuit is ON only when pushbutton A or B is pressed, *but not both*.


Relay schematic

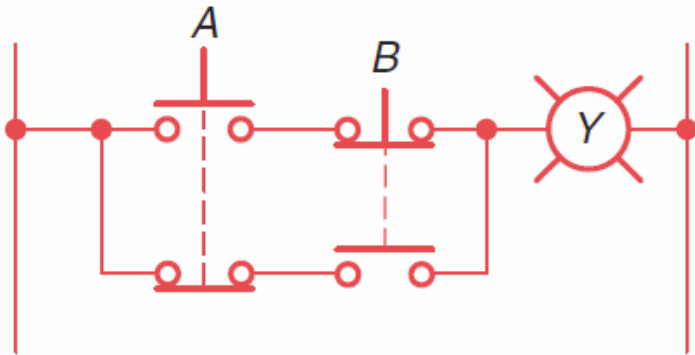

Ladder logic program


 


Gate logic

 


Boolean equation: $\bar{A}B + A\bar{B} = Y$
 $A \oplus B = Y$

  Program simulation of an exclusive OR circuit.



$$\begin{aligned}\text{Boolean equation: } \bar{A}B + A\bar{B} &= Y \\ A \oplus B &= Y\end{aligned}$$


Program

 


I/O

When either start button is depressed, the motor runs. Either stop button stops the motor when it is depressed.


Relay schematic

 

Ladder logic program

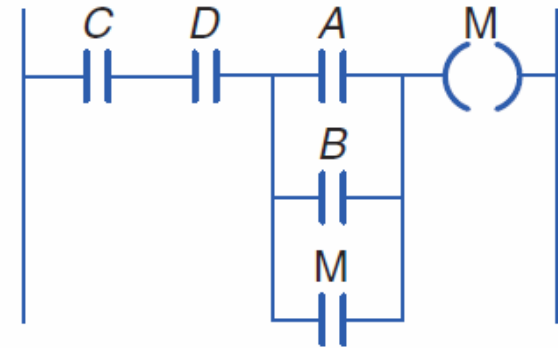


Gate logic

 


Program simulation of a motor starter circuit.


Relay schematic

 

Gate logic

 

Program

 

I/O

4.7




Programming Word Level Logic Instructions

Selecting Word Logic Instructions

If you want to . . .	. . . use this instruction.
Know when matching bits in two different words are both ON	AND
Know when one or both matching bits in two different words are ON	OR
Know when one or the other bit of matching bits in two different words is ON	XOR
Reverse the state of bits in a word	NOT


Word-level *AND* instruction.

 

This instruction tells the processor to perform an **AND** operation on **B3:5** and **B3:7** and to store the result in destination **B3:10** when input device A is true.

Program simulation of the word level AND instruction.


Program

 

I/O

B3 Data Table

Word-level *OR* instruction.

 

This instruction **ORs** the data in Source **A**, bit by bit, with the data in Source **B** and stores the result at the **destination** address.

Program simulation of the word level OR instruction.

Program

LAD 2:

000

I:1/0

A

001

I/O Simulation

I:1

00

01

02

03

04

05

06

07

08

O:2

00

01

02

03

04

05

06

07

08

OR

Bitwise Inclusive OR

SourceB3:152428

Source BB3:265280

DestB3:30

Binary Table

	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
B3:0/	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
B3:1/	1	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0
B3:2/	1	1	1	1	1	1	1	1	0	0	0	0	0	0	0	0
B3:3/	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
B3:4/	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
B3:5/	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0


Radix: BinaryTable: B3: BinaryForces

AddressB3:3Symbol

I/O

B3 Data Table

Word-level XOR instruction.

 

Data from input **I:1.0** are **compared**, bit by bit, with data from input **I:3.0**. Any **mismatches** energize the **corresponding** bit in word **O:4.0**.

Program simulation of the word level XOR instruction

The screenshot displays a PLC simulation environment. On the left, the 'I/O Simulator II' window shows four columns of digital inputs and outputs, labeled I:1, I:2, I:3, and O:4. Each column contains 16 bits, numbered 00 to 15. The I:1 and I:3 columns have toggle switches, while I:2 and O:4 have indicator lights. The main window shows the Ladder Logic (LAD) editor for 'LAD 2'. It features a network table with two rows: '000' and '001'. The '001' row contains an XOR instruction. A pop-up window titled 'XOR' provides details for this instruction: 'Bitwise Exclusive OR', 'Source I:1', 'Source B I:3', and 'Dest O:4'. Below the network table, an 'Input Table' window is open, showing a 16-bit binary input table for I:0 through I:5. The table has columns for bits 15 down to 0. The 'Radix' is set to 'Binary' and the 'Table' is 'I1: Input'. The 'Address' and 'Symbol' fields are empty.

I/O Simulator II

I:1	I:2	I:3	O:4
00	00	00	00
01	01	01	01
02	02	02	02
03	03	03	03
04	04	04	04
05	05	05	05
06	06	06	06
07	07	07	07
08	08	08	08
09	09	09	09
10	10	10	10
11	11	11	11
12	12	12	12
13	13	13	13
14	14	14	14
15	15	15	15

LAD 2

Network	Instruction
000	
001	XOR

XOR

- Bitwise Exclusive OR
- Source I:1
- Source B I:3
- Dest O:4

Input Table

	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
I:0/																
I:1/	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
I:2/																
I:3/	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
I:4/																
I:5/	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0


Radix: Binary Table: I1: Input Forces

Address Symbol

I:1 I:3 O:4

Input Table

Word-level NOT operation.

 

The bit pattern in **B3:10** is the result of the instruction being **true** and is the **inverse** of the bit pattern in **B3:9**.

Program simulation of the word level NOT instruction

The screenshot displays a PLC programming interface with a ladder logic diagram and a 'Binary Table' window.

Ladder Logic:

- Address 000: A normally open contact labeled 'A' is connected to a coil labeled 'NOT'.
- Address 001: The output of the 'NOT' instruction is connected to a coil labeled '<END>'.

NOT Instruction Details:

- Source: B3:9 (170)
- Dest: B3:10 (-65536)

Binary Table:

	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
B3:9/	0	0	0	0	0	0	0	0	1	0	1	0	1	0	1	0
B3:10/	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
B3:11/	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
B3:12/	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
B3:13/	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
B3:14/	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

Radix: Binary Table: B3: Binary Forces

Address: Symbol: