

Electrical Basics **&** **Classic Control**

COURSE CONTENTS

Part One **Electrical Basics & Control Circuits**


- Chapter 1*** Electrical Basics
- Chapter 2*** Types of Control System
- Chapter 3*** Classic control components
- Chapter 4*** Motor Name Plate
- Chapter 5*** Types of AC Motors
- Chapter 6*** Different types of Control Circuits
- Chapter 7*** Types of Starter for Induction motors
- Chapter 8*** Testing of Induction Motor
- Chapter 9*** Typical Motor Failure & Protection

CHAPTER 1

Electrical Basics

Electric Circuit

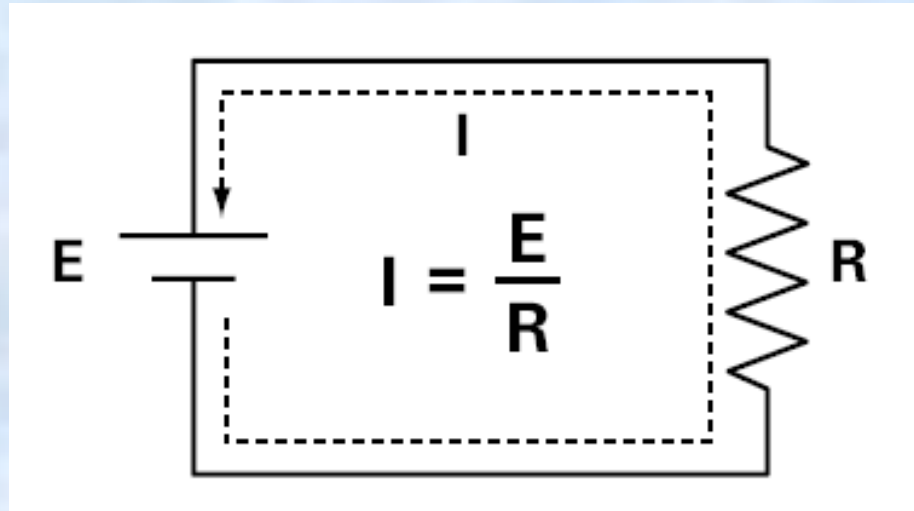
A simple electric circuit consists of a voltage source, some type of loads, and conductors to allow electrons to flow between the voltage source and the load.



Direct & Alternating current

There are two methods that voltage forces current to flow:

- Direct Current
- Alternating Current

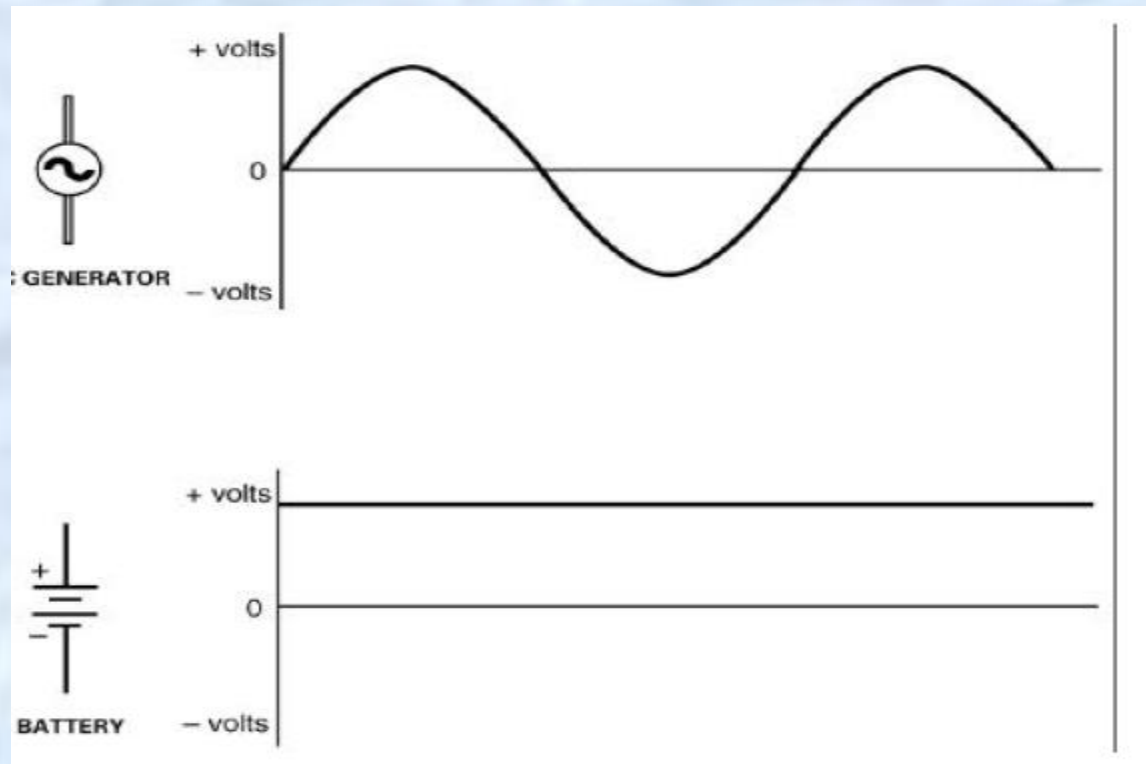

$$\text{peak} = \text{RMS} \times 1.414$$

Direct & Alternating current

DC (Thomas Edison)


Unidirectional (one way street)

AC (Nicolas Tesla)

Bidirectional (HZ) (number of alternating in a second
50 HZ === It is alternated 50 times in a second.

Electric Power

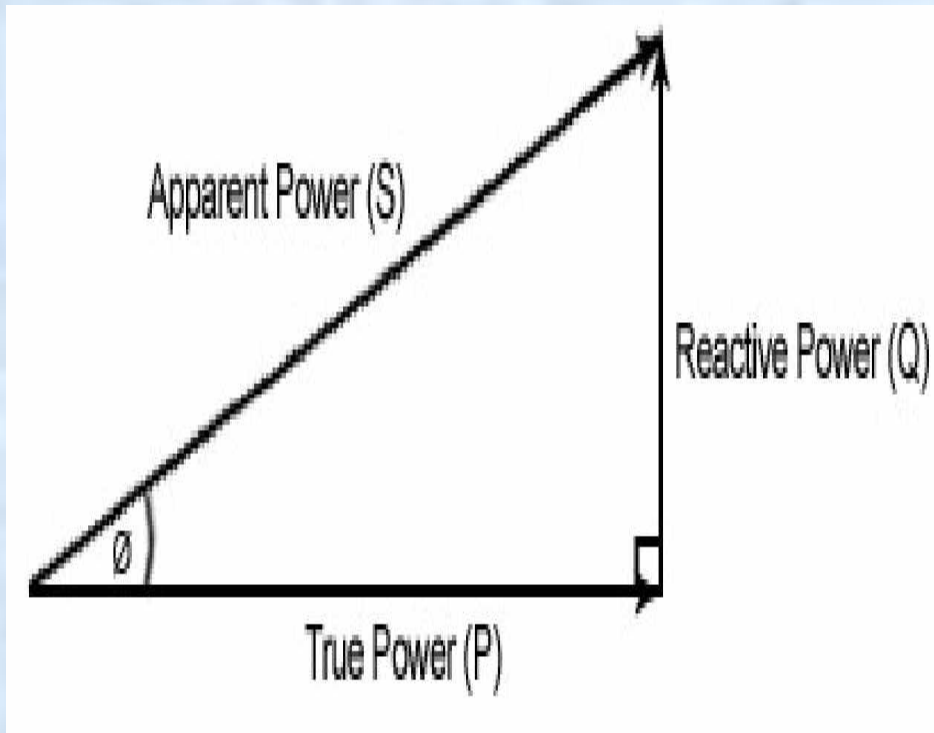The apparent power is a combination of both reactive power and true power. True power is a result of resistive components and reactive power is a result of capacitive and inductive components.



$$P = \text{true power} \quad P = I^2 R \quad P = \frac{E^2}{R}$$

*Measured in units of **Watts***

$$Q = \text{reactive power} \quad Q = I^2 X \quad Q = \frac{E^2}{X}$$

*Measured in units of **Volt-Amps-Reactive (VAR)***

$$S = \text{apparent power} \quad S = I^2 Z \quad S = \frac{E^2}{Z} \quad S = IE$$

*Measured in units of **Volt-Amps (VA)***

Formula Cheatsheet


1. Impedance $Z = R$ or X_L or X_C (if only one is present)
2. Impedance **in series only** $Z = \sqrt{R^2 + X^2}$ (if both R and one type of X are present)
3. Impedance **in series only** $Z = \sqrt{R^2 + (|X_L - X_C|)^2}$ (if R , X_L , and X_C are all present)
4. Impedance **in any circuit** $= R + jX$ (j is the imaginary number $\sqrt{-1}$)
5. Resistance $R = I / \Delta V$
6. Inductive reactance $X_L = 2\pi fL = \omega L$
7. Capacitive reactance $X_C = 1 / 2\pi fC = 1 / \omega C$

Resistive load only:

$$P = \text{true power} = I^2 R = 240 \text{ W}$$

$$Q = \text{reactive power} = I^2 X = 0 \text{ VAR}$$
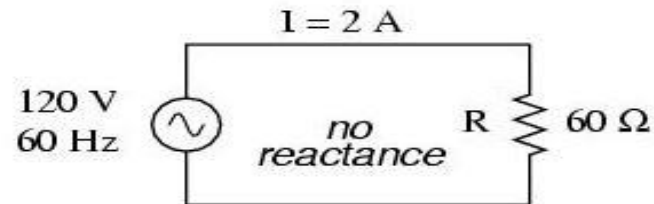
$$S = \text{apparent power} = I^2 Z = 240 \text{ VA}$$




Reactive load only:


$$P = \text{true power} = I^2 R = 0 \text{ W}$$

$$Q = \text{reactive power} = I^2 X = 238.73 \text{ VAR}$$
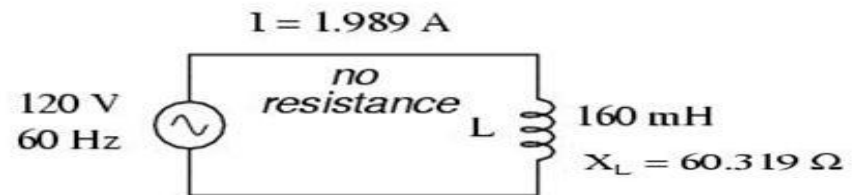
$$S = \text{apparent power} = I^2 Z = 238.73 \text{ VA}$$



Resistive/reactive load:

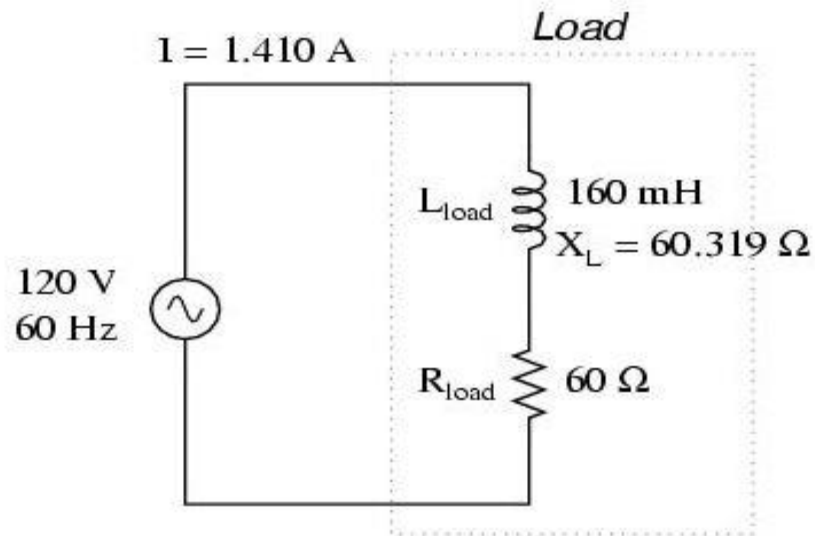

$$P = \text{true power} = I^2 R = 119.365 \text{ W}$$

$$Q = \text{reactive power} = I^2 X = 119.998 \text{ VAR}$$

$$S = \text{apparent power} = I^2 Z = 169.256 \text{ VA}$$

Magnetic field VS Electric field

Magnetic fields are created whenever there is a flow of electric current. This can also be thought of as the flow of water in a garden hose. As the amount of current flowing increases, the level of magnetic field increases. Magnetic fields are measured in milliGauss (mG).

An electric field occurs wherever a voltage is present. Electric fields are created around appliances and wires wherever a voltage exists. You can think of electric voltage as the pressure of water in a garden hose – the higher the voltage, the stronger the electric field strength. Electric field strength is measured in volts per meter (V/m). The strength of an electric field decreases rapidly as you move away from the source. Electric fields can also be shielded by many objects, such as trees or the walls of a building.

Electric Field

Magnetic Field

Nature Created around electric charge

Created around moving electric charge and magnets

Units Newton per coulomb, volts per meter

Gauss or Tesla

Force Proportional to the electric charge

Proportional to charge and speed of electric charge



Movement In Electromagnetic field Perpendicular to the magnetic field

Perpendicular to the electric field

Electromagnetic Field Generates VARS (Capacitive)

Absorbs VARS (Inductive)

Power Flow

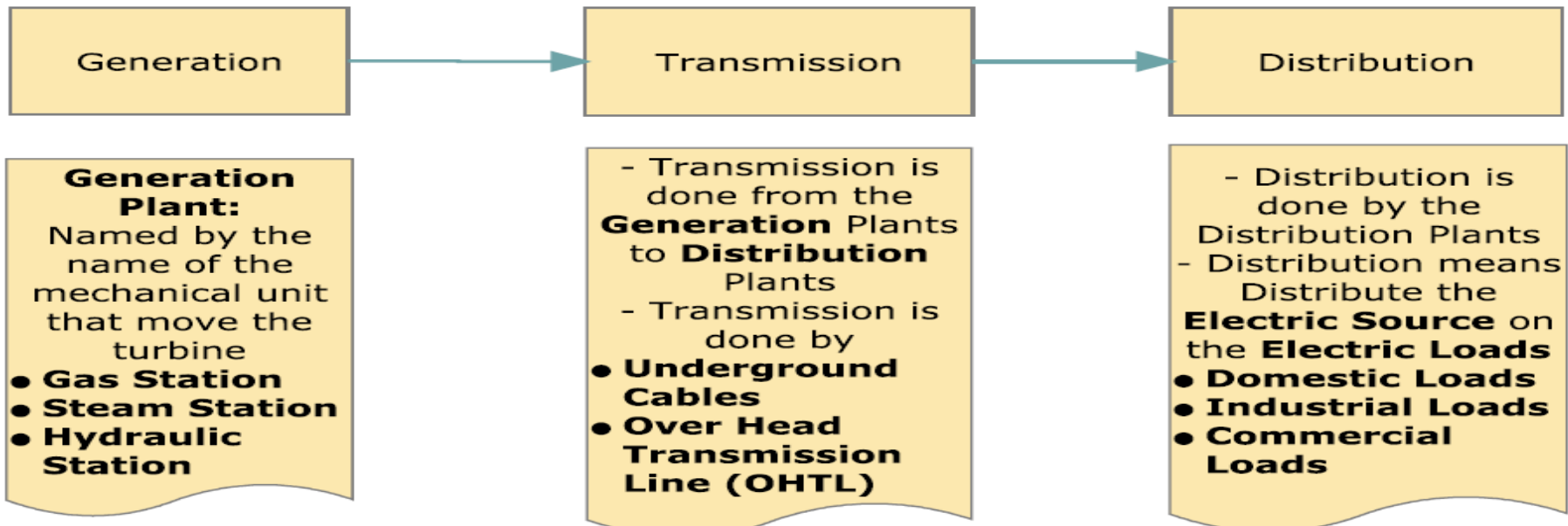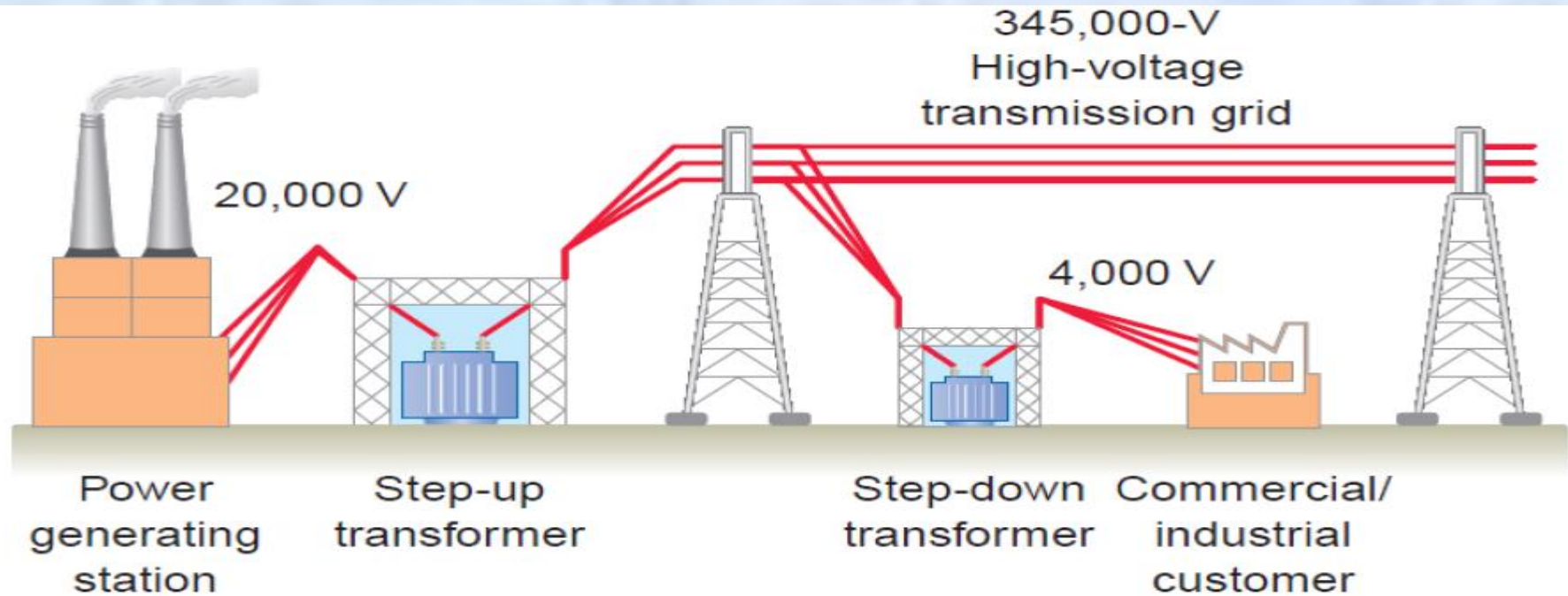

Energy Price

تعريفة عام ٢٠١٥ / ٢٠١٦ للاستخدامات المختلفة

مقابل القدرة ^(١) (جنيه / ك.و. شهر)		متوسط سعر الطاقة ^(٢) (قرش / ك.و.س)		خارج الذروة ^(٣) (قرش / ك.و.س)		داخل الذروة ^(٣) (قرش / ك.و.س)	
استخدامات الطاقة على الجهد الفائق (٢٢٠ – ١٣٢ ك . ف)							
كيما		=				٤,٧	
مترو الأنفاق		=				١٨,٠	
الصناعات الكثيفة ^(١)		١٥,٠	٣٩,٦	٣٦,٦		٥٤,٨	
باقي المشتركين		١٥,٠	٢٦,٩	٢٤,٨		٣٧,٢	
استخدامات الطاقة على الجهد العالي (٦٦ – ٢٢ ك . ف)							
مترو الأنفاق		-				٢٠,٥٠	
الصناعات الكثيفة ^(١)		٢٦,٠	٤١,١	٣٧,٩		٥٦,٩	
باقي المشتركين		٢٦,٠	٢٩,١	٢٦,٩		٤٠,٣	
استخدامات الطاقة على الجهد المتوسط (٢٢ – ١١ ك . ف)							
جميع المشتركين		٣٠,٠	٤٣,٥	٤٠,٢		٦٠,٢	
استخدامات الطاقة على الجهد المنخفض (٣٨٠ فولت)							
الرى						٢٢,٠	
باقي المشتركين						٤٦,٠	
إنارة عامة						٥٨,٠	
الاستخدامات المنزلية							
شرائح الاستهلاك (ك.و.س / شهر)				قرش / ك.و.س			
من ٠ – ٥٠				٧,٥			
من ٥١ إلى ١٠٠				١٤,٥			
١٠٠ إلى ٢٠٠				١٦,٠			
٢٠١ إلى ٣٥٠				٣٠,٥			
٣٥١ إلى ٦٥٠				٤٠,٥			
٦٥١ إلى ١٠٠٠				٧١,٠			
أكثر من ١٠٠٠				٨٤,٠			
الاستخدامات التجارية							
شرائح الاستهلاك (ك.و.س / شهر)				قرش / ك.و.س			
من ٠ – ١٠٠				٣٢,٠			
من ١٠٠ – ٢٥٠				٥٠,٠			
من ٢٥١ إلى ٦٠٠				٦١,٠			
٦٠١ إلى ١٠٠٠				٨١,٠			
أكثر من ١٠٠٠				٨٦,٠			

Energy Price

تعريفة الكهرباء لعام ٢٠١٧/٢٠١٦ للاستخدامات المختلفة

الاستخدام	مقابل القدرة (٢) (جنيه / ك.و.شهر)	متوسط سعر الطاقة (٤) (قرش/ك.و.س)	خارج الذروة (٣) (قرش/ك.و.س)	داخل الذروة (٣) (قرش/ك.و.س)
استخدامات الطاقة على الجهد الفائق (٢٢٠-١٣٢ ك.ف)				
كيما	—			٩,٤
مترو الأنفاق	—			٣٠,٠
الصناعات الكثيفة (١)	٢٥,٠	٤٦,٥	٤٢,٩	٦٤,٤
باقي المشتركين	٢٥,٠	٤١,٩	٣٨,٧	٥٨,١
استخدامات الطاقة على الجهد العالي (٦٦ ك.ف)				
مترو الأنفاق	—			٣٢,٠٠
الصناعات الكثيفة (١)	٣٥,٠	٤٩,٠	٤٥,٢	٦٧,٨
باقي المشتركين	٣٥,٠	٤٤,٦	٤١,١	٦١,٧
استخدامات الطاقة على الجهد المتوسط (٢٢-١١ ك.ف)				
جميع المشتركين	٤٥,٠	٥٢,٠	٤٨,٠	٧٢,٠
استخدامات الطاقة على الجهد المنخفض (٣٨٠ فولت)				
الري				٢٧,١
باقي المشتركين				٦٤,٤
انارة عامة				٧٥,٠
الاستخدامات المنزلية				
شرائح الاستهلاك (ك.و.س / شهر)		قرش/ك.و.س		
من ٥٠ - ٠		١١,٠		
من ٥١ الى ١٠٠		١٩,٠		
من ٠ الى ٢٠٠		٢١,٥		
من ٢٠١ الى ٣٥٠		٤٢,٠		
من ٣٥١ الى ٦٥٠		٥٥,٠		
من ٦٥١ الى ١٠٠٠		٩٥,٠		
من صفر لأكثر من ١٠٠٠		٩٥,٠		

Energy Price

ملحوظة ٢: لا تعتبر هذه المطالبة مخالصة عن مبالغ سابقة مستحقة للشركة المصرية لنقل الكهرباء.

Energy Price

رقم العداد	نوع العداد	رقم المحاولة	القراءة الحالية	الثابت	الاجمالي
	قياس اقصى حمل اثناء الذروة	٦٨	٤	١٠٠٠	٤٠٠٠
متوسط الحمل الشهري	الطاقة المستهلكة خلال الشهر	=	٢٣٥٤٥٨٠	٣١٦٥	٨٣٥
	عدد ساعات الشهر	=	٧٤٤		
متوسط الحمل الشهري	١٠٥	=	٣٣٢٣.٢٥		
	١٠٠				
بناء على الفقرة (ج) من البند الرابع من عقد توريد التيار الكهربى :					
فى حالة زيادة الحمل الأقصى خلال فترة الذروة عن ١٠٥% من متوسط الحمل الشهري					
يلتزم المنتفع بأداء مايقابل كامل الزيادة عن متوسط الحمل الشهري					
بسر قدره ٢ جنيه / كيلو وات					
فروق الاحمال					٨٣٥.٠٠
قيمة فروق الاحمال					١٦٧٠.٠٠
دمغات ورسوم					٠.٤١٠
احمال المطالبة (فقط وقدره ألف وستمائة وسبعون جنيها و١٤ قرش لاغير).					١٦٧٠.٤١

Energy Price

مقابل القدرة

اقصى حمل x 35 ج

نحيط سيادتكم علما أن مقابل القدره الذى تم المحاسبة عليه خلال الفترة من أكتوبر ٢٠١٦ / ديسمبر ٢٠١٦ أعلى أقصى حمل هو ١٣٥٠ ك.و (أسترشادى من الفترة السابقة) وحيث أنه تم تسجيل أقصى حمل وصلت إليه شركتكم فعلى خلال الفترة من أكتوبر ٢٠١٦ حتى ديسمبر ٢٠١٦ هو ٨٣٠ ك.و (فعلى) .




نتشرف بأن نرفق لسيادتكم التسوية الخاصة بفرق حساب مقابل القدره عن الفترة من ٢٠١٦/١٠/١ حتى ٢٠١٦/١٢/٣١ كالاتى:

ما تم المحاسبة عليه	أقصى حمل	السعر	القيمة شهريا	القيمة ٣ شهور
	١٣٥٠	٣٥٠٠	٤٧٢٥٠٠٠٠	١٤١٧٥٠٠٠٠
ما يجب المحاسبة عليه	أقصى حمل	السعر	القيمة شهريا	القيمة ٣ شهور
	٨٣٠	٣٥٠٠	٢٩٠٥٠٠٠٠	٨٧١٥٠٠٠٠


- الفرق المستحق لشركتكم من فرق مقابل القدره الذى تم المحاسبة عليه ٥٤٦٠٠.٠٠

Power factor

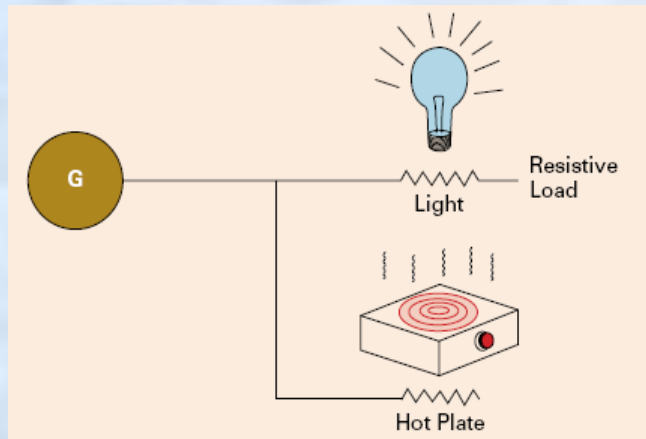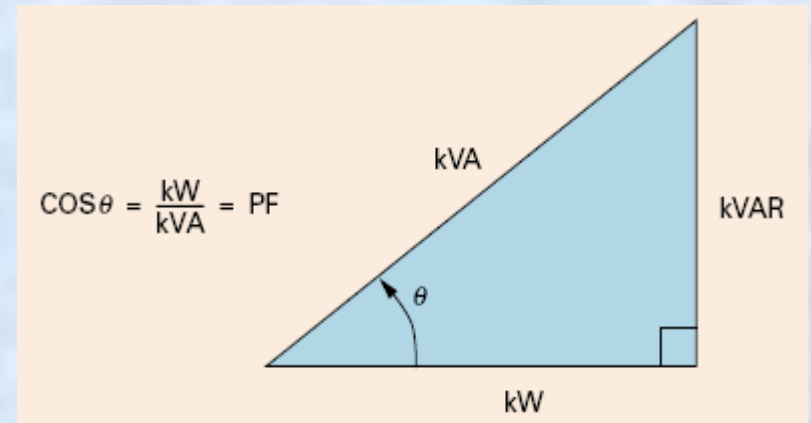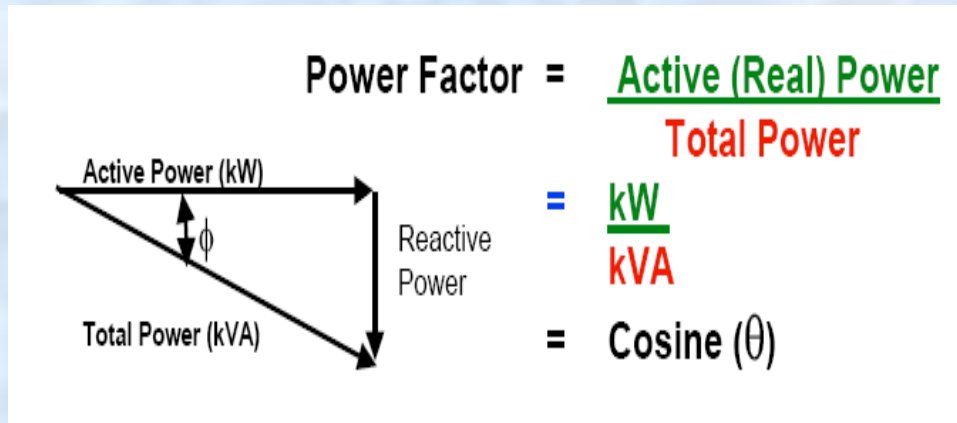
Power Factor is the ratio of Active Power to Total Power



P

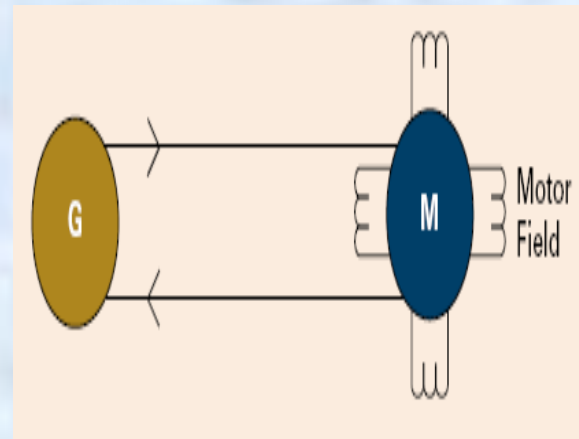


Q

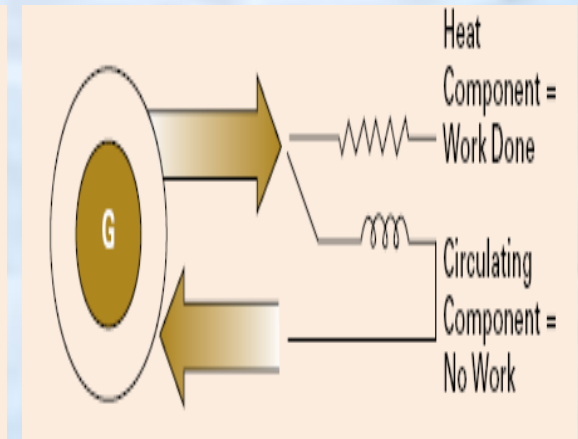

S

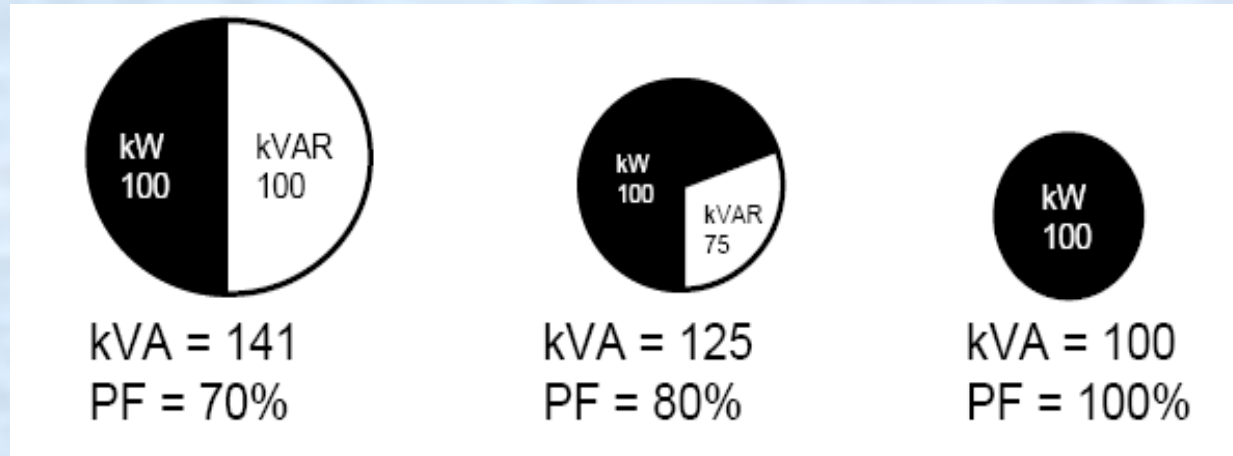The effect of PF on current drawn is shown below:



Decreasing size of conductors required to carry the same 100kW load at P.F. ranging from 70% to 100%


Why is Power Factor Important?

Consider the following example: A generator is rated at 600 V and supplies one of two possible loads.

Load 1: $P = 120 \text{ kW}$, $PF = 1$

Load 2: $P = 120 \text{ kW}$, $PF = 0.6$

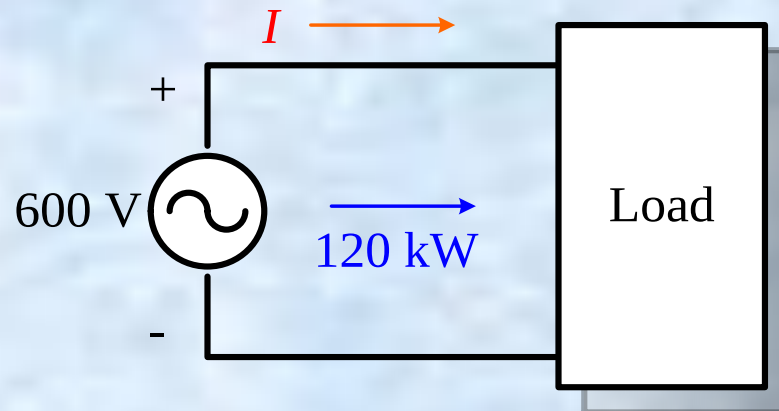How much current (I) is the generator required to supply in each case?




Why is Power Factor Important?

For the load with $PF = 0.6$, the generator had to supply 133 more amperes in order to do the same work (P)!

Larger current means larger equipment (wires, transformers, generators) which cost more.

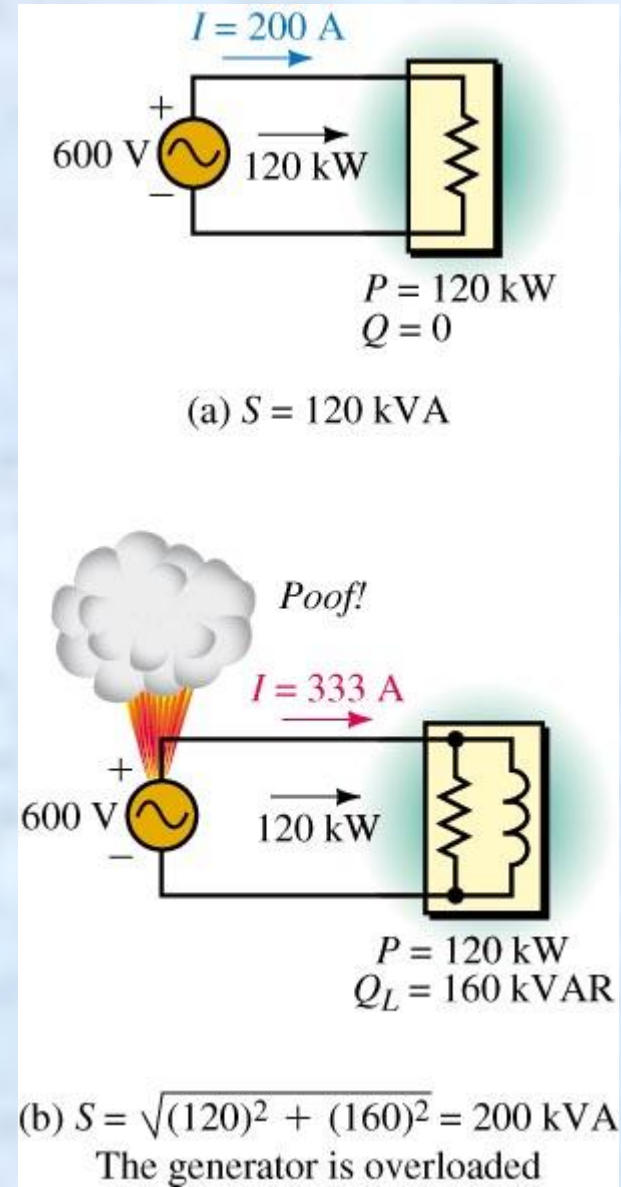
Larger current also means larger transmission losses (think I^2R).



Is it possible to change the power factor of the load?



Power Factor Correction

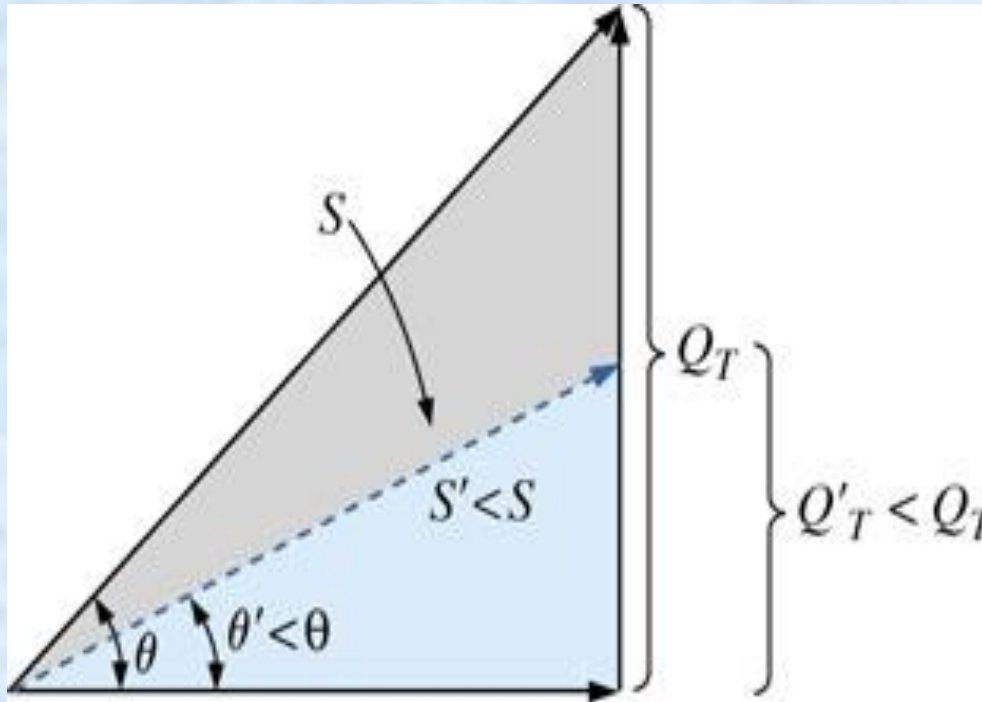

Demonstrating the impact of power-factor correction on the power triangle of a network.


Power Factor Correction

Almost all loads are inductive.

In order to cancel the reactive component of power, we must add reactance of the opposite type . This is called **power factor correction**.




P.F Regulator

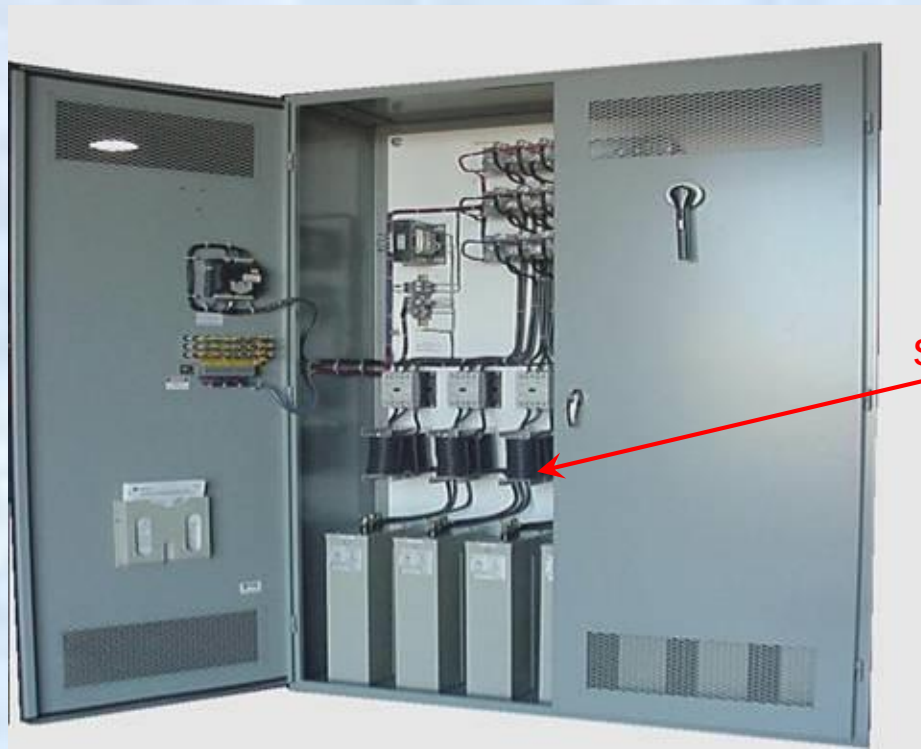

Capacitor bank in shipboard power panel for PF correction


Power Factor Correction

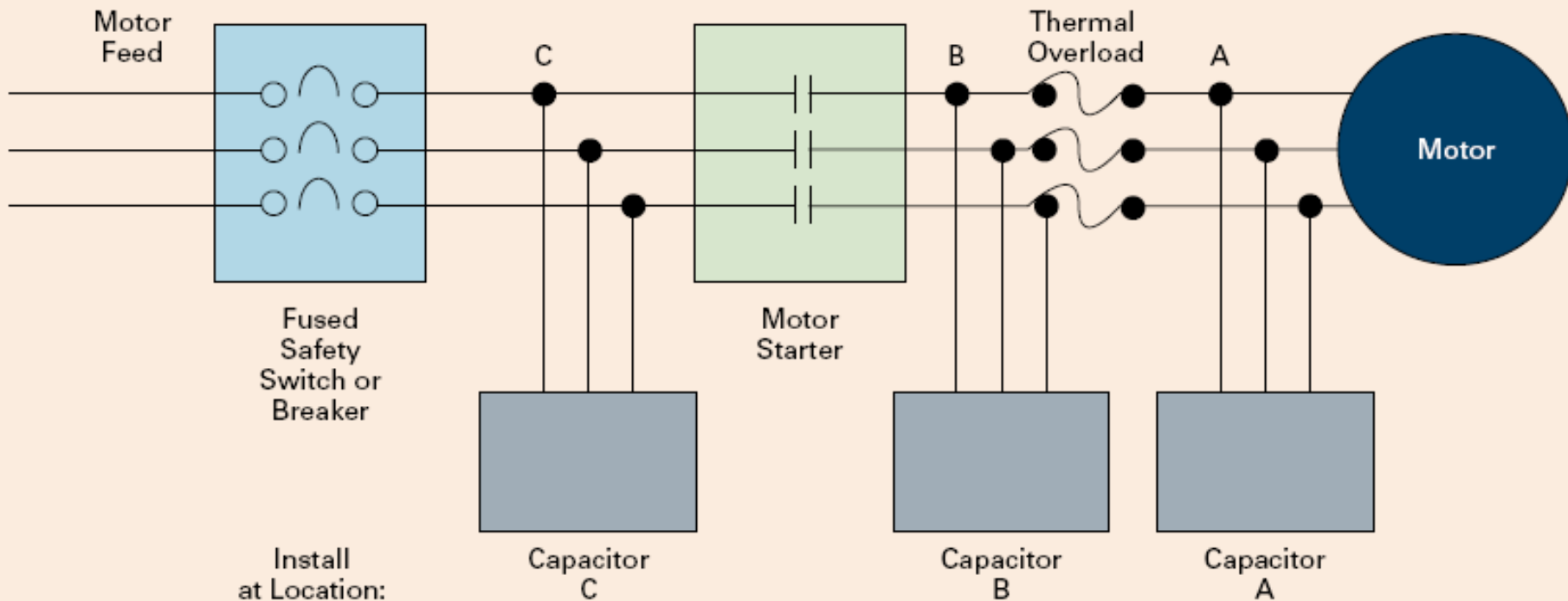

Power Factor Correction

In practice, almost all loads (commercial, industrial and residential) look ***inductive*** (due to motors, fluorescent lamp ballasts, etc.).

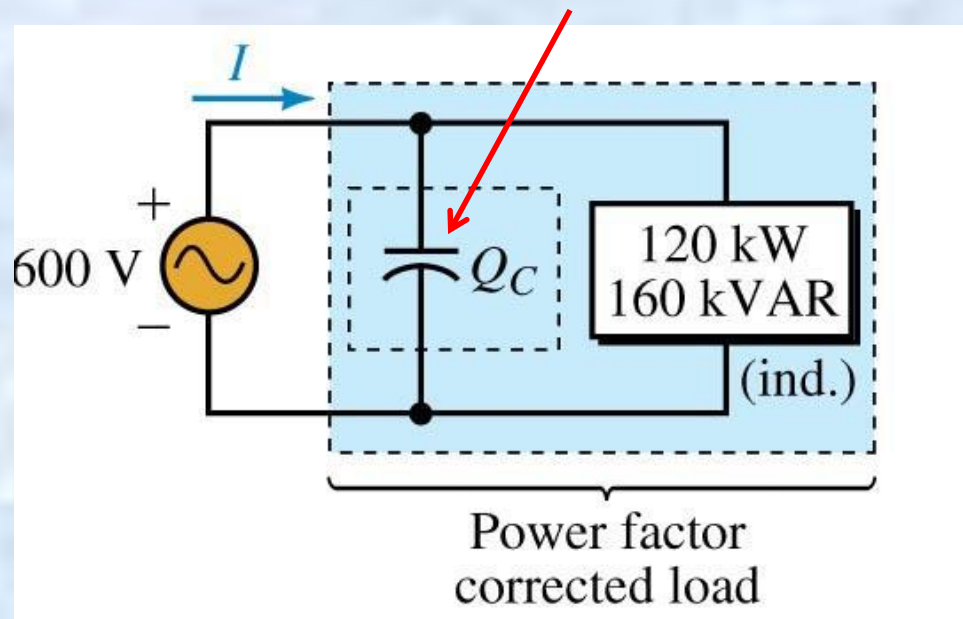Hence, almost all power factor correction consists of adding ***capacitance***.



Power Factor Correction Solution

Steps

- Calculate the reactive power (Q) of the load
- Insert a component in parallel of the load that will cancel out that reactive power

e.g. If the load has $Q_{LD}=512 \text{ VAR}$, insert a capacitor with $Q_C=-512 \text{ VAR}$.

- Calculate the reactance (X) that will give this value of Q Normally the $Q=V^2/X$ formula will work
- Calculate the component value (F or H) required to provide that reactance.

Power Factor Correction

$$Q_c = P (\tan (\cos^{-1} \Theta_1) - \tan (\cos^{-1} \Theta_2))$$

Existing Power Factor Cosθ ₁	Desired Power Factor [Proposed / Target P.F (Cosθ ₂)]																				Copy right @ http://electricaltechnology.org/
	0.80	0.81	0.82	0.83	0.84	0.85	0.86	0.87	0.88	0.89	0.90	0.91	0.92	0.93	0.94	0.95	0.96	0.97	0.98	0.99	
0.50	0.982	1.008	1.034	1.060	1.086	1.112	1.139	1.165	1.192	1.220	1.248	1.276	1.306	1.337	1.369	1.403	1.442	1.481	1.529	1.590	1.732
0.51	.937	.962	.989	1.015	1.041	1.067	1.094	1.120	1.147	1.175	1.203	1.231	1.261	1.292	1.324	1.358	1.395	1.436	1.484	1.544	1.687
0.52	.893	.919	.945	.971	.997	1.023	1.050	1.076	1.103	1.131	1.159	1.187	1.217	1.248	1.280	1.314	1.351	1.392	1.440	1.500	1.643
0.53	.850	.876	.902	.928	.954	.980	1.007	1.033	1.060	1.088	1.116	1.144	1.174	1.205	1.237	1.271	1.308	1.349	1.397	1.457	1.600
0.54	.809	.835	.861	.887	.913	.939	.966	.992	1.019	1.047	1.075	1.103	1.133	1.164	1.196	1.230	1.267	1.308	1.356	1.416	1.559
0.55	.769	.795	.821	.847	.873	.899	.926	.952	.979	1.007	1.035	1.063	1.090	1.124	1.156	1.190	1.228	1.268	1.316	1.377	1.519
0.56	.730	.756	.782	.808	.834	.860	.887	.913	.940	.968	.996	1.024	1.051	1.085	1.117	1.151	1.189	1.229	1.277	1.338	1.480
0.57	.692	.718	.744	.770	.796	.822	.849	.875	.902	.930	.958	.986	1.013	1.047	1.079	1.113	1.151	1.191	1.239	1.300	1.442
0.58	.655	.681	.707	.733	.759	.785	.812	.838	.865	.893	.921	.949	.976	1.010	1.042	1.076	1.114	1.154	1.202	1.263	1.405
0.59	.618	.644	.670	.696	.722	.748	.775	.801	.828	.856	.884	.912	.939	.973	1.005	1.039	1.077	1.117	1.165	1.226	1.368
0.60	.584	.610	.636	.662	.688	.714	.741	.767	.794	.822	.850	.878	.905	.939	.971	1.005	1.043	1.083	1.131	1.192	1.334
0.61	.549	.575	.601	.627	.653	.679	.706	.732	.759	.787	.815	.843	.870	.904	.936	.970	1.008	1.048	1.096	1.157	1.299
0.62	.515	.541	.567	.593	.619	.645	.672	.698	.725	.753	.781	.809	.836	.870	.902	.936	.974	1.014	1.062	1.123	1.265
0.63	.483	.509	.535	.561	.587	.613	.640	.666	.693	.721	.749	.777	.804	.838	.870	.904	.942	.982	1.030	1.091	1.233
0.64	.450	.476	.502	.528	.554	.580	.607	.633	.660	.688	.716	.744	.771	.805	.837	.871	.909	.949	.997	1.058	1.200
0.65	.419	.445	.471	.497	.523	.549	.576	.602	.629	.657	.685	.713	.740	.774	.806	.840	.878	.918	.966	1.027	1.169
0.66	.388	.414	.440	.466	.492	.518	.545	.571	.598	.626	.654	.682	.709	.743	.775	.809	.847	.887	.935	.996	1.138
0.67	.358	.384	.410	.436	.462	.488	.515	.541	.568	.596	.624	.652	.679	.713	.745	.779	.817	.857	.905	.966	1.108
0.68	.329	.355	.381	.407	.433	.459	.486	.512	.539	.567	.595	.623	.650	.684	.716	.750	.788	.828	.876	.937	1.079
0.69	.299	.325	.351	.377	.403	.429	.456	.482	.509	.537	.565	.593	.620	.654	.686	.720	.758	.798	.840	.907	1.049
0.70	.270	.296	.322	.348	.374	.400	.427	.453	.480	.508	.536	.564	.591	.625	.657	.691	.729	.769	.811	.878	1.020
0.71	.242	.268	.294	.320	.346	.372	.399	.425	.452	.480	.508	.536	.563	.597	.629	.663	.701	.741	.783	.850	.992
0.72	.213	.239	.265	.291	.317	.343	.370	.396	.423	.451	.479	.507	.534	.568	.600	.634	.672	.712	.754	.821	.963
0.73	.186	.212	.238	.264	.290	.316	.343	.369	.396	.424	.452	.480	.507	.541	.573	.607	.645	.685	.727	.794	.936
0.74	.159	.185	.211	.237	.263	.289	.316	.342	.369	.397	.425	.453	.480	.514	.546	.580	.618	.658	.700	.767	.909

$$Q_c = P * \text{Multiplier (get from table 0.536 if 0.7 to be 0.9)}$$

Formula

Power Factor penalty

If PF desire is 0,9

Actual PF = 0,87


D(PF) = 0,03

$$\text{Penalty (LE)} = D(\text{PF}) \times \text{LE/KWH} \times (\text{KWH})$$

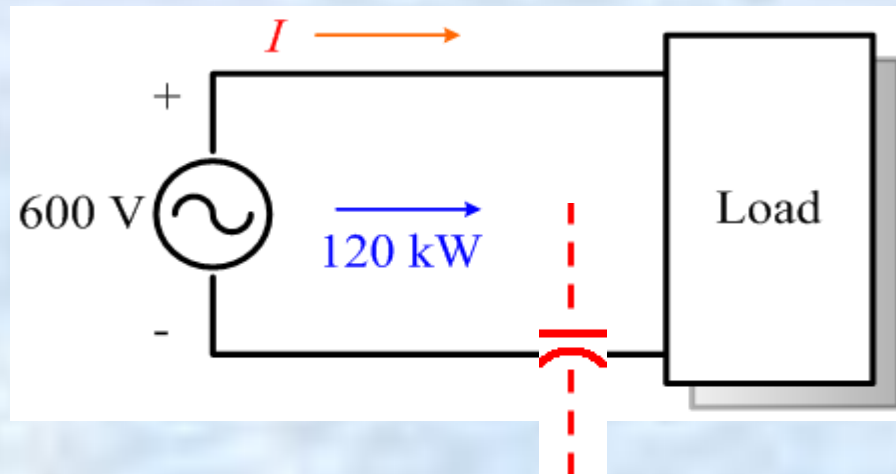Example

The 600 V (60 Hz) generator is connected to a load with $P_{LD} = 120 \text{ kW}$ and $Q_{LD} = 160 \text{ kVAR}$.

- Determine the power factor of the load.
- Determine the Capacitance (in Farads) required to correct the power factor to unity.



[Other Examples](http://www.electricaltechnology.org/2013/11/How-to-Calculate-Suitable-Capacitor-Size-for-Power-factor-Improvement.html)

<http://www.electricaltechnology.org/2013/11/How-to-Calculate-Suitable-Capacitor-Size-for-Power-factor-Improvement.html>

CHAPTER 2

Types of Control System

```
graph TD; A[Control Circuit] --> B[Classic Control]; A --> C[Modern Control]; B --> D[Magnetic]; B --> E[Digital];
```

Control
Circuit


Classic
Control

Modern
Control

Magnetic


Digital

1- Classic control

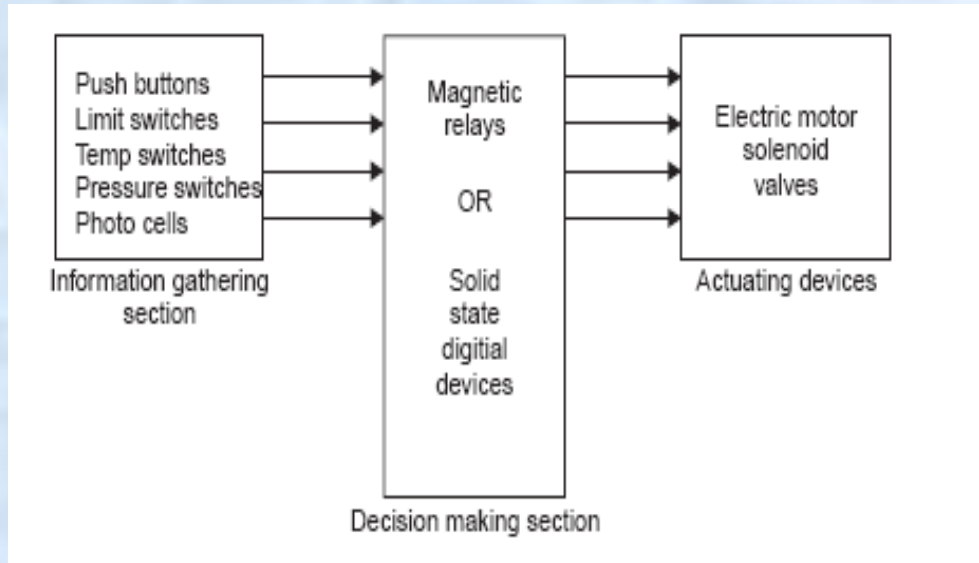



An industrial control system, whether it is magnetic control or static control can be divided into three

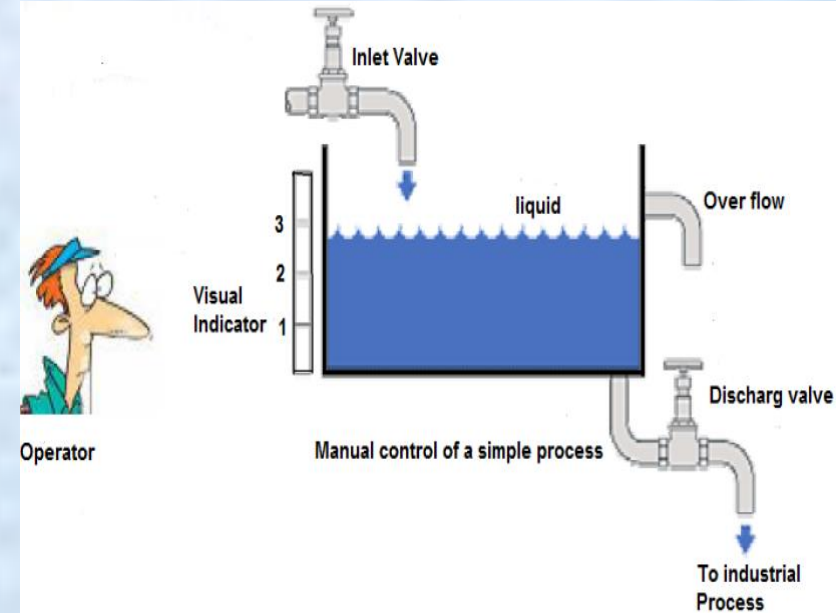- (i) input section
- (ii) logic section
- (iii) output section





A- Relay control System

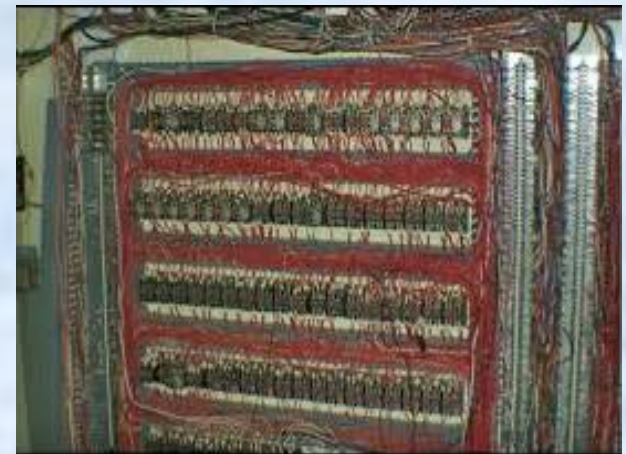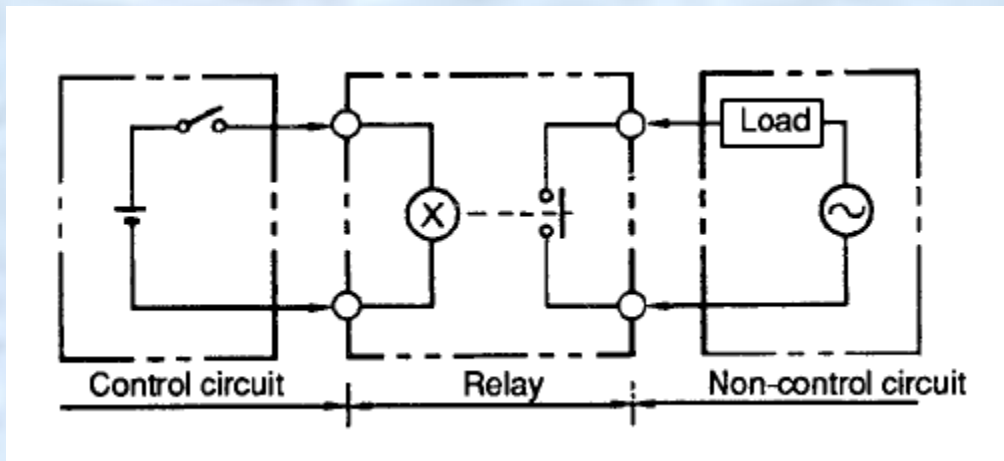A relay is defined as a device in which predefined changes occur rapidly in single or multiple electrical output circuits, when the control electrical input circuit fulfills a certain condition



RELAYS

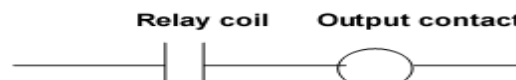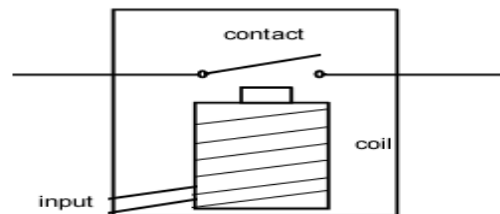
A switch whose operation is activated by an electromagnet is called a "relay"




B- Digital control System

- Digital ICs processing information through various logic gates
- Operate at much higher speeds & less power than relay circuit
- Advantage of small size but it cannot switch higher power signal


AND Gate

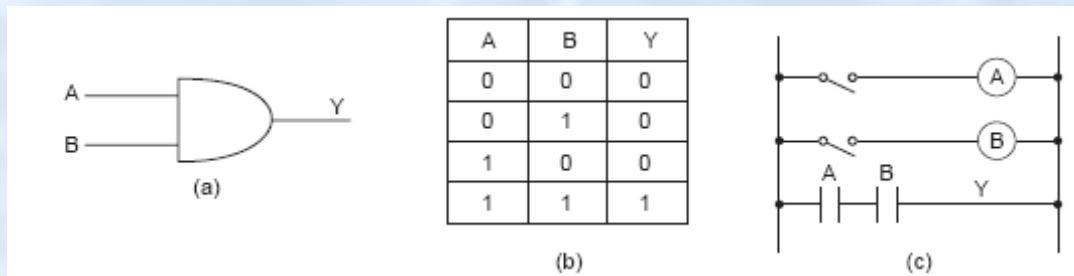





OR Gate

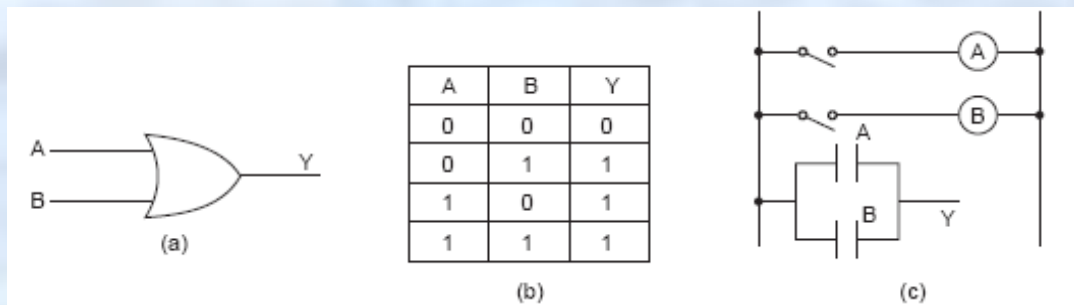











NOT Gate

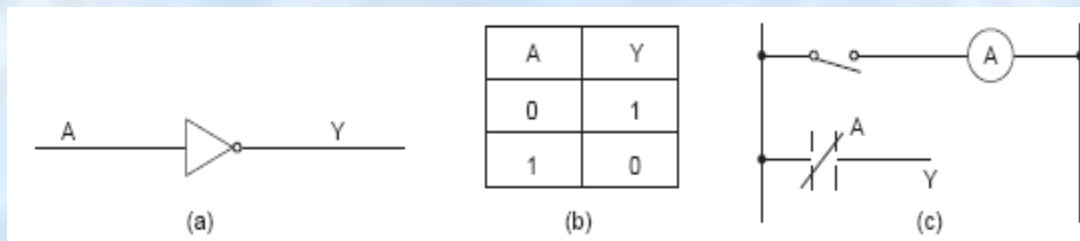

Example of both system

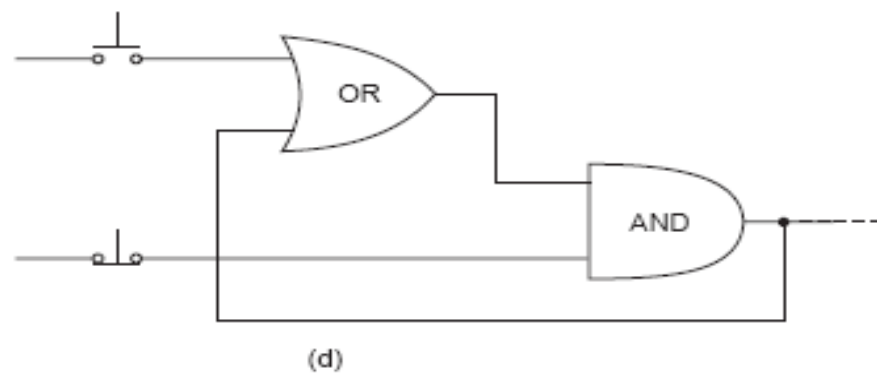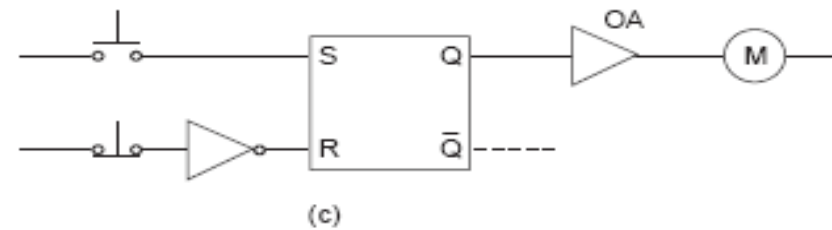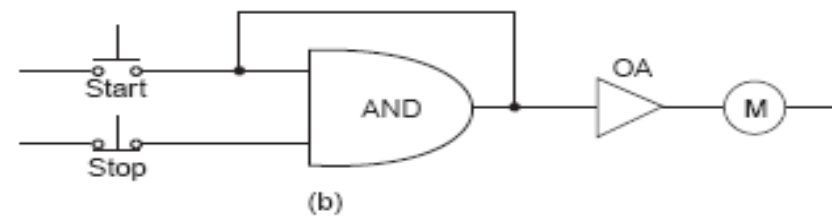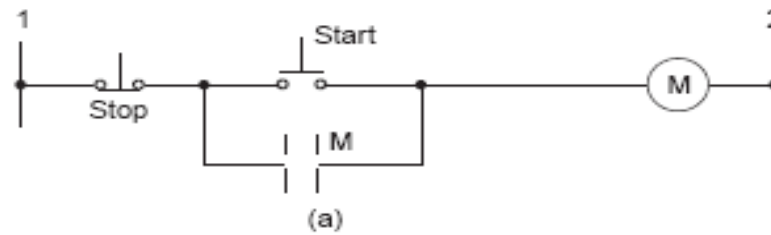

Other logic gates

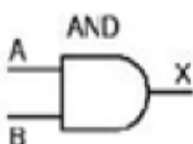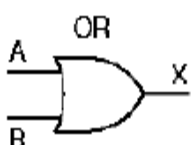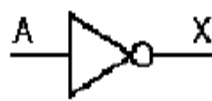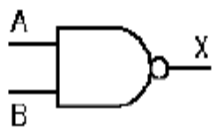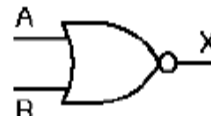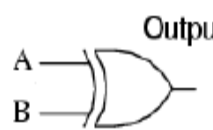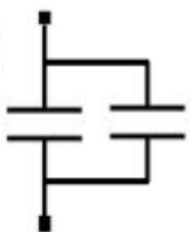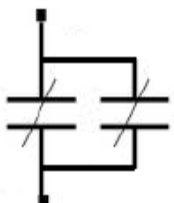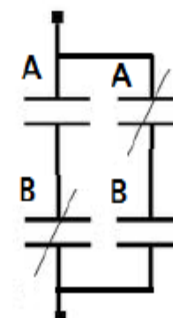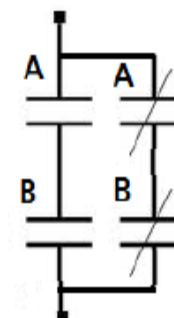AND	OR	NOT	NAND	NOR	EOR(XOR)	ENOR																																																																																																
AND  <table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	0	1	0	0	1	1	1	OR  <table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	1	 <table><tr><th>A</th><th>X</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	X	0	1	1	0	 <table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	1	1	0	1	1	1	0	 <table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	0	Output  <table><tr><th>A</th><th>B</th><th>Output</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	Output	0	0	0	0	1	1	1	0	1	1	1	0	 <table><tr><th>A</th><th>B</th><th>O</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	O	0	0	1	0	1	0	1	0	0	1	1	1
A	B	X																																																																																																				
0	0	0																																																																																																				
0	1	0																																																																																																				
1	0	0																																																																																																				
1	1	1																																																																																																				
A	B	X																																																																																																				
0	0	0																																																																																																				
0	1	1																																																																																																				
1	0	1																																																																																																				
1	1	1																																																																																																				
A	X																																																																																																					
0	1																																																																																																					
1	0																																																																																																					
A	B	X																																																																																																				
0	0	1																																																																																																				
0	1	1																																																																																																				
1	0	1																																																																																																				
1	1	0																																																																																																				
A	B	X																																																																																																				
0	0	1																																																																																																				
0	1	0																																																																																																				
1	0	0																																																																																																				
1	1	0																																																																																																				
A	B	Output																																																																																																				
0	0	0																																																																																																				
0	1	1																																																																																																				
1	0	1																																																																																																				
1	1	0																																																																																																				
A	B	O																																																																																																				
0	0	1																																																																																																				
0	1	0																																																																																																				
1	0	0																																																																																																				
1	1	1																																																																																																				
 Serial	 Parallel	 NOT	 NAND	 NOR	 XOR	 XNOR																																																																																																

2- Modern control


The early history of the PLC & DCS goes back to the 1960's when control systems were still handled using relay control. During this time the control rooms consisted of several walls containing many relays, terminal blocks and mass of wires. The problems related to such kind of systems were many, among those one could mention:

- The lack of flexibility
- Troubleshooting.



"necessity is the mother of invention"

The SIMATIC S7 System Family

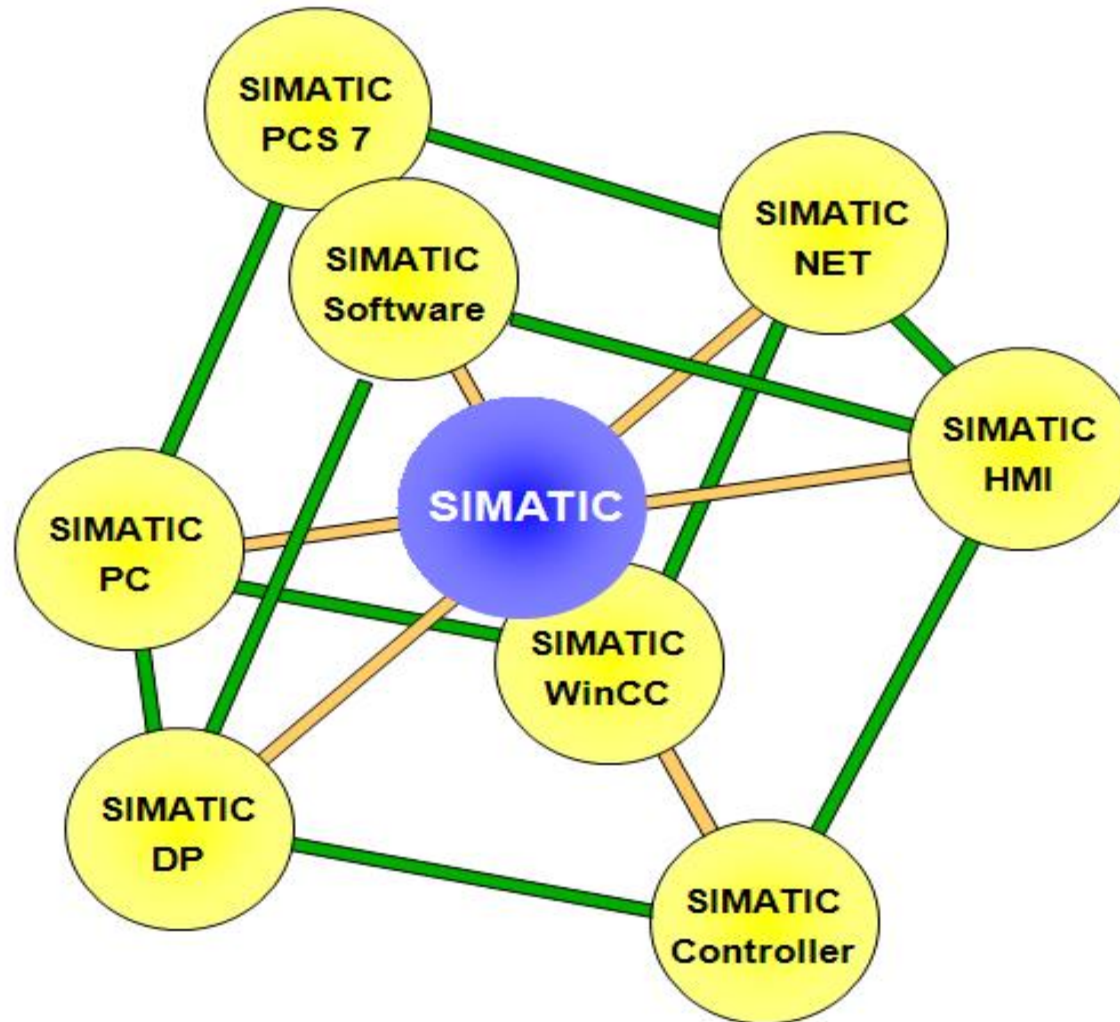

```
graph TD; A[Control System] --> B[Classic Control]; A --> C[Intelligent Control]
```

**Control
System**

**Classic
Control**


**Intelligent
Control**

1- Classic control

the designer constructs a mathematical model of the system. This model contains all the dynamics of the plant that affects controlling it.


A- Open loop

$$U = K \cdot D$$

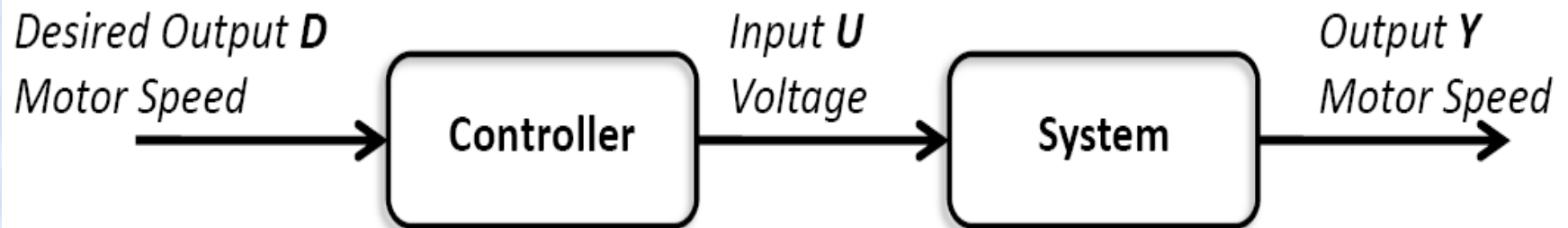


B- Closed loop


$$U = K \cdot (D - Y)$$

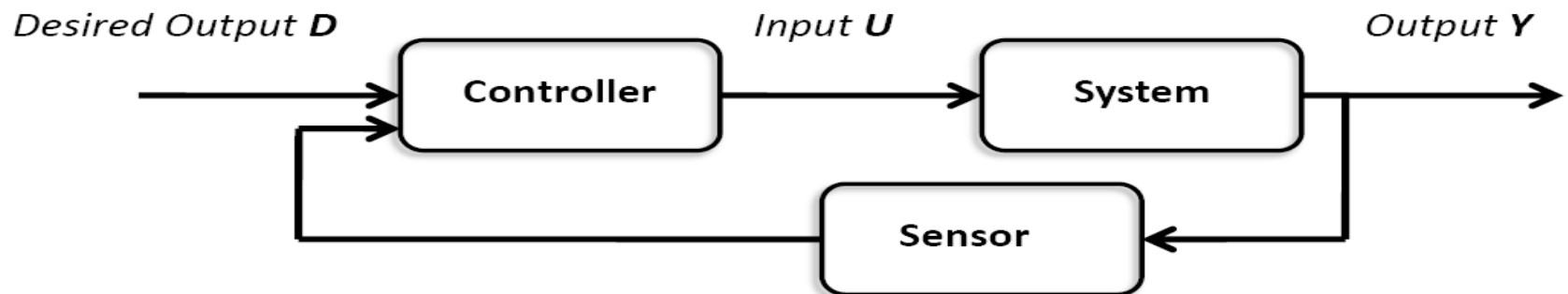


System modeling & Stability

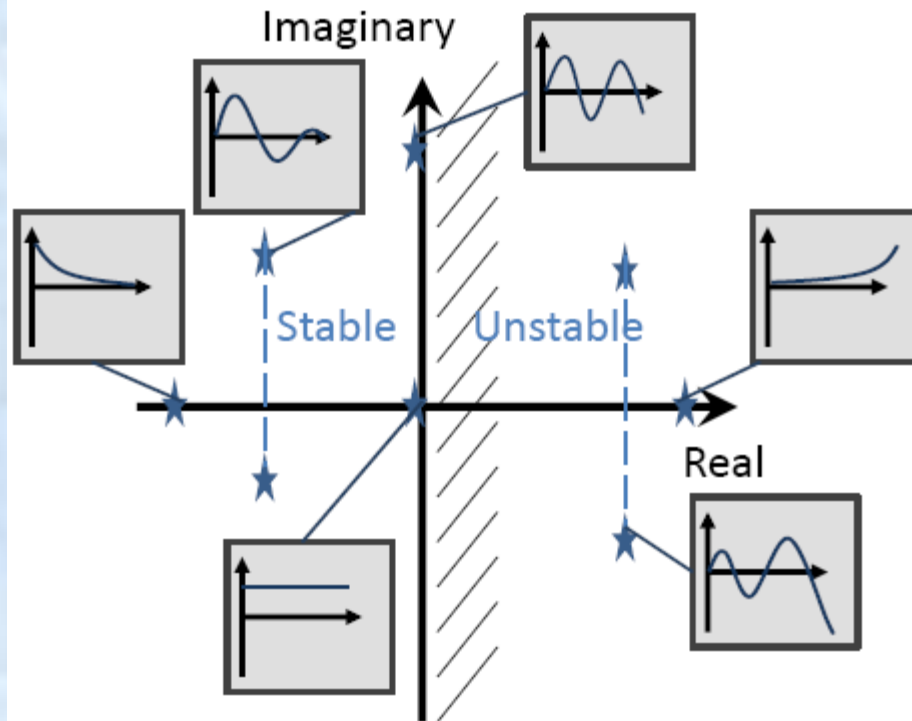

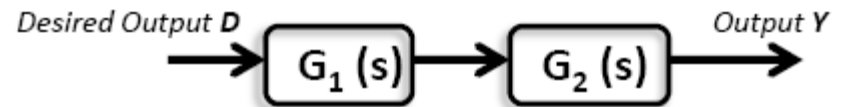
Roots of Characteristic equation
determine stability



$$Y = G_1(s) G_2(s) D$$

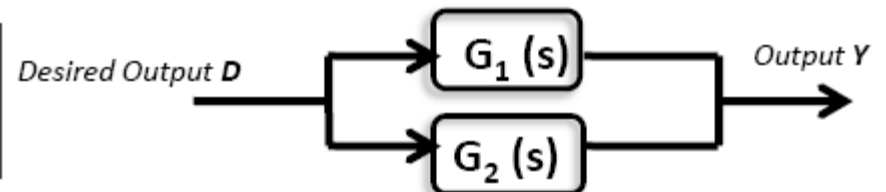


$$Y = G_1(s) + G_2(s) D$$

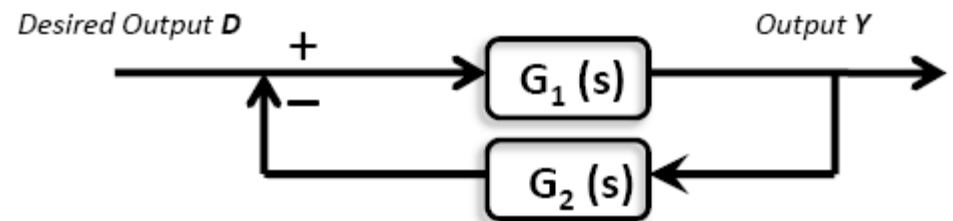

$$Y = \frac{G_1(s)}{1 + G_1(s)G_2(s)} \times D$$

Closed Loop Stability

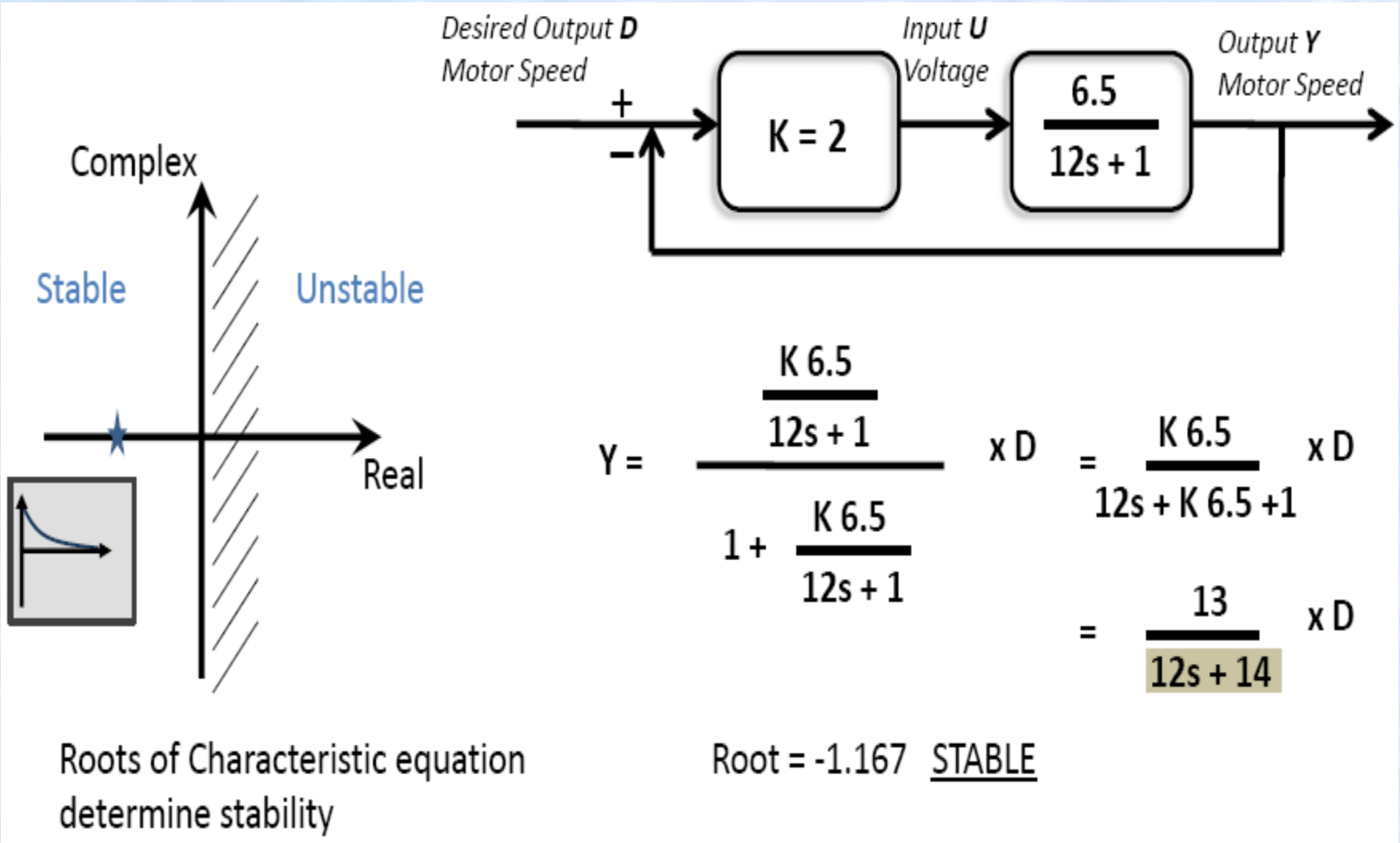

Control Requirement PID

Proportional Gain

Applicable to Error between setpoint & output

Larger values $\rightarrow$ faster response

Very large values $\rightarrow$ process instability and oscillation.

Results in Steady State Error

Integral Gain

Proportional to integral of Error between setpoint & output

Larger values $\rightarrow$ steady state errors rapidly eliminated.

Overshoot may lead to instability



Zero Steady State Error

Derivative Gain


Proportional to derivative of Error between setpoint & output

Larger values $\rightarrow$ decreased overshoot, but slower transient response

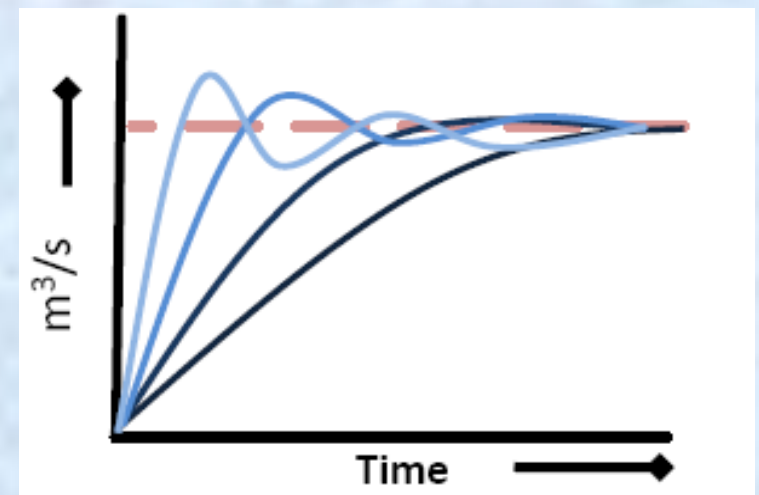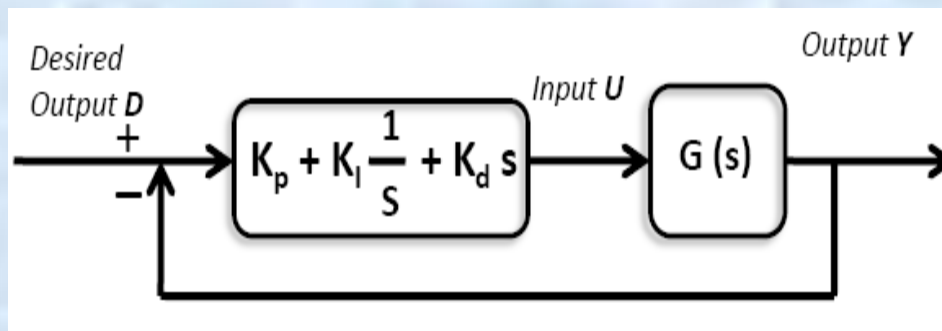May lead to instability due to signal noise amplification in the differentiation of the error



Explain this video

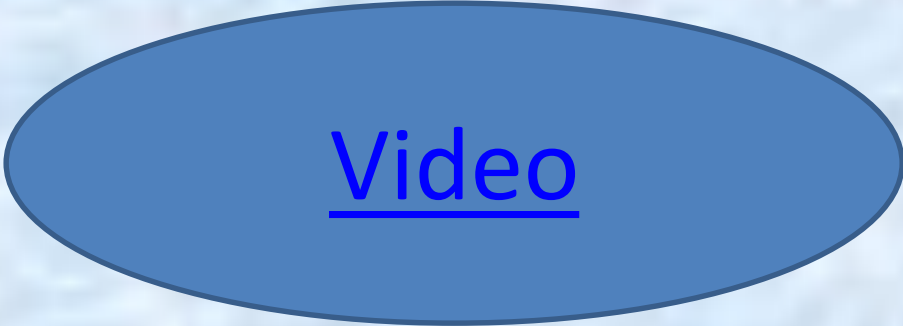


Video

CHAPTER 3

Classic Control


Components

Process flow sheet

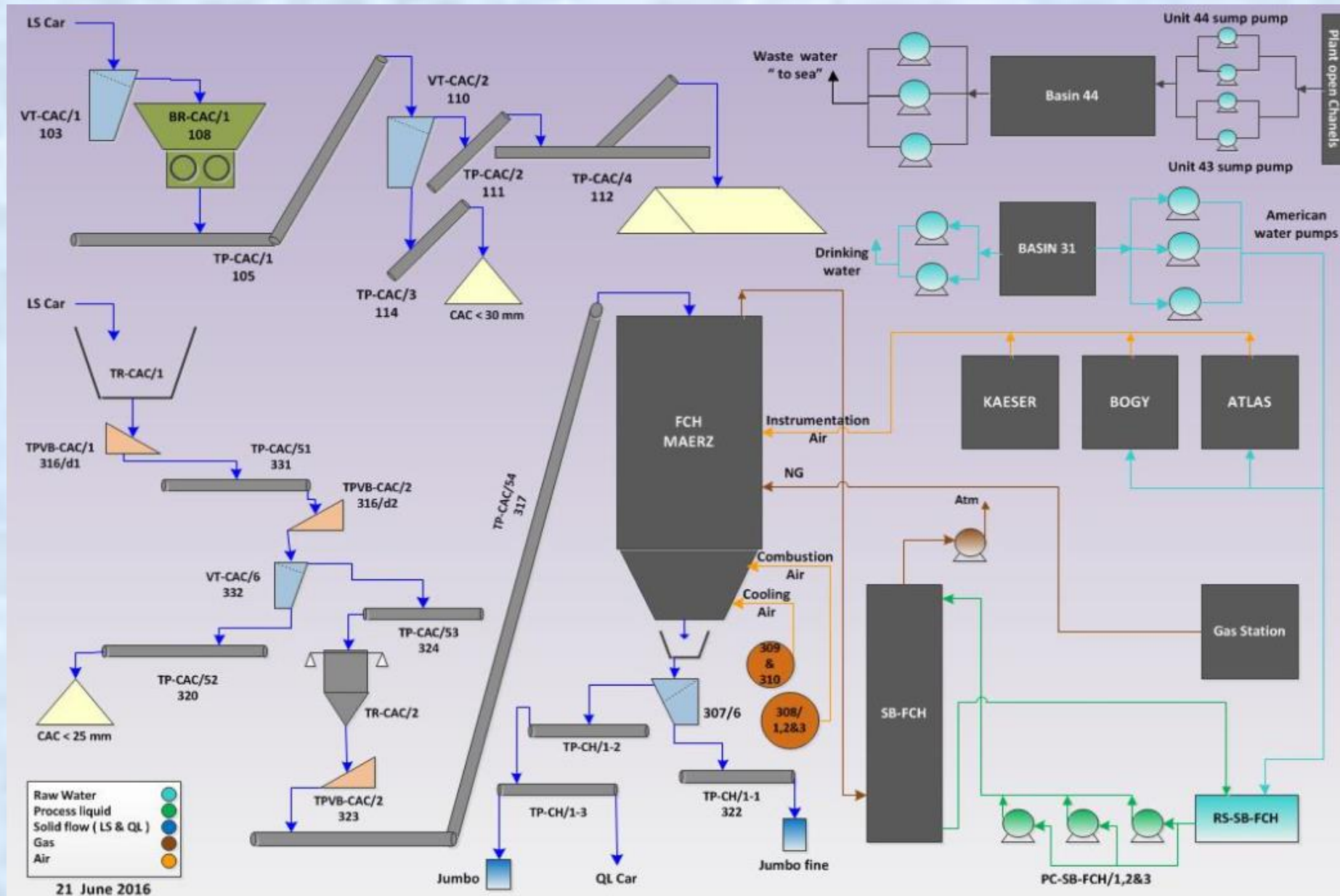


Power circuit


3NPE ~50Hz, 220V/380V TT SYSTEM

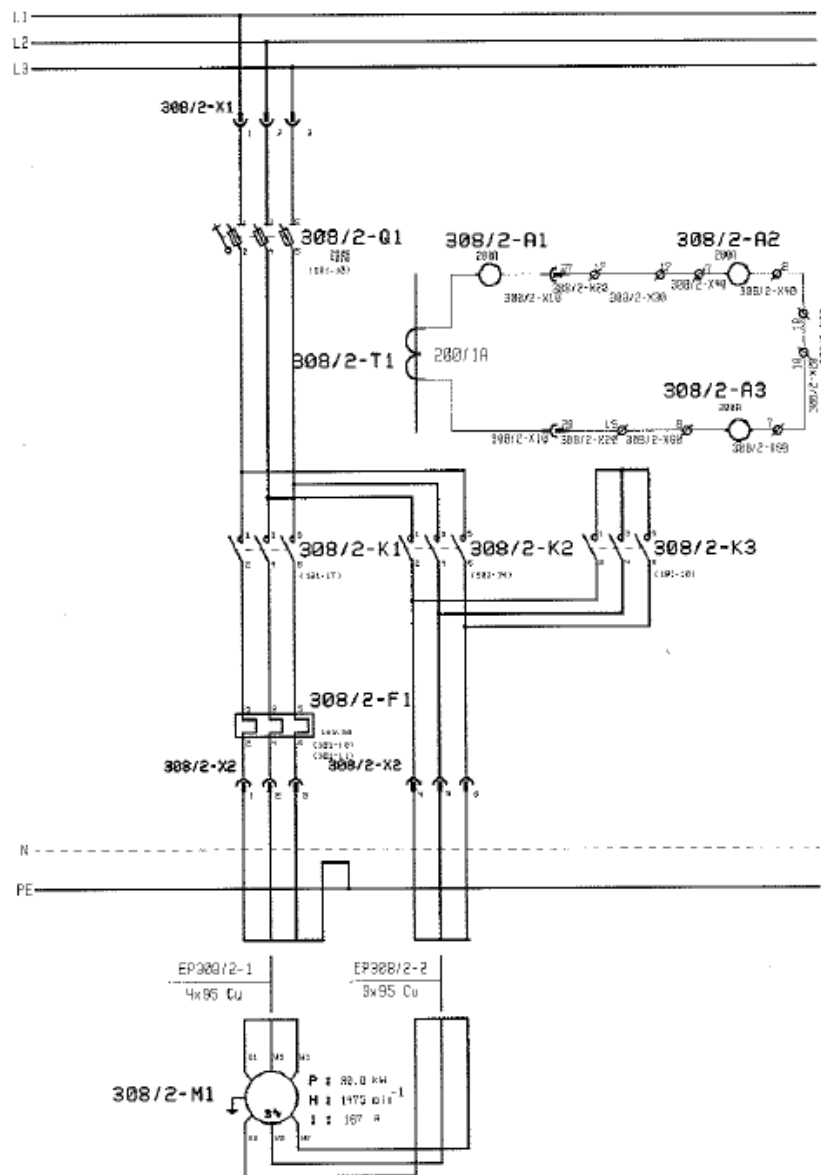

3NPE, 50Hz, 220V/380V TT SYSTEM



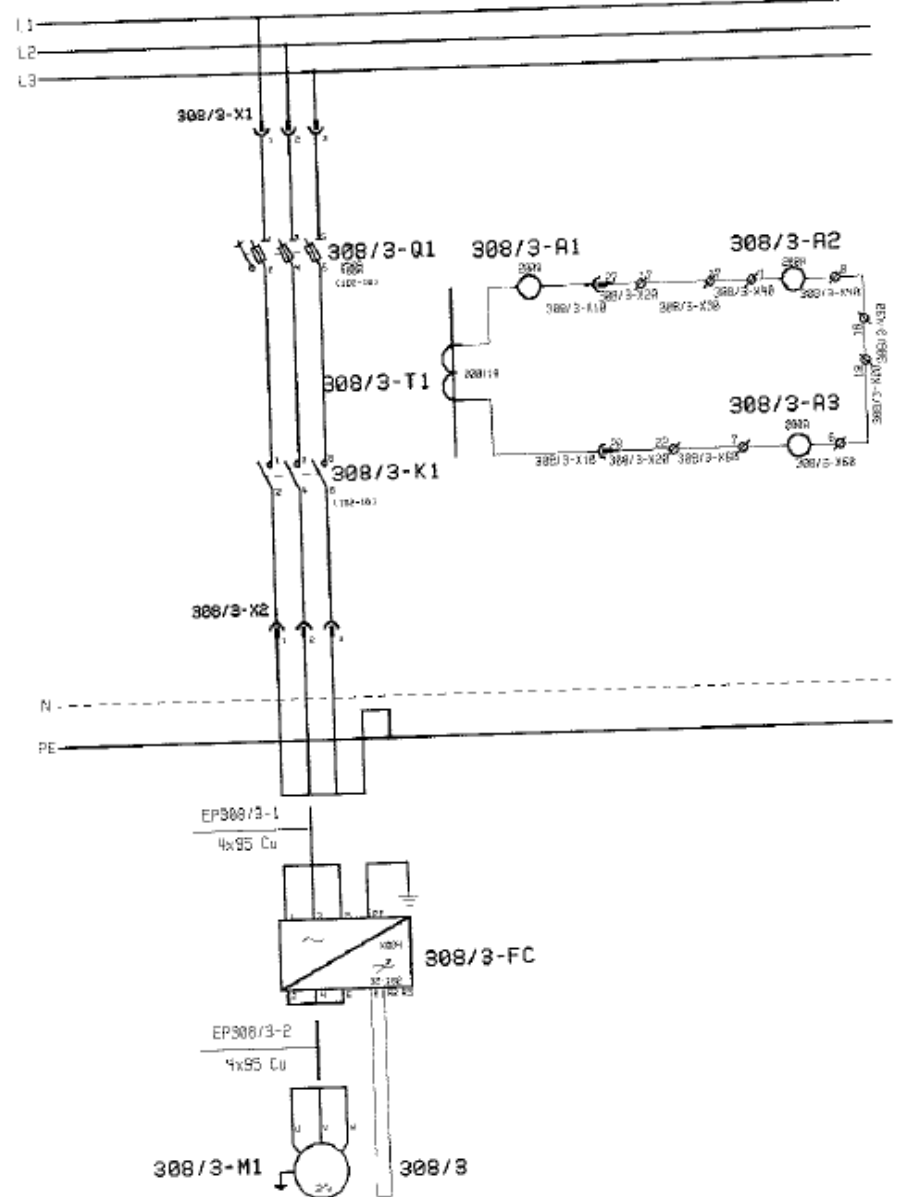


Control circuit

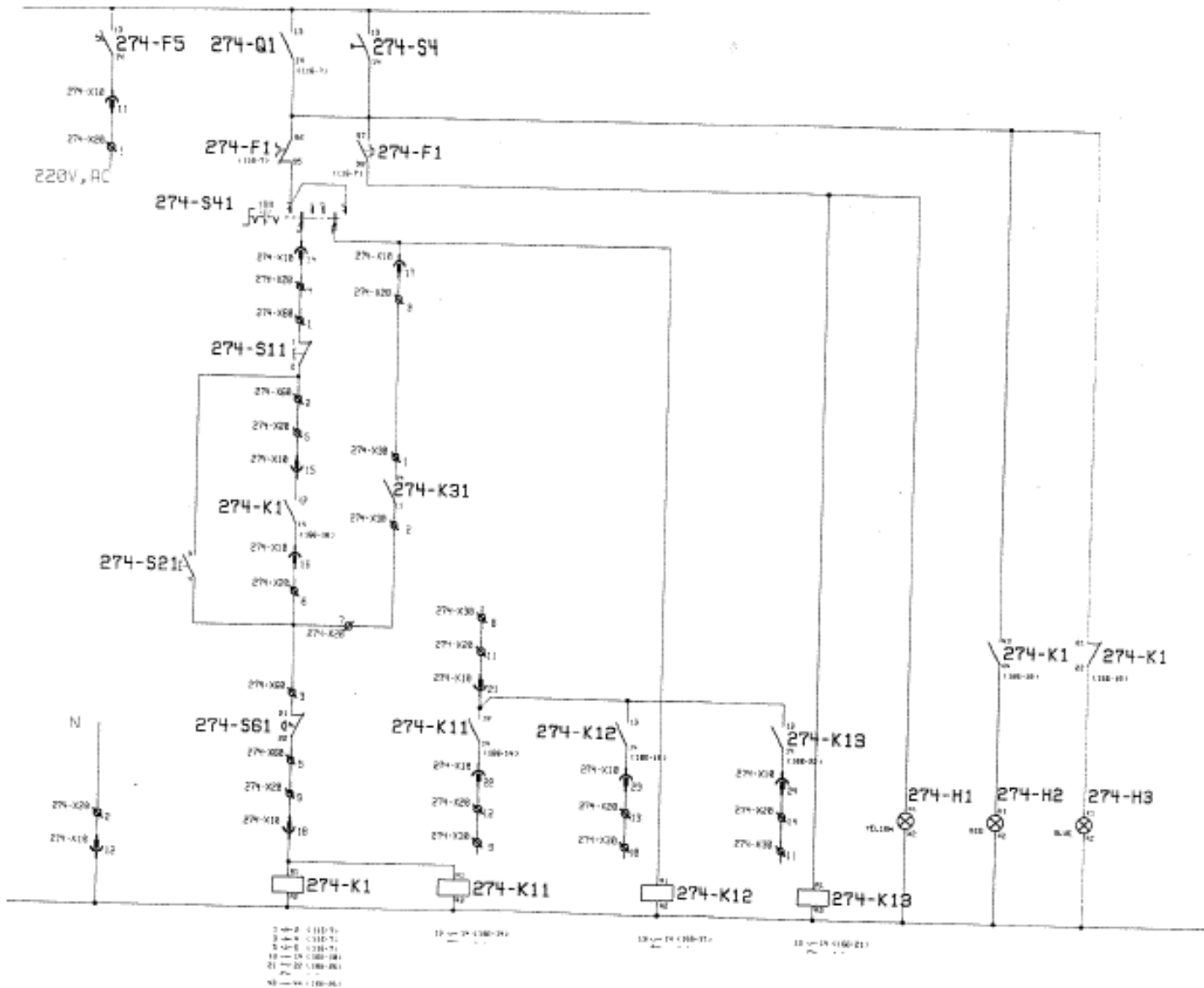


Power & control circuit

To 3- ϕ , 480 volt power source

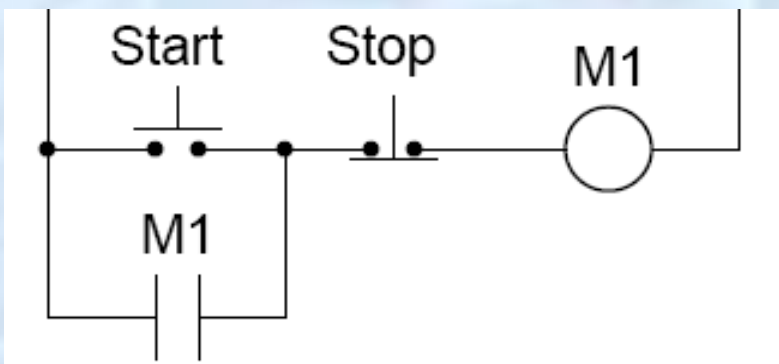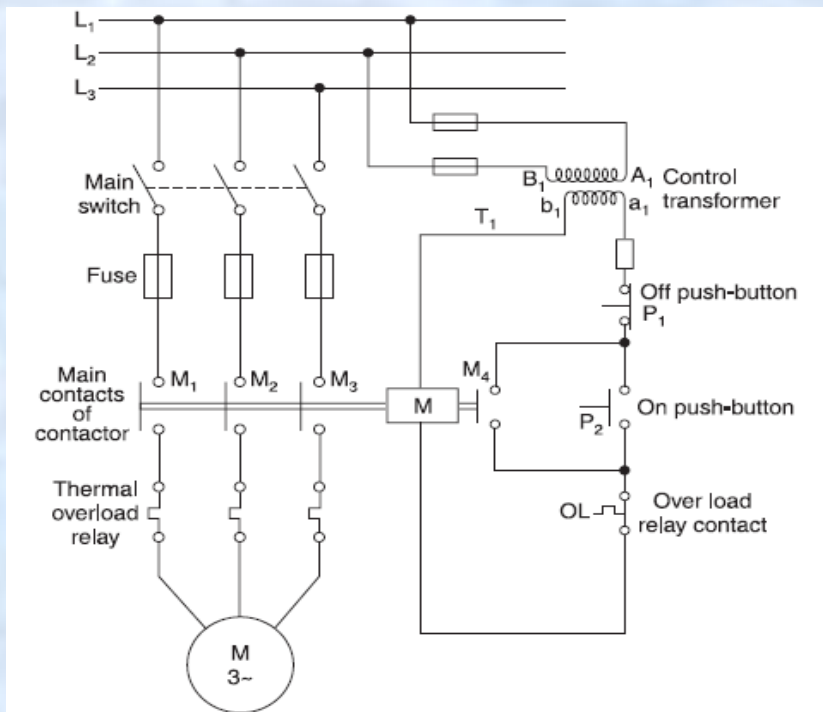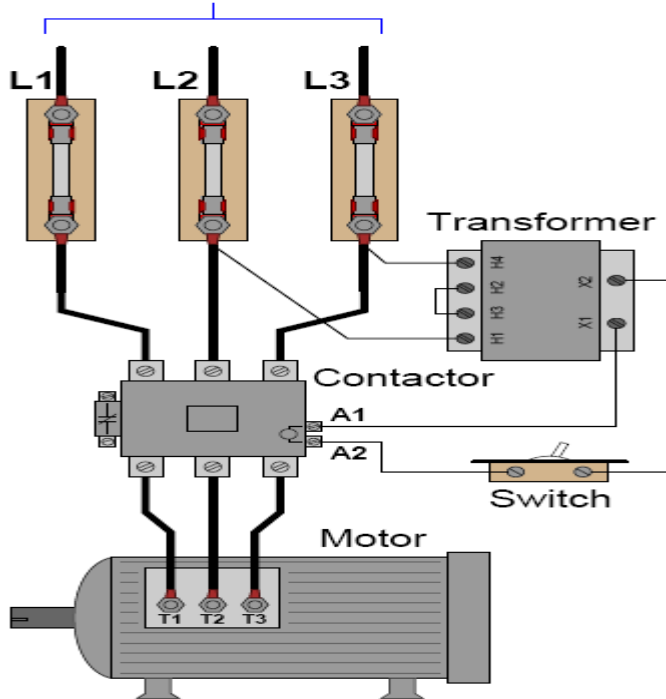



Control circuit

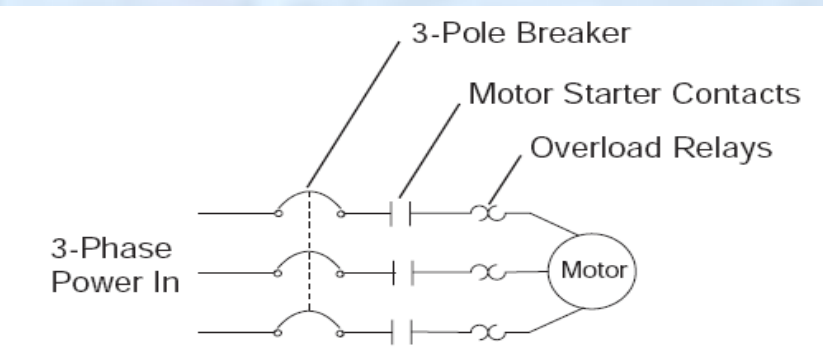

Power circuit



Power circuit components

Fuses

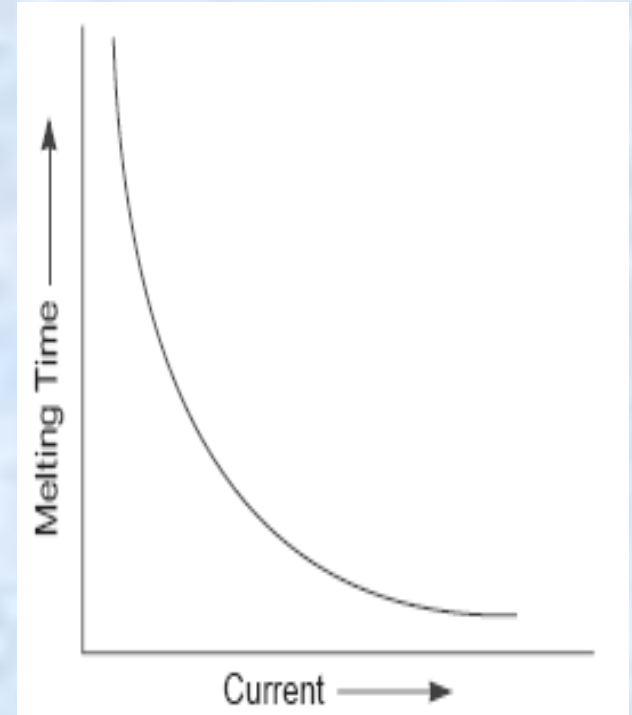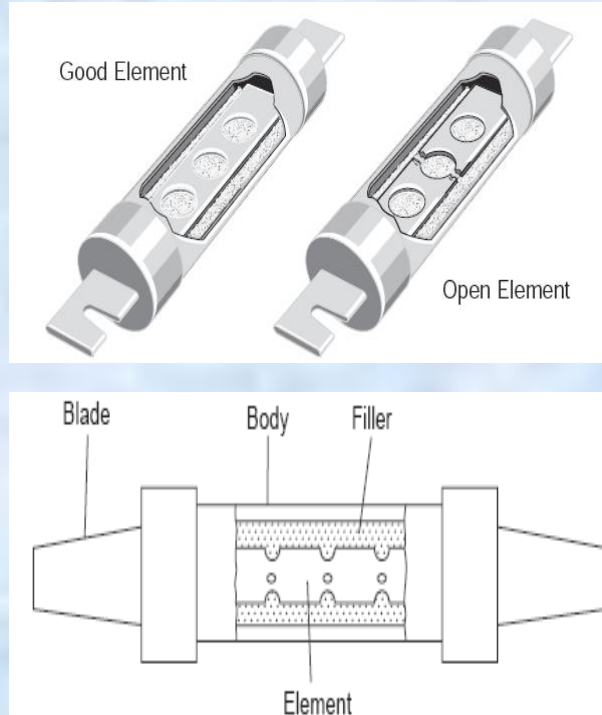


The fuse element can sustain small overloads for longer duration but in case of large overloads and short circuits the small cross-section of the fuse element melts quickly and opens the circuit.

Circuit Breaker

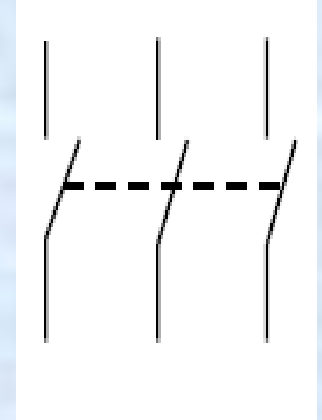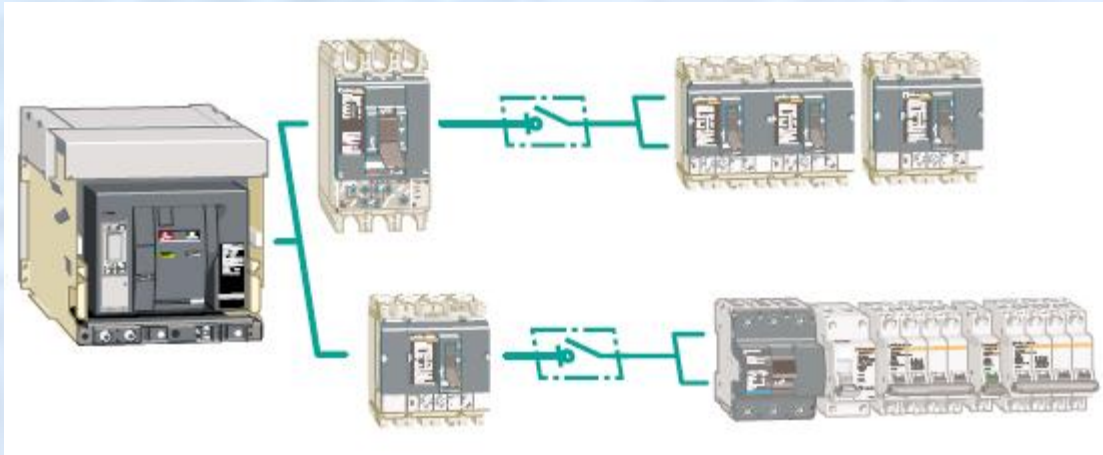


An MCCB automatically isolates an electrical circuit under sustained overloads or short circuits.

Video

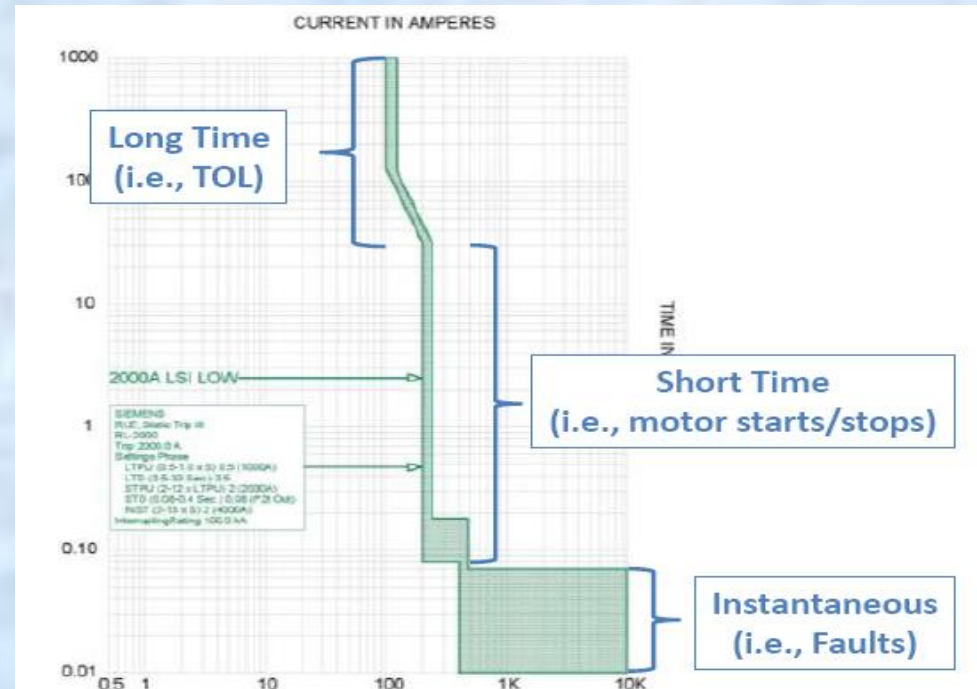


Name plate

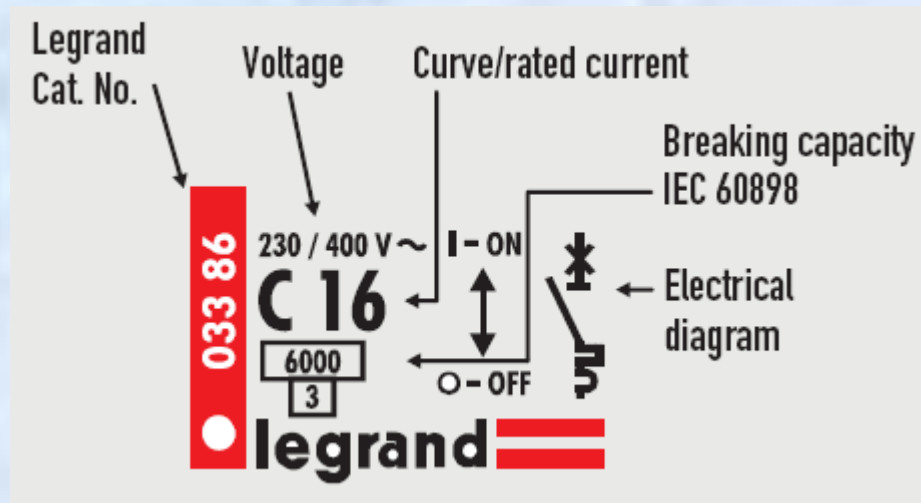


Tripping curve

Thermal-magnetic release

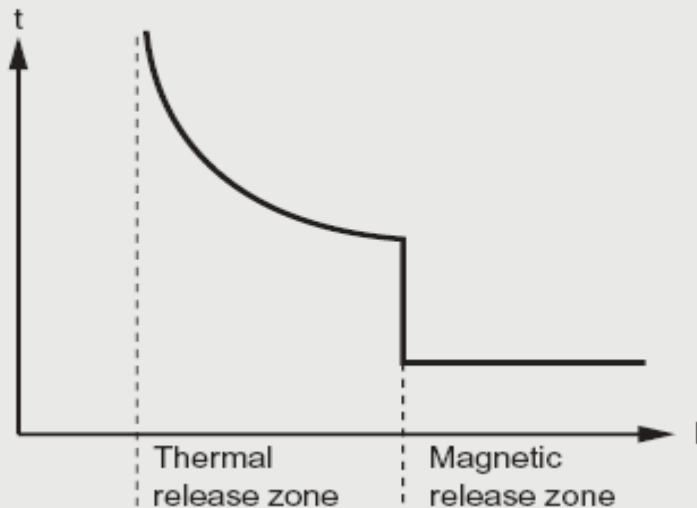


Electronic release

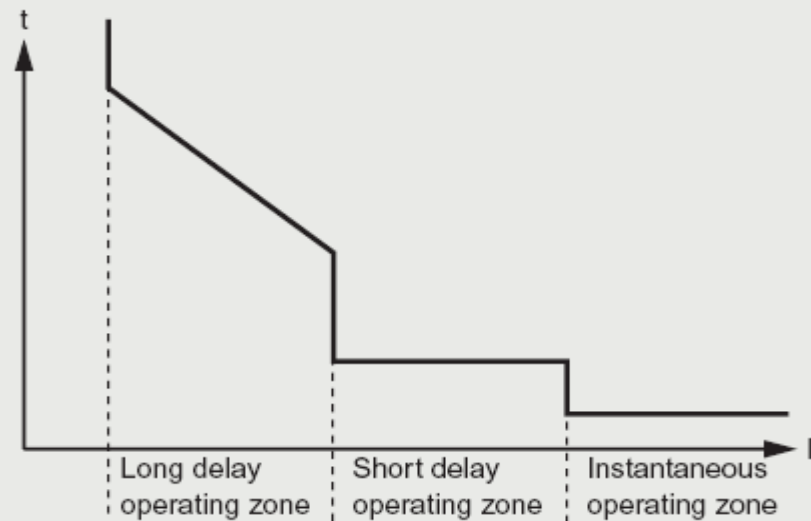

Adjustment

Parameters			Settings
Overload	I _r	$I_r = I_n \times \dots$	0.4 - 0.5 - 0.6 0.7 - 0.75 - 0.8 0.85 - 0.9 0.95 - 1
	T _r	Time delay in s at $6 \times I_r$	0.5 - 1 - 2 - 4 6 - 8 - 12 - 18 24 - 30
	Neutral protection	$I_N = I_r \times \dots$	0 % - 50 % - 100 %
Short-circuit	I _s	$I_s = I_n \times \dots$	0.6 - 1 - 1.5 2 - 3 - 4 - 6 8 - 9 - 10
	T _s	Time delay in ms at $10 \times I_n - I^2 t$ Off Time delay in ms at $10 \times I_n - I^2 t$ On	20 - 100 - 200 300 - 400 20 - 100 - 200 - 300 - 400
Instantaneous	I _p	$I_p = I_r \times \dots$	1.5 - 2 - 3 - 4 5 - 6 - 8 - 10 12 - Max.
Earth fault	I _g	$I_g = I_r \times \dots$	0.2 - 0.3 - 0.4 0.5 - 0.6
	T _g	Time delay in s $I^2 t$ Off Time delay in s - $I^2 t$ On	0.1 - 0.2 - 0.3 0.4 - 1 - Off 0.1 - 0.2 - 0.3 0.4

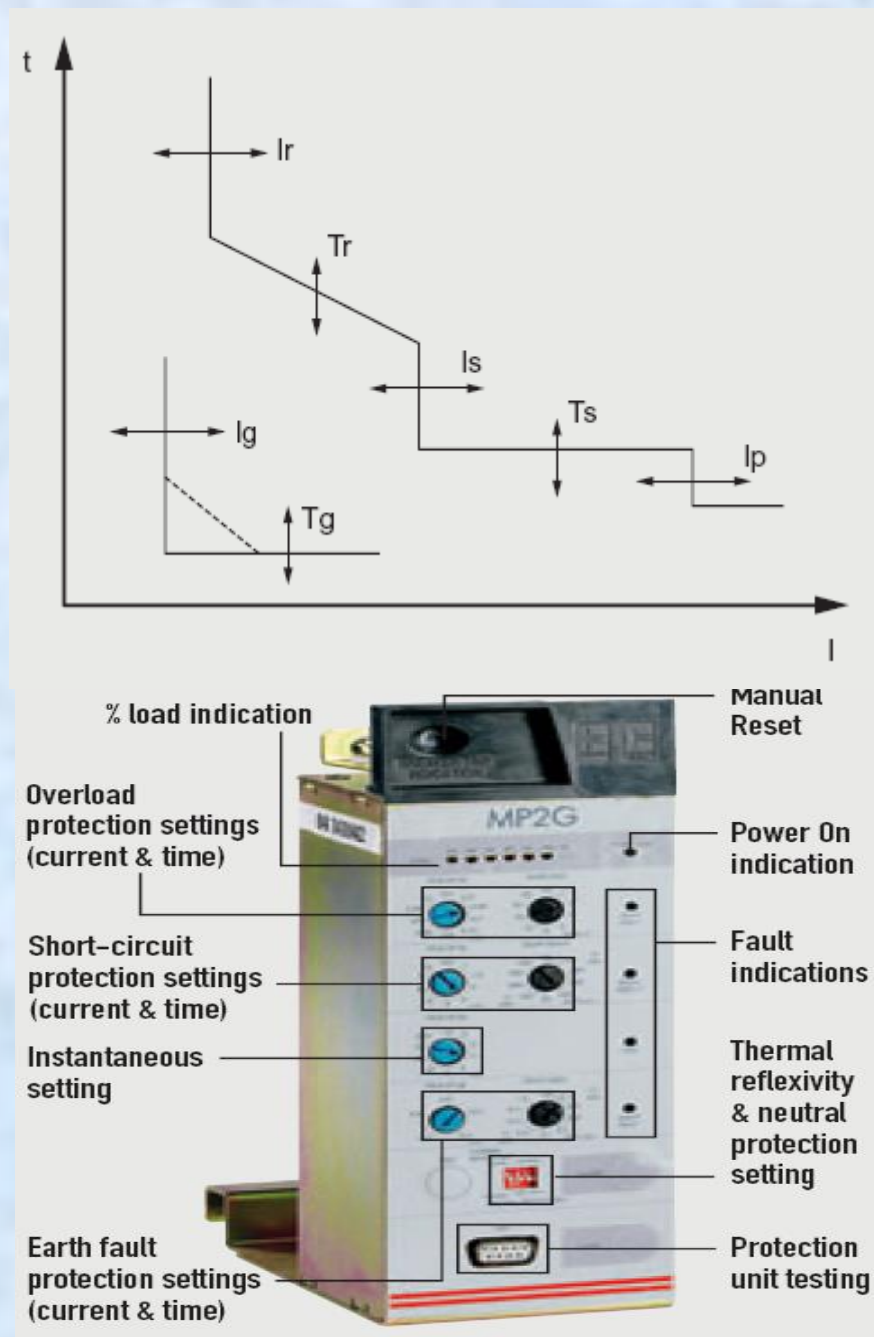

Contactor




Siemens




Telemecanique





ABB

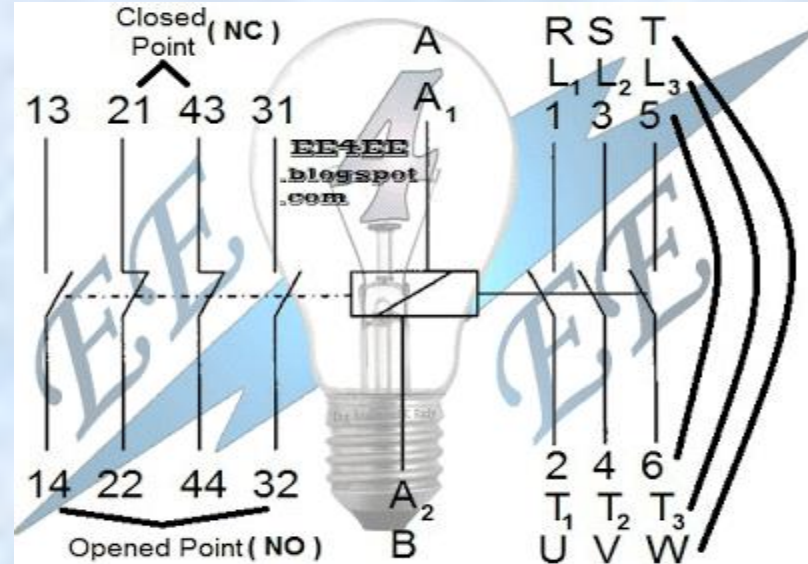



Category		Type of Duty
AC	AC ₁	Non Inductive or slightly inductive loads, resistance furnaces.
	AC ₂	Starting of slip ring motors, Reverse current breaking
	AC ₃	Starting of squirrel cage motors, switching off motors during running.
	AC ₄	Starting of squirrel cage motors, plugging, inching.
DC	DC ₁	Non inductive and slightly inductive loads, resistance furnaces.
	DC ₂	Starting shunt motors, switching off shunt motors during running.
	DC ₃	Starting shunt motors, plugging, inching
	DC ₄	Starting series motors, switching of series motors during running.
	DC ₅	Starting series motors, plugging, inching

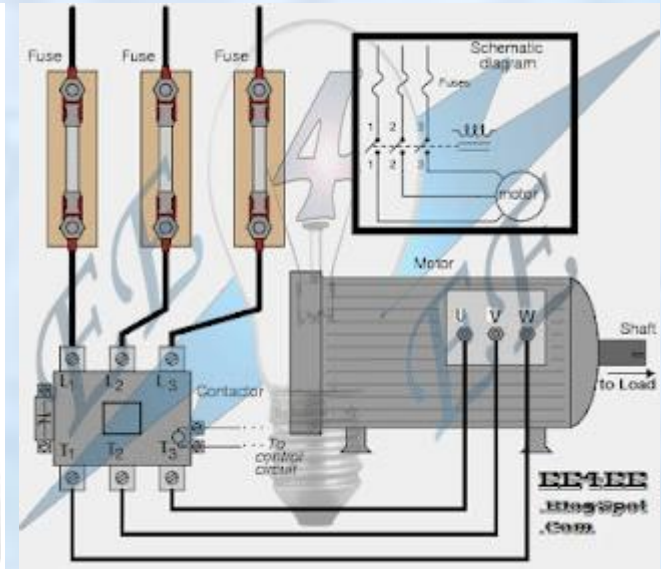


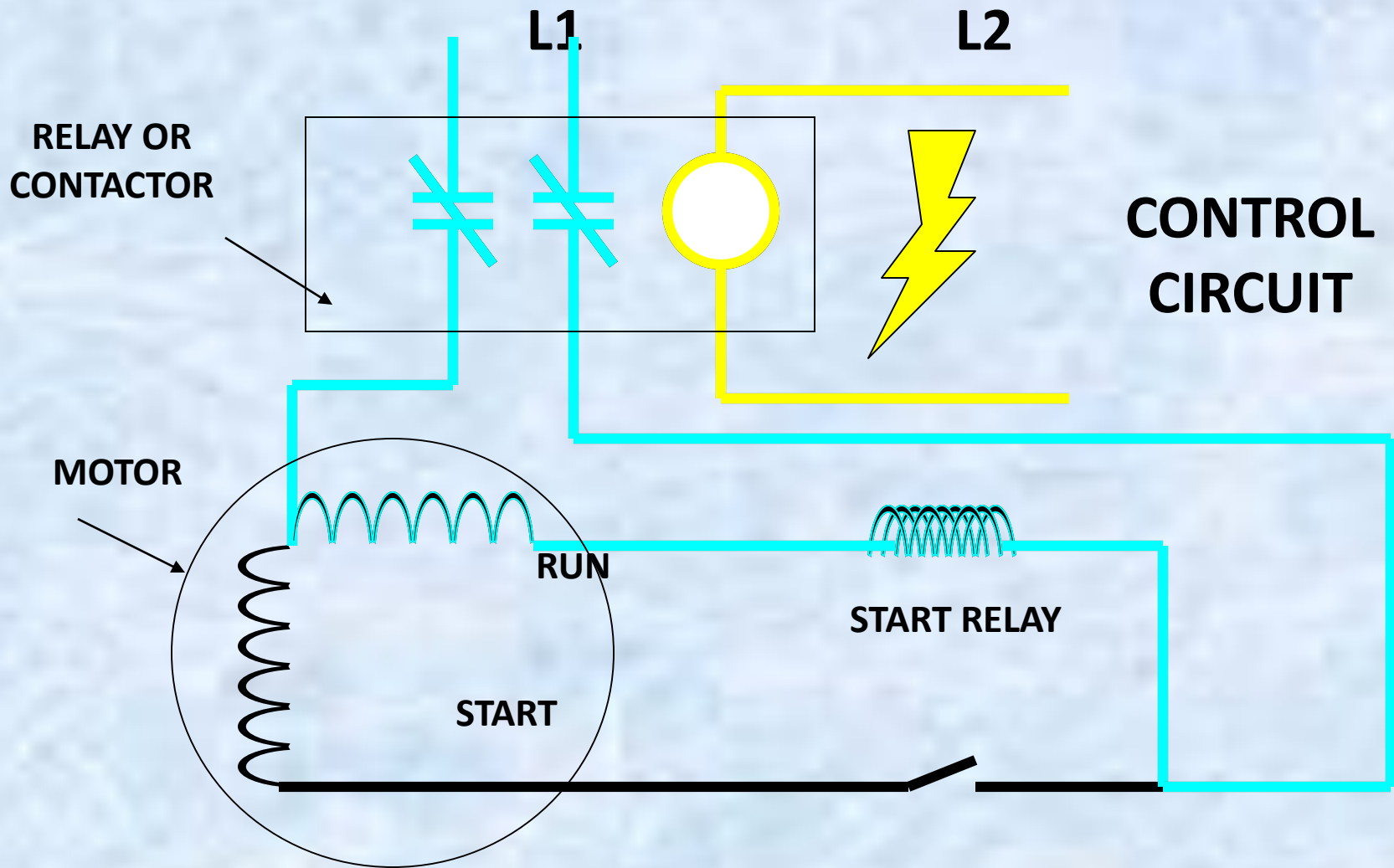

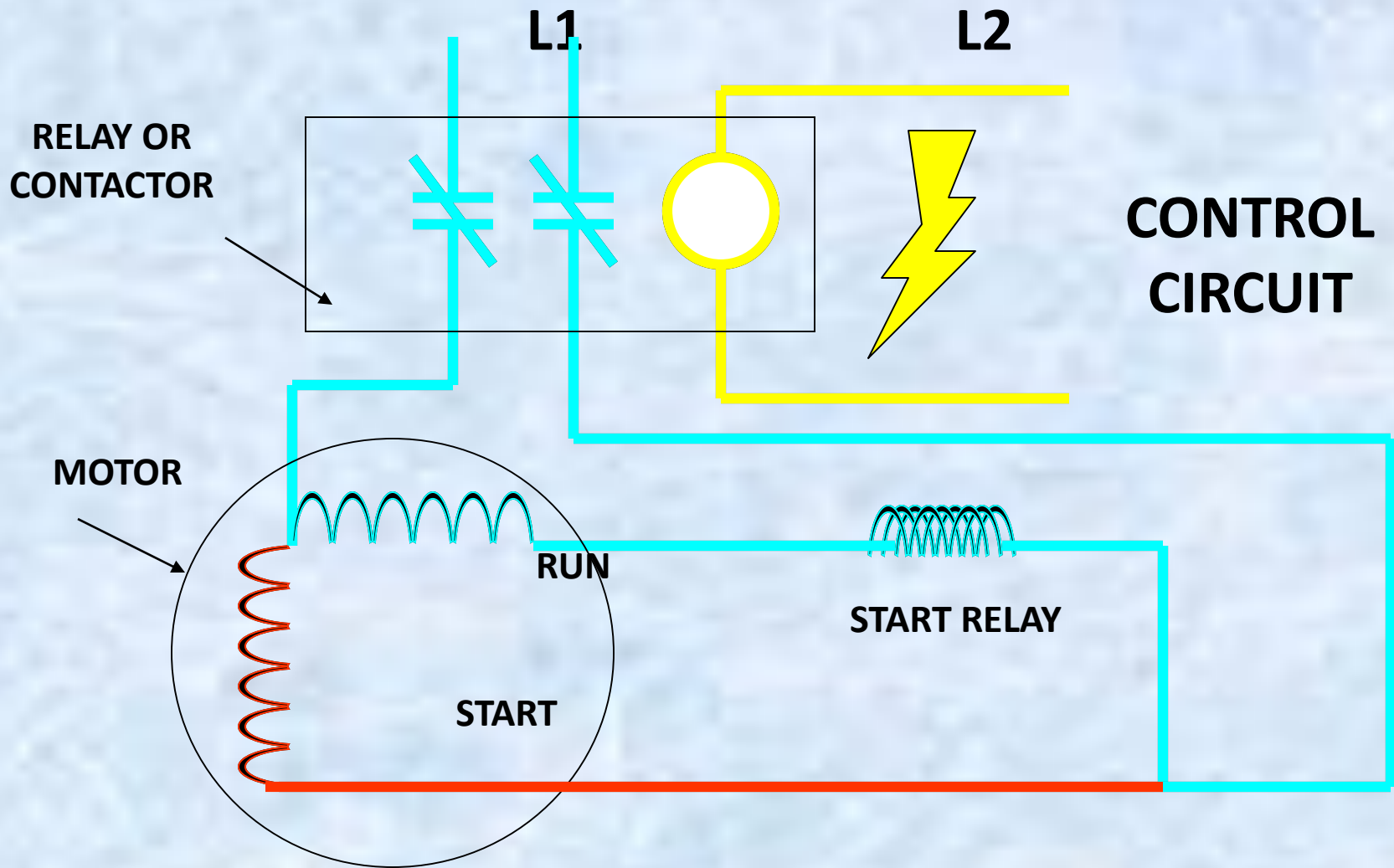


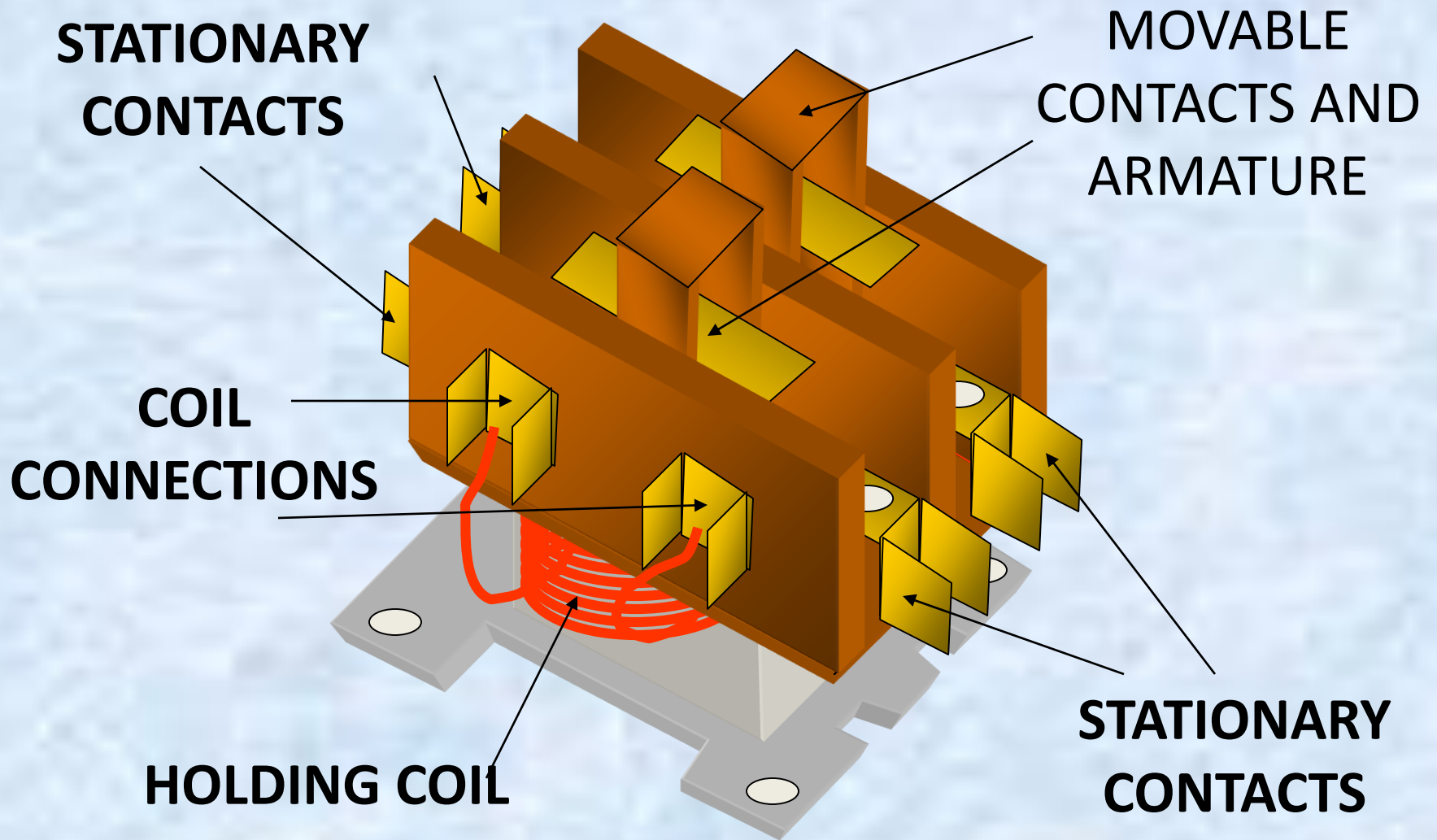

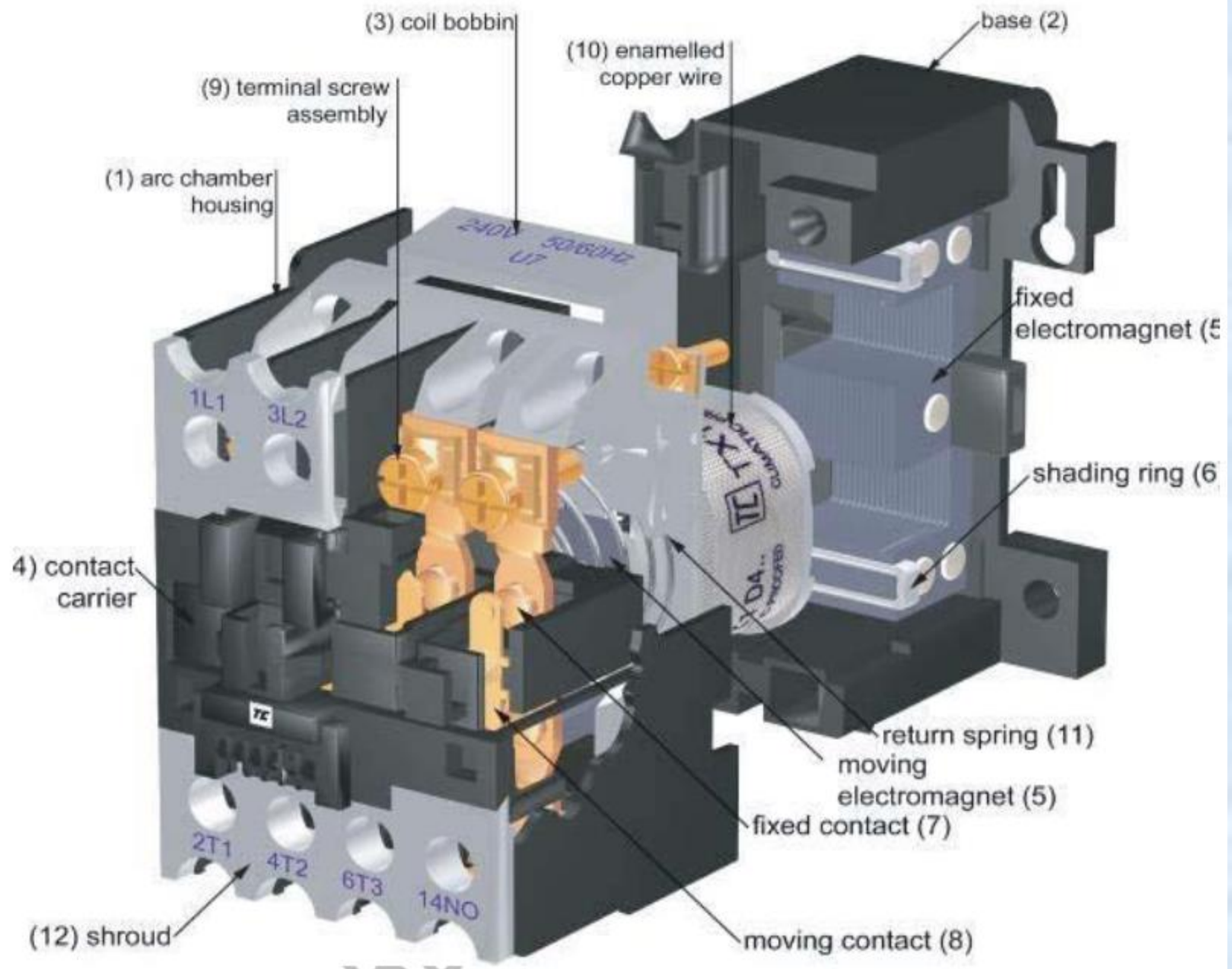


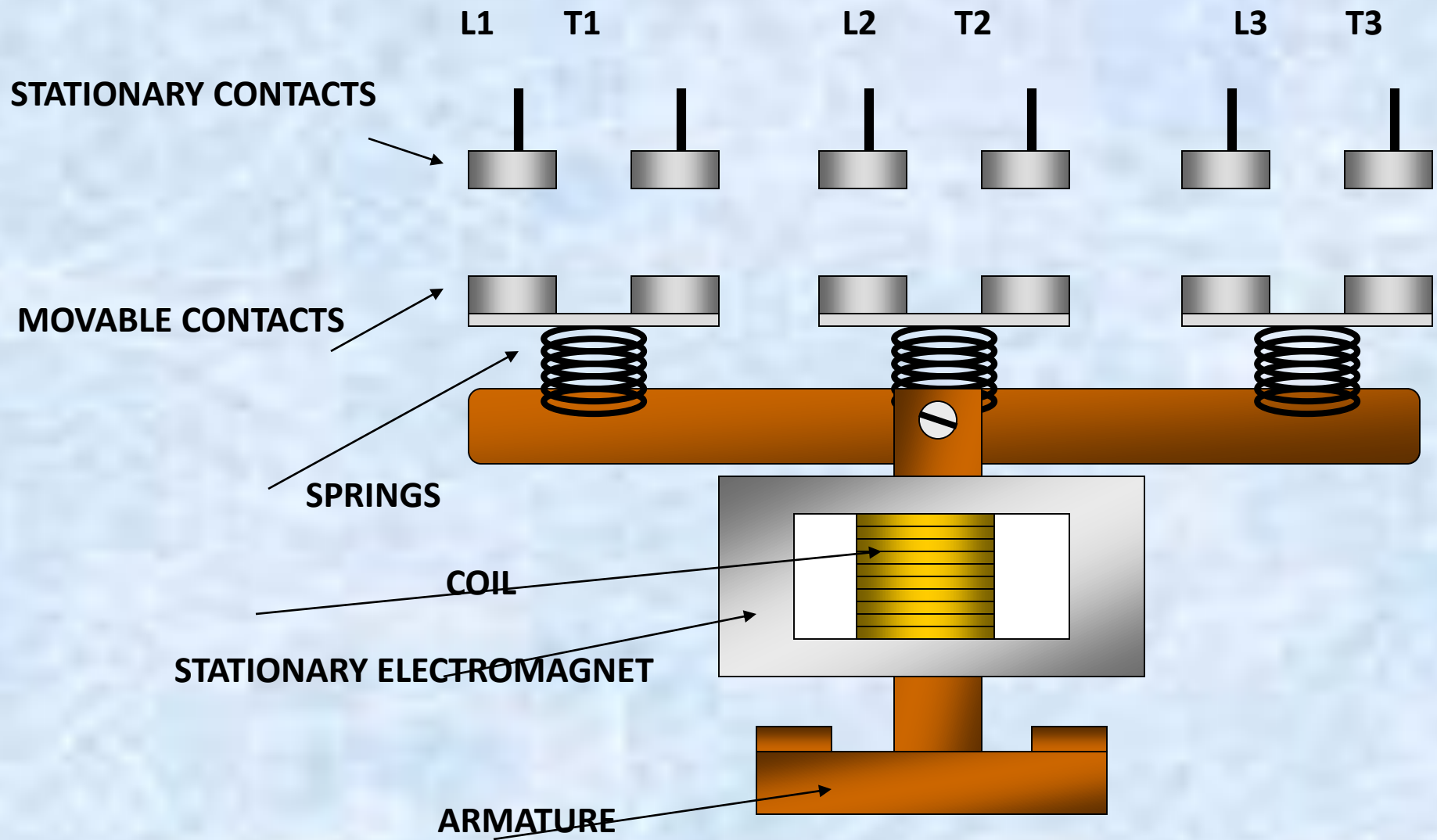

CLEAN CONTACT

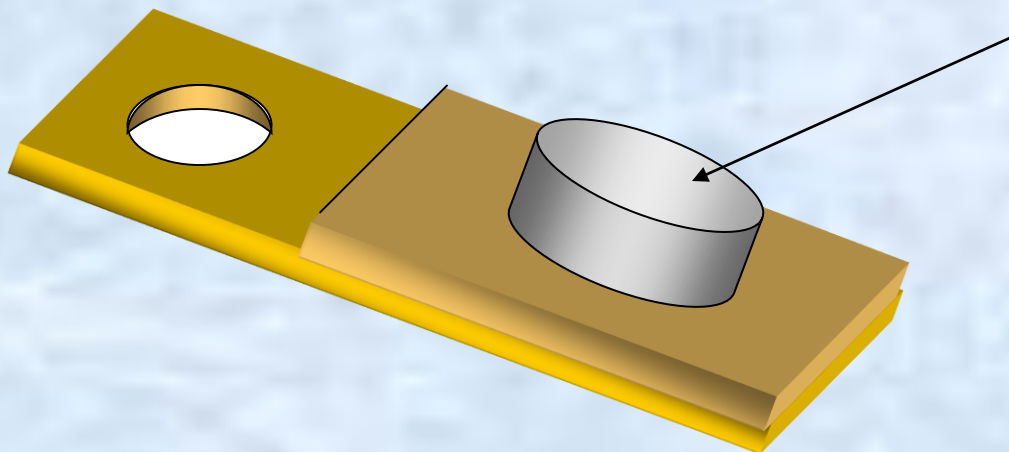


DIRTY, PITTED CONTACT



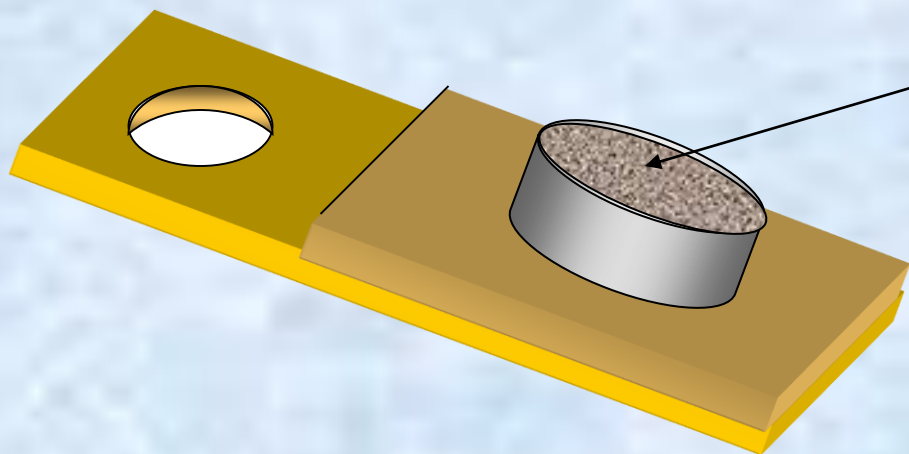


Overload

For low rating

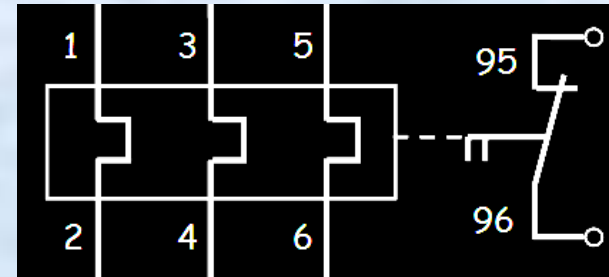


For high rating

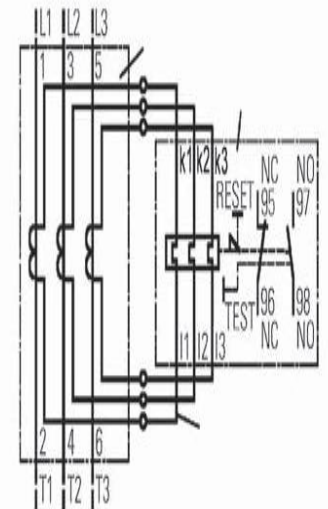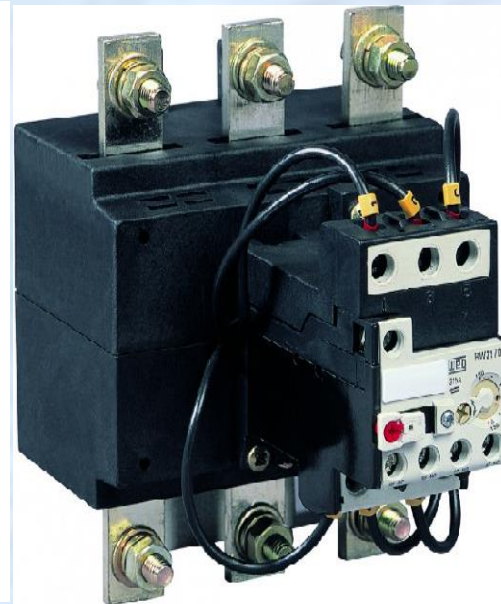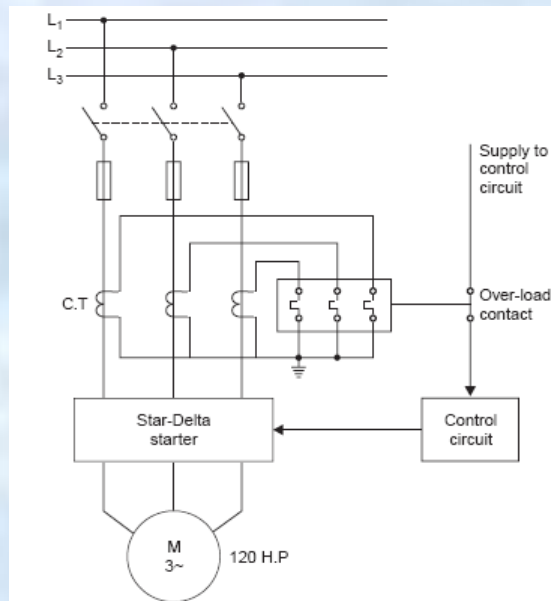

IEC Bimetallic Overload Relay


Rockwell Automation
on the move

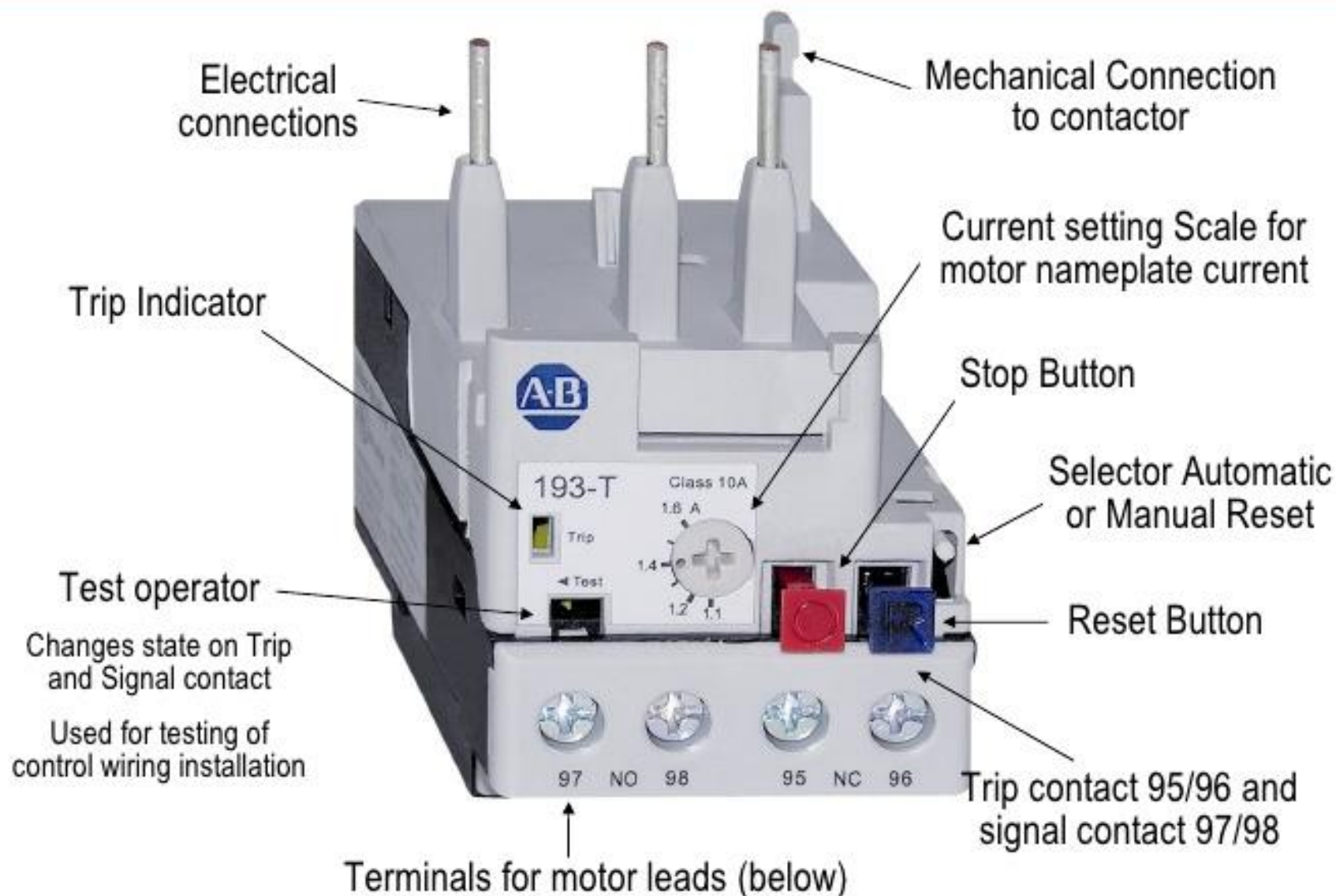


Control circuit components

Start and Stop pushbuttons



Start button is green

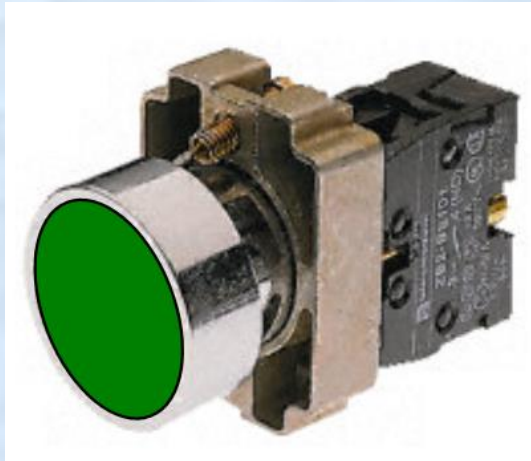

Stop button is red

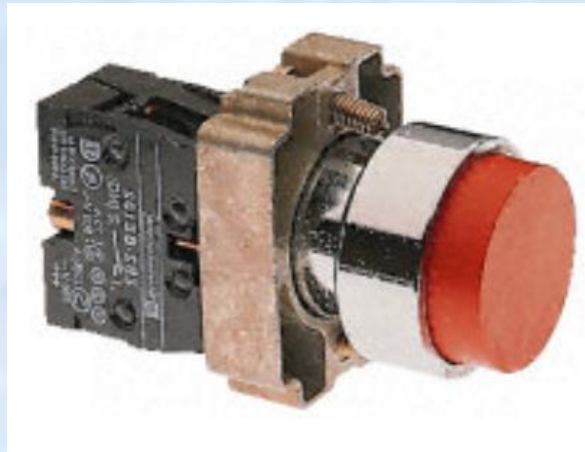

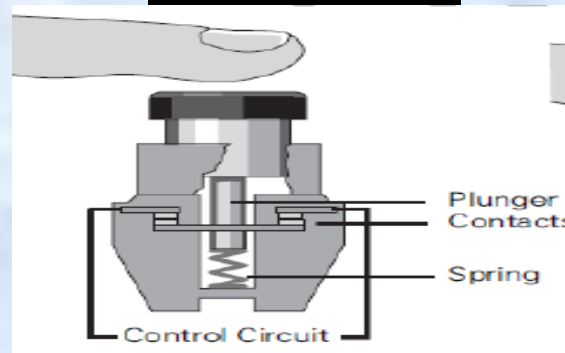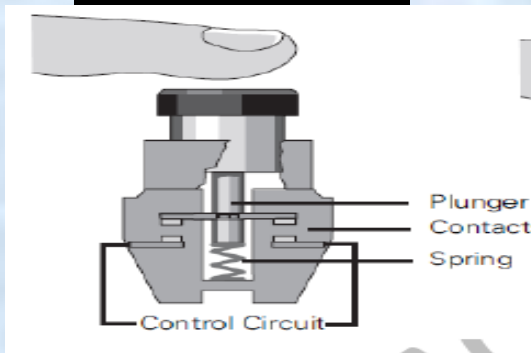Emergency Stop button has a red mushroom head which latches in and must be turned to release



Selector 2 position





Relays

- Input & Output contacts in series and/or parallel
- Combinations of logic elements create complex control plans



RELAYS

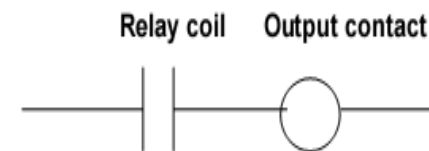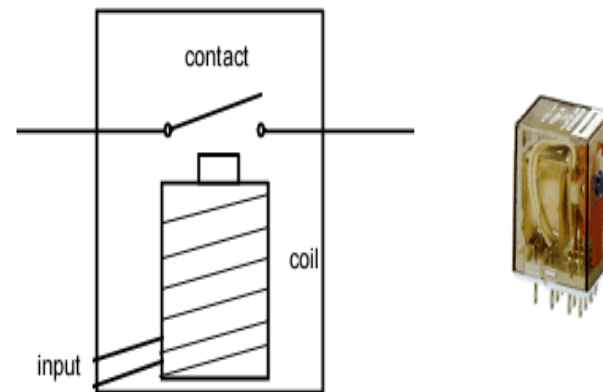A switch whose operation is activated by an electromagnet is called a "relay"




TI-3222: Otomasi Sistem Produksi - 7

Control Relay


relay
not
activated


relay
contacts

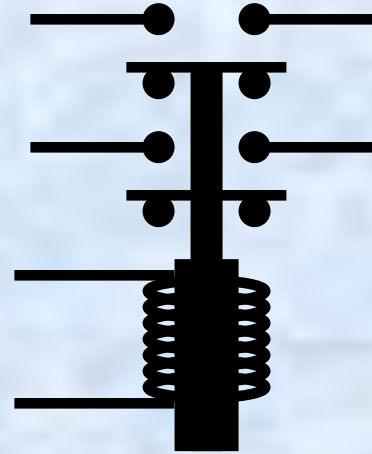


relay
activated

relay
contacts

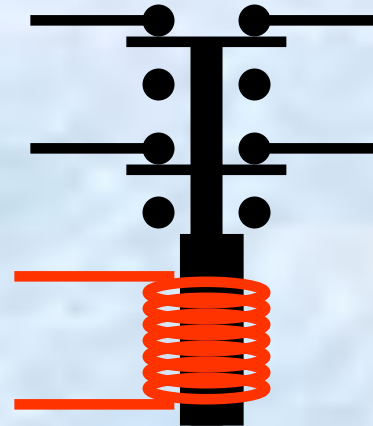


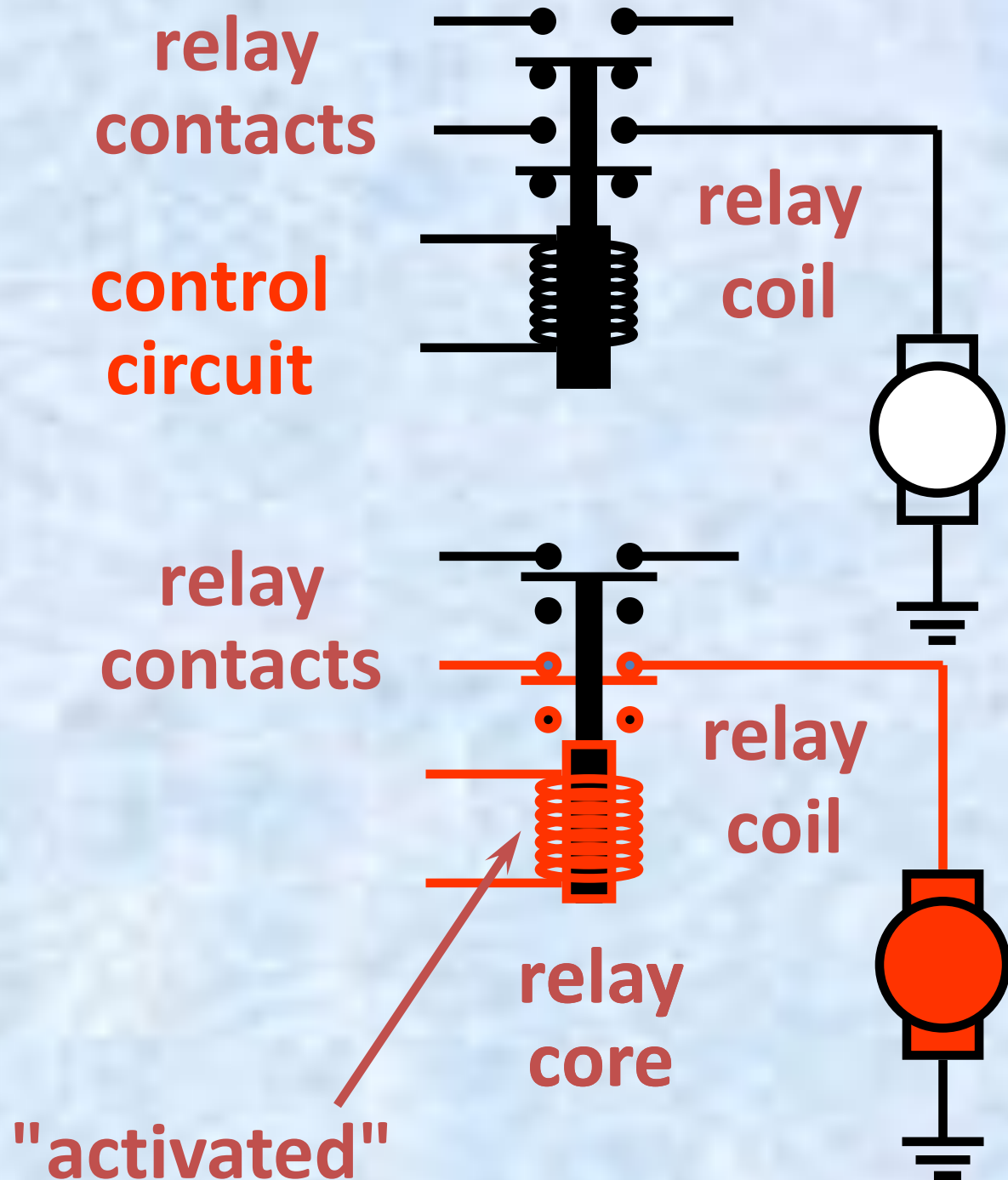


Electronic Timer

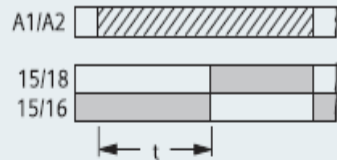


ON-delay

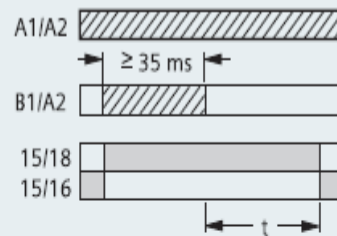


OFF-delay
With auxiliary voltage

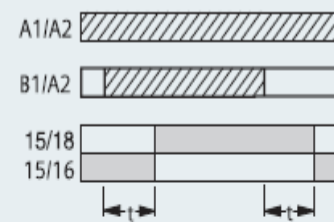

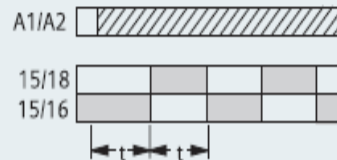
ON + OFF delay
($t = t_{\text{ON}} = t_{\text{OFF}}$)




Flashing (Cyclic)
(Pulse interval 1:1)

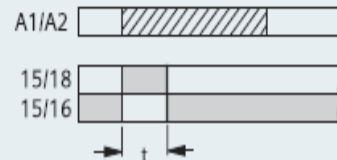


Make Contact

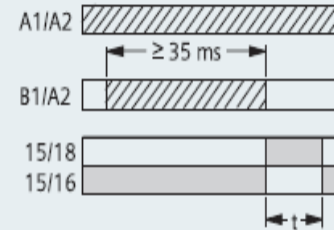


Break contact

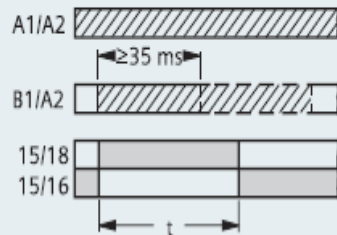


Pulse shaping

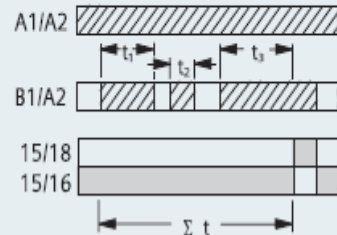

Additive ON-delay

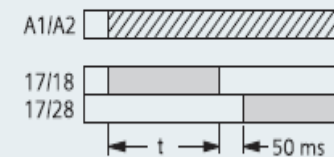

Star delta

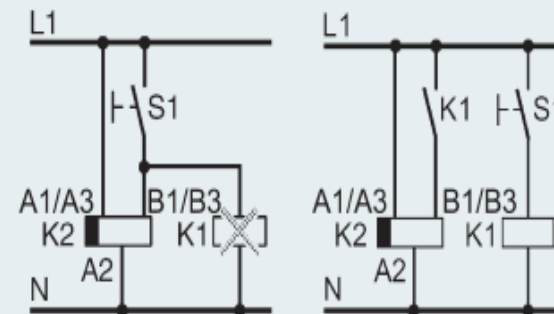

Electronic Timer

Function	Operation	Timing Chart
ON DELAY Delay on Make Delay on Operate	Upon application of input voltage, the time delay (t) begins. At the end of the time delay (t), the output is energized. Input voltage must be removed to reset the time delay relay & de-energize the output.	INPUT VOLTAGE OUTPUT
INTERVAL ON Interval	Upon application of input voltage, the output is energized and the time delay (t) begins. At the end of the time delay (t), the output is de-energized. Input voltage must be removed to reset the time delay relay.	INPUT VOLTAGE OUTPUT
OFF DELAY Delay on Release Delay on Break Delay on De-Energization	Upon application of input voltage, the time delay relay is ready to accept a trigger. When the trigger is applied, the output is energized. Upon removal of the trigger, the time delay (t) begins. At the end of the time delay (t), the output is de-energized. Any application of the trigger during the time delay will reset the time delay (t) and the output remains energized.	INPUT VOLTAGE TRIGGER OUTPUT
SINGLE SHOT One Shot Momentary Interval	Upon application of input voltage, the time delay relay is ready to accept a trigger. When the trigger is applied, the output is energized and the time delay (t) begins. During the time delay (t), the trigger is ignored. At the end of the time delay (t), the output is de-energized and the time delay relay is ready to accept another trigger.	INPUT VOLTAGE TRIGGER OUTPUT
FLASHER (Off First)	Upon application of input voltage, the time delay (t) begins. At the end of the time delay (t), the output is energized and remains in that condition for the time delay (t). At the end of the time delay (t), the output is de-energized and the sequence repeats until input voltage is removed.	INPUT VOLTAGE OUTPUT

Electronic Timer

Function	Operation	Timing Chart
FLASHER (Off First)	Upon application of input voltage, the time delay (t) begins. At the end of the time delay (t), the output is energized and remains in that condition for the time delay (t). At the end of the time delay (t), the output is de-energized and the sequence repeats until input voltage is removed.	INPUT VOLTAGE OUTPUT t t t t <t
FLASHER (On First)	Upon application of input voltage, the output is energized and the time delay (t) begins. At the end of the time delay (t), the output is de-energized and remains in that condition for the time delay (t). At the end of the time delay (t), the output is energized and the sequence repeats until input voltage is removed.	INPUT VOLTAGE OUTPUT t t t t <t
ON/OFF DELAY	Upon application of input voltage, the time delay relay is ready to accept a trigger. When the trigger is applied, the time delay (t1) begins. At the end of the time delay (t1), the output is energized. When the trigger is removed, the output contacts remain energized for the time delay (t2). At the end of the time delay (t2), the output is de-energized & the time delay relay is ready to accept another trigger. If the trigger is removed during time delay period (t1), the output will remain de-energized and time delay (t1) will reset. If the trigger is re-applied during time delay period (t2), the output will remain energized and the time delay (t2) will reset.	INPUT VOLTAGE TRIGGER OUTPUT t1 t2 * For TD-7 catalog numbers, t1 & t2 are the same length of time.
SINGLE SHOT FALLING EDGE	Upon application of input voltage, the time delay relay is ready to accept a trigger. When the trigger is applied, the output remains de-energized. Upon removal of the trigger, the output is energized and the time delay (t) begins. At the end of the time delay (t), the output is de-energized unless the trigger is removed and re-applied prior to time out (before time delay (t) elapses). Continuous cycling of the trigger at a rate faster than the time delay (t) will cause the output to remain energized indefinitely.	INPUT VOLTAGE TRIGGER OUTPUT t <t t

Electronic Timer

Function	Operation	Timing Chart
WATCHDOG Retriggerable Single Shot	Upon application of input voltage, the time delay relay is ready to accept a trigger. When the trigger is applied, the output is energized and the time delay (t) begins. At the end of the time delay (t), the output is de-energized unless the trigger is removed and re-applied prior to time out (before time delay (t) elapses). Continuous cycling of the trigger at a rate faster than the time delay (t) will cause the output to remain energized indefinitely.	
TRIGGERED ON DELAY	Upon application of input voltage, the time delay relay is ready to accept a trigger. When the trigger is applied, the time delay (t) begins. At the end of the time delay (t), the output is energized and remains in that condition as long as either the trigger is applied or the input voltage remains. If the trigger is removed during the time delay (t), the output remains de-energized & the time delay (t) is reset.	
REPEAT CYCLE (OFF 1st)	Upon application of input voltage, the time delay (t_1) begins. At the end of the time delay (t_1), the output is energized and remains in that condition for the time delay (t_2). At the end of this time delay, the output is de-energized and the sequence repeats until input voltage is removed.	
REPEAT CYCLE (ON 1st)	Upon application of input voltage, the output is energized and the time delay (t_1) begins. At the end of the time delay (t_1), the output is de-energized and remains in that condition for the time delay (t_2). At the end of this time delay, the output is energized and the sequence repeats until input voltage is removed.	
DELAYED INTERVAL Single Cycle	Upon application of input voltage, the time delay (t_1) begins. At the end of the time delay (t_1), the output is energized and remains in that condition for the time delay (t_2). At the end of this time delay (t_2), the output is de-energized. Input voltage must be removed to reset the time delay relay.	

Electronic Timer

Function	Operation	Timing Chart
TRIGGERED DELAYED INTERVAL Single Cycle	Upon application of input voltage, the time delay relay is ready to accept a trigger. When the trigger is applied, the time delay (t_1) begins. At the end of the time delay (t_1), the output is energized and remains in that condition for the time delay (t_2). At the end of the time delay (t_2), the output is de-energized & the relay is ready to accept another trigger. During both time delay (t_1) & time delay (t_2), the trigger is ignored.	INPUT VOLTAGE TRIGGER OUTPUT t_1 t_2 t_1 t_2
TRUE OFF DELAY	Upon application of input voltage, the output is energized. When the input voltage is removed, the time delay (t) begins. At the end of the time delay (t), the output is de-energized. Input voltage must be applied for a minimum of 0.5 seconds to assure proper operation. Any application of the input voltage during the time delay (t) will reset the time delay. No external trigger is required.	INPUT VOLTAGE OUTPUT t t
ON DELAY/ TRUE OFF DELAY	Upon application of input voltage, the time delay (t_1) begins. At the end of the time delay (t_1), the output is energized. When the input voltage is removed, the output remains energized for the time delay (t_2). At the end of the time delay (t_2), the output is de-energized. Input voltage must be applied for a minimum of 0.5 seconds to assure proper operation. Any application of the input voltage during the time delay (t_2) will keep the output energized & reset the time delay (t_2). No external trigger is required.	INPUT VOLTAGE OUTPUT t_1 t_2 t_1 t_2
SINGLE SHOT- FLASHER	Upon application of input voltage, the time delay relay is ready to accept a trigger. When the trigger is applied, the time delay (t_1) begins and the output is energized for the time delay (t_2). At the end of this time delay (t_2), the output is de-energized and remains in that condition for the time delay (t_2). At the end of the time delay (t_2), the output is energized and the sequence repeats until time delay (t_1) is completed. During the time delay (t_1), the trigger is ignored.	INPUT VOLTAGE TRIGGER OUTPUT t_1 t_2 t_2 t_2 t_2 $<t_2$


Electronic Timer

Function	Operation	Timing Chart
ON DELAY- FLASHER	Upon application of input voltage, the time delay begins (t_1). At the end of the time delay (t_1), the output is energized and remains in that condition for the time delay (t_2). At the end of this time delay (t_2), the output is de-energized and remains in that condition for the time delay (t_2). At the end of the time delay (t_2), the output is energized and the sequence repeats until input voltage is removed.	Timing chart for ON DELAY-FLASHER. The INPUT VOLTAGE is a continuous high pulse. The OUTPUT shows a sequence of pulses: a pulse of duration t_1, followed by a pulse of duration t_2, then a gap of duration t_2, then another pulse of duration t_2, and finally a pulse of duration $<t_2$.
PERCENTAGE	Upon initial application of input voltage, the output is energized and time delay (t_1) begins. Time Delay (t_1) is adjustable as a percentage of the overall cycle time (t_2). At the end of time delay (t_1), the output is de-energized for the remainder of overall cycle (t_2-t_1). The sequence then repeats until input voltage is removed. If input voltage is removed and reapplied, the timing cycle will continue from where it left off when the input voltage was removed. A setting of 100% energizes the output continuously while a setting of 0% de-energizes the output continuously.	Timing chart for PERCENTAGE mode. The INPUT VOLTAGE is a pulse. The OUTPUT shows a cycle where the output is ON for t_1 and OFF for (t_2-t_1). The second cycle starts with a shorter ON time, labeled $<(t_2-t_1)$, indicating it continues from the previous cycle.
PERCENTAGE (NO MEMORY)	Upon initial application of input voltage, the output is energized and time delay (t_1) begins. Time Delay (t_1) is adjustable as a percentage of the overall cycle time (t_2). At the end of time delay (t_1), the output is de-energized for the remainder of overall cycle (t_2-t_1). The sequence then repeats until input voltage is removed. If input voltage is removed and reapplied, the timing cycle will be reset. A setting of 100% energizes the output continuously while a setting of 0% de-energizes the output continuously.	Timing chart for PERCENTAGE (NO MEMORY) mode. The INPUT VOLTAGE is a pulse. The OUTPUT shows a cycle where the output is ON for t_1 and OFF for (t_2-t_1). The second cycle starts with a shorter ON time, labeled $<TIME RANGE t_2$, indicating it is reset.

Transducers

- A device which converts 1 form of energy into another.
- In a process industry 4 basic and very important parameters to be measured and controlled are:

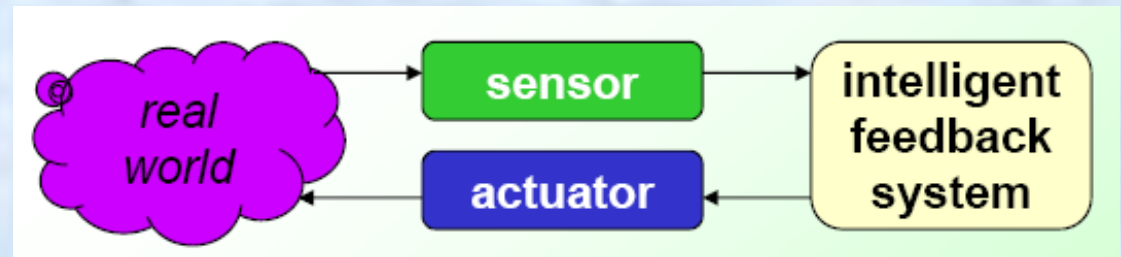- 1) Flow
- 2) Temperature
- 3) Pressure
- 4) Level



Sensor (e.g., thermometer)

- Device that detects/measures a signal
- Acquires information from the “real world”

Actuator (e.g., heater)

- Device that generates a signal or stimulus

CHAPTER 4

Motor Name Plate

ABB		IE2					CE	
3~Motor		M3BP 90SLB 4 IMB3/IM1001					734278-2	
3GBP092322-ASB441					No.3GF12141567		Cl. F	IP 55
V	Hz	r/min	kW	A	cos φ	Duty		
400 Y	50	1435	1.1	2.3	0.80	S1		
230 D	50	1435	1.1	3.9	0.80	S1		
460 Y	60	1740	1.1	2.0	0.77	S1		
IE2-50Hz-83.6%(100%)-84.5%(75%) / IE2-60Hz-85.4%(100%)								
6205-2Z/C3  6204-2Z/C3							2013	25 kg
							IEC 60034-1	

Motor sizes 71 to 90

ABB		IE2					
3~ Motor M3BP 112MB 2 IMB3/IM1001				2013		Cl. F IP 55	
3GBP111322-ADB							
738524-1		No. 3GF12143206					
V	Hz	r/min	kW	A	cos φ	Duty	
690 Y	50	2895	4	4.4	0.86	S1	
400 D	50	2895	4	7.7	0.86	S1	
460 D	60	2900	4	7.6	0.85	S1	
IE2-86.1%(100%)-87.0%(75%)-86.6%(50%)							
6206-2Z/C3 							
6205-2Z/C3						37 kg	
						IEC60034-1	

Motor sizes 100 to 132

ABB				CE			
3~ Motor M3BP 180 MLB4				Cl.F	IP 55	IEC 60034-1	
V	Hz	kW	r/min	A	cos φ	duty	
400 Δ	50	22	1475	40,9	0,84	S1	
690 Y	50	22	1475	23,7	0,84	S1	
415 Δ	50	22	1477	39,8	0,83	S1	
460 Y	60	22	1780	35,7	0,83	S1	
3GBP 182 032-ADG				No.			
50 Hz: IE2-92,4(100%)-93,3(75%)-93,0(50%)						2013	
60 Hz: IE2-93,1(100%)-93,4(75%)-92,6(50%)							
6310/C3				6209/C3		222 kg	
spare-parts: www.abb.com/portsonline							

Motor sizes 160 to 180

M3BP 160MLC 3GBP 161 033 - ADG

003, etc.

1 2 3 4 5 6 7 8 9 10 11 12 13 14

Positions 1 to 4

3GBP: Totally enclosed fan cooled squirrel cage motor with cast iron frame

Positions 5 and 6**IEO size**

71: 71

80: 80

90: 90

10: 100

12: 112

13: 132

16: 160

18: 180

20: 200

22: 225

25: 250

28: 280

31: 315

35: 355

40: 400

45: 450

Position 7**Speed (Pole pairs)**

1: 2 poles

2: 4 poles

3: 6 poles

4: 8 poles

5: 10 poles

6: 12 poles

7: > 12 poles

8: Two-speed motors for fan drive motors for constant torque

9: Multi-speed motors, two-speed

Positions 8 to 10

Serial number

Position 11

- (dash)

Position 12**Mounting arrangement**

A: Foot-mounted, top-mounted terminal box

R: Foot-mounted, terminal box RHS seen from D-end

L: Foot-mounted, terminal box LHS seen from D-end

B: Flange-mounted, large flange

O: Flange-mounted, small flange (sizes 71 to 112)

H: Foot- and flange-mounted, terminal box top-mounted

J: Foot- and flange-mounted, small flange with tapped holes

S: Foot- and flange-mounted, terminal box RHS seen from D-end

T: Foot- and flange-mounted, terminal box LHS seen from D-end

V: Flange-mounted, special flange

F: Foot- and flange-mounted. Special flange

Position 13**Voltage and frequency****Single-speed motors**

B: 380 VΔ 50 Hz

D: 400 VΔ, 415 VΔ, 690 VY 50 Hz

E: 500 VΔ 50 Hz

F: 500 VY 50 Hz

G: 230 VΔ, 400 VY, 415 VY 50 Hz

T: 680 VΔ 50 Hz

U: 690 VΔ 50 Hz

X: Other rated voltage, connection or frequency, 690 V maximum

Two-speed motors

A: 220 V 50 Hz

B: 380 V 50 Hz

D: 400 V 50 Hz

E: 500 V 50 Hz

G: 230 V 50 Hz

X: Other rated voltage, connection or frequency, 690 V maximum

Remark: For voltage code X the variant code "209 Non-standard voltage or frequency (special winding)" must be ordered.

Position 14**Generation code**

A, B, O...G...K: The product code must be, if needed, followed by variant codes.

- Manufacturer type
- Rated horsepower
- Rated voltage and amps
- Rated full-load amps
- Rated full-load speed
- Frequency
- Service Factor
- Frame Size
- Insulation class
- Efficiency



➤ Manufacturer type

CE IE2						
3 ~ Motor M3BP 315SMC 4 IMB3 / IM1001						
1060392-1				2013		No. 3GP12061919
				Ins.cl. F		IP 55
V	Hz	kW	r/min	A	cos φ	Duty
690 Y	50	160	1487	165	0.85	S1
400 D	50	160	1487	284	0.85	S1
415 D	50	160	1488	277	0.84	S1
IE2-95.6%(100%)-95.6%(75%)-95.1%(50%)						
Prod. code 3GBP312230-ADG						
					Nmax	2300 r/min
6319/C3  6316/C3					1000 kg	
ABB IEC 60034-1						

➤ Rated horsepower

CAT. NO.	EM3615T											
SPEC.	36G271S268G1											
HP	5											
VOLTS	208-230/460											
AMPS	13.9-13.4/6.7											
R.P.M.	1750											
FRAME	184T				HZ		60			PH	3	
SER. F.	1.15		CODE		J		DES		B		CLASS	F
NEMA NOM. EFF.			89.5		%		P.F.		78		%	
RATING	40C AMB-CONT											
CC	010A				USABLE AT 208V				13.9		A	
BEARINGS	DE		6206						ODE		6205	
ENCL.	TEFC		SN									

➤ Rated voltage

CAT. NO.	EM3615T									
SPEC.	36G271S268G1									
HP	5									
VOLTS	208-230/460									
AMPS	13.9-13.4/6.7									
R.P.M.	1750									
FRAME	184T		HZ	60			PH	3		
SER. F.	1.15		CODE	J		DES	B	CLASS	F	
NEMA NOM. EFF.		89.5		%		P.F.	78		%	
RATING	40C AMB-CONT									
CC	O10A		USABLE AT 208V					13.9	A	
BEARINGS	DE	6206				ODE	6205			
ENCL.	TEFC	SN								

➤ Rated full load current

CAT. NO.	EM3615T									
SPEC.	36G271S268G1									
HP	5									
VOLTS	208-230/460									
AMPS	13.9-13.4/6.7									
R.P.M.	1750									
FRAME	184T		HZ	60			PH	3		
SER. F.	1.15		CODE	J		DES	B	CLASS	F	
NEMA NOM. EFF.		89.5		%		P.F.	78		%	
RATING	40C AMB-CONT									
CC	O10A		USABLE AT 208V					13.9	A	
BEARINGS	DE	6206				ODE	6205			
ENCL.	TEFC	SN								

➤ Frequency

CAT. NO.	EM3615T										
SPEC.	36G271S268G1										
HP	5										
VOLTS	208-230/460										
AMPS	13.9-13.4/6.7										
R.P.M.	1750										
FRAME	184T			HZ		60			PH 3		
SER. F.	1.15		CODE		J	DES		B	CLASS F		
NEMA NOM. EFF.			89.5		%		P.F.		78 %		
RATING	40C AMB-CONT										
CC	010A			USABLE AT 208V				13.9 A			
BEARINGS	DE	6206					ODE	6205			
ENCL.	TEFC		SN								

CAT. NO.	EM3615T											
SPEC.	36G271S268G1											
HP	5											
VOLTS	208-230/460											
AMPS	13.9-13.4/6.7											
R.P.M.	1750											
FRAME	184T				HZ		60				PH	3
SER. F.	1.15		CODE	J	DES		B	CLASS		F		
NEMA NOM. EFF.	89.5		%		P.F.		78		%			
RATING	40C AMB-CONT											
CC	010A			USABLE AT 208V				13.9		A		
BEARINGS	DE	6206					ODE	6205				
ENCL.	TEFC		SN									

CAT. NO.	EM3615T										
SPEC.	36G271S268G1										
HP	5										
VOLTS	208-230/460										
AMPS	13.9-13.4/6.7										
R.P.M.	1750										
FRAME	184T			HZ		60			PH		3
SER. F.	1.15		CODE		J	DES		B	CLASS		F
NEMA NOM. EFF.	89.5		%		P.F.		78 %				
RATING	40C AMB-CONT										
CC	010A			USABLE AT 208V				13.9 A			
BEARINGS	DE		6206					ODE		6205	
ENCL.	TEFC		SN								



CAT. NO.	EM3615T													
SPEC.	36G271S268G1													
HP	5													
VOLTS	208-230/460													
AMPS	13.9-13.4/6.7													
R.P.M.	1750													
FRAME	184T				HZ		60				PH		3	
SER. F.	1.15		CODE		J		DES		B		CLASS		F	
NEMA NOM. EFF.			89.5		%		P.F.		78				%	
RATING	40C AMB-CONT													
CC	010A				USABLE AT 208V				13.9				A	
BEARINGS	DE		6206						ODE		6205			
ENCL.	TEFC		SN											

➤ Roll Bearing

DE – Drive End
(output shaft end)




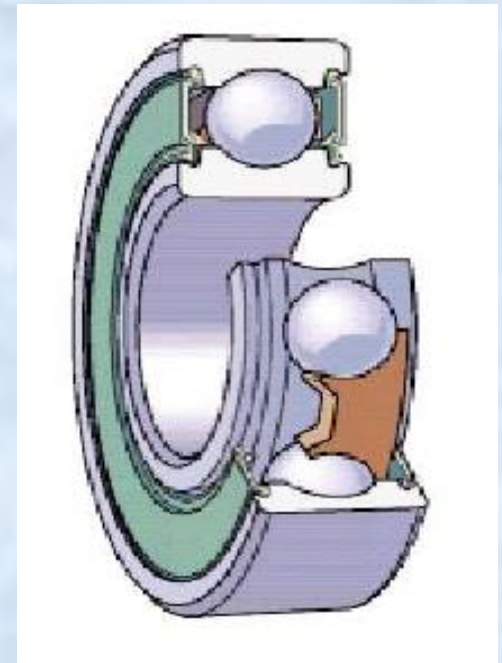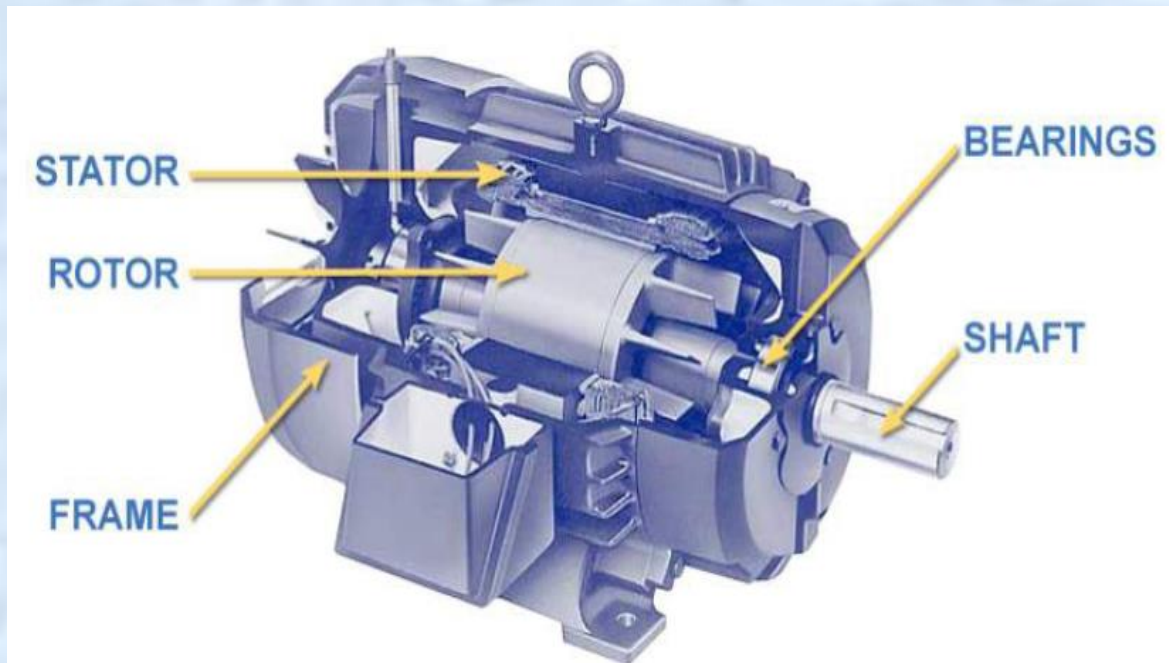ODE = Opposite Drive End
(fan end or rear of motor)



Note : Last 2 number * 5 except 00,01,02,03 (6205 inner diameter 25 mm)

Typical motor failure

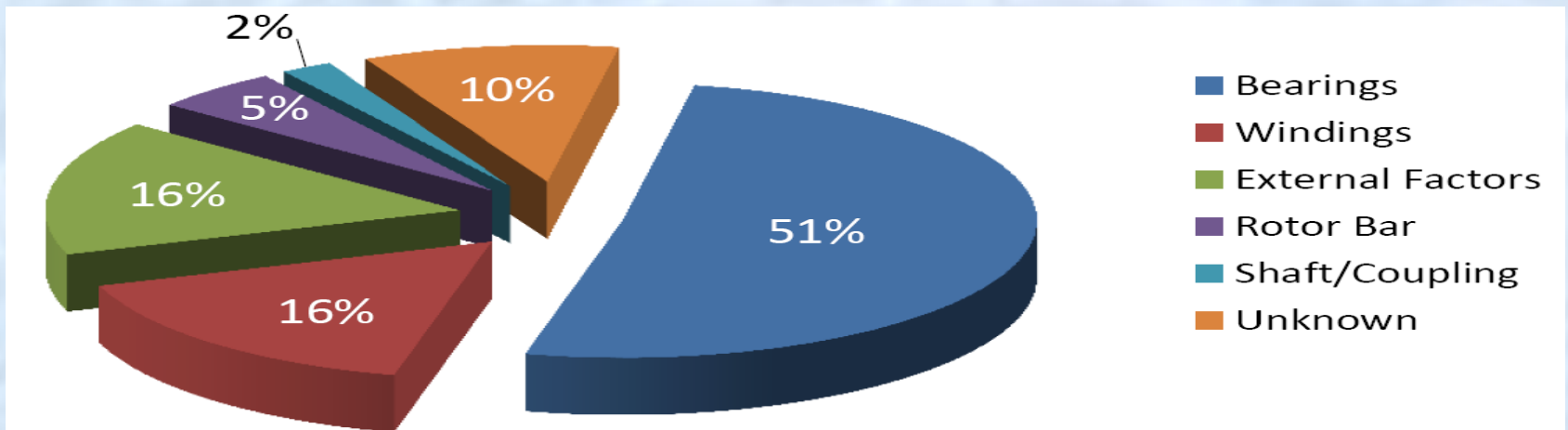


Component	% Failures	Potential Cause
Bearings	51%	Lubrication, mechanical, shaft currents, contamination
Windings	16%	Overvoltage, water, overload, undervoltage, environment
External Factors	16%	Environmental or load related
Rotor Bar	5%	Overload, locked rotor, vibration
Shaft/Coupling	2%	Mechanical, overload
Unknown	10%	No root cause determined

CHAPTER 5

Types of AC

Motors


Classification of Motors

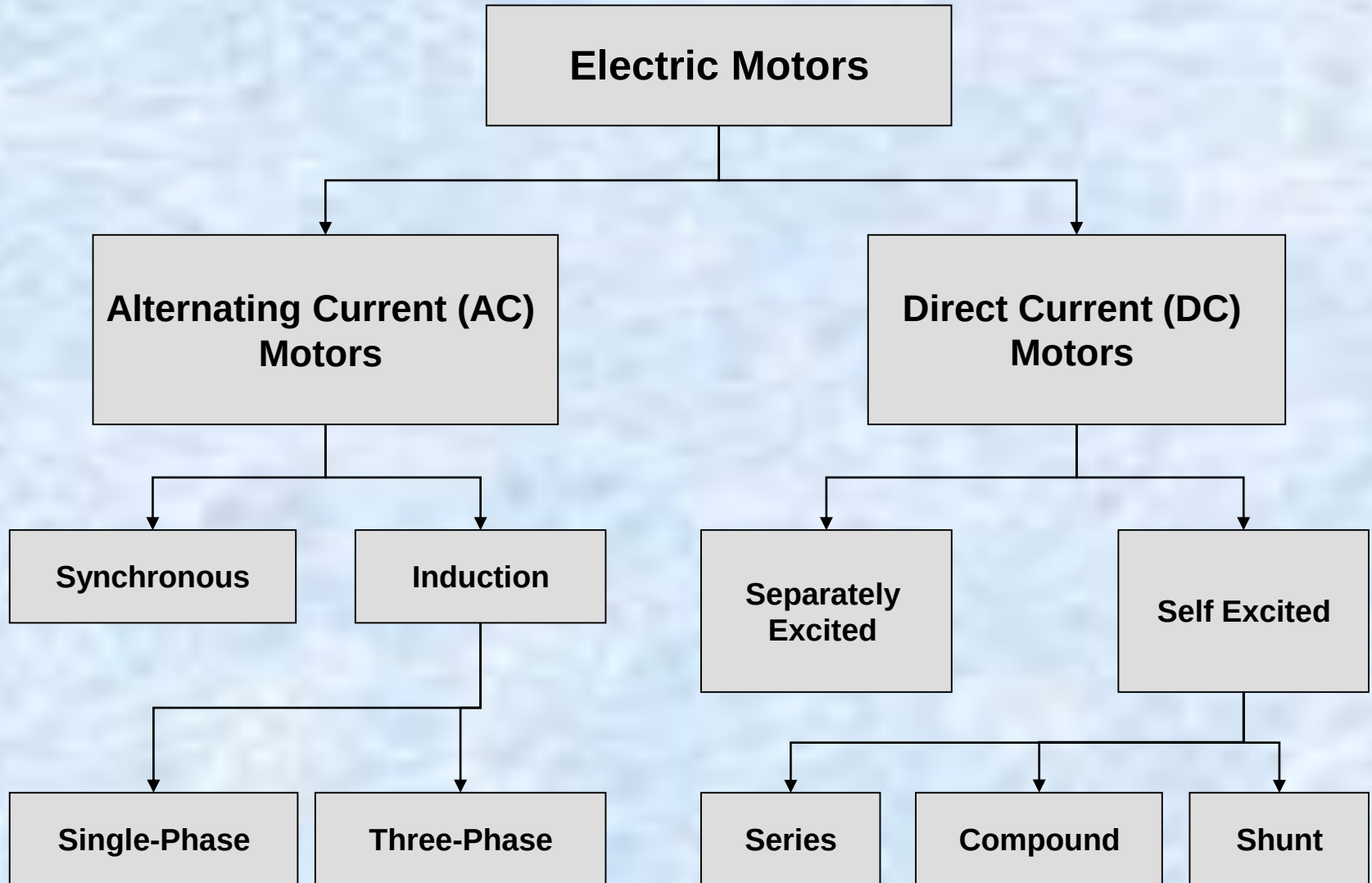

DC Generators

Separately Excited




Self-Excited

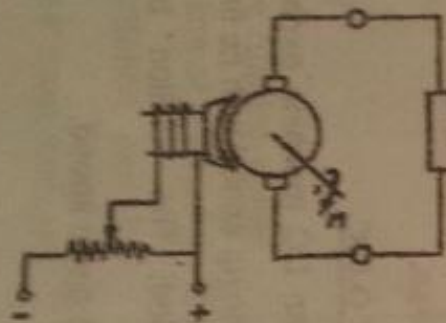


Shunt Type

Series Type

Compounded Type

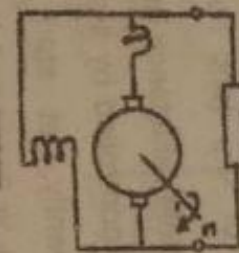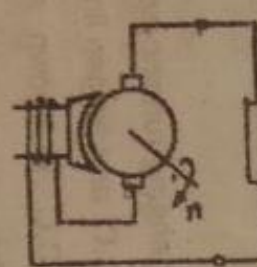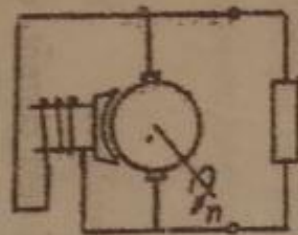

Long-Shunt

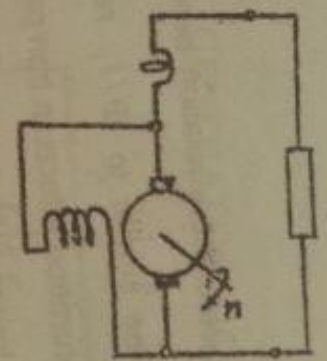

Short-Shunt

What is the difference between an AC motor and a DC motor ?


While both A.C. and D.C. motors serve the same function of converting electrical energy into mechanical energy, they are powered, constructed and controlled differently. The most basic difference is the power source. A.C. motors are powered from alternating current (A.C.) while D.C. motors are powered from direct current (D.C.), such as batteries, D.C. power supplies or an AC-to-DC power converter. D.C. wound field motors are constructed with brushes and a commutator, which add to the maintenance, limit the speed and usually reduce the life expectancy of brushed D.C. motors.

A.C. induction motors do not use brushes; they are very rugged and have long life expectancies. The final basic difference is speed control.

The speed of a D.C. motor is controlled by varying the armature winding's current while the speed of an A.C. motor is controlled by varying the frequency, which is commonly done with an adjustable frequency drive control.

AC Motors

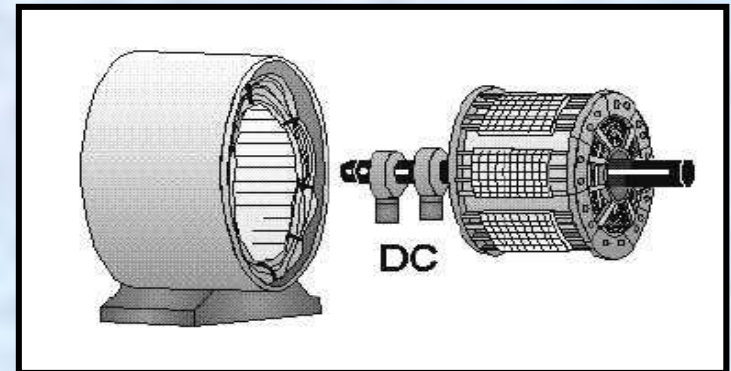- **Two parts: stator and rotor**
 - **Stator:** stationary electrical component
 - **Rotor:** rotates the motor shaft
- **Speed difficult to control**
- **Two types**
 - **Synchronous motor**
 - **Induction motor**



Synchronous motor

- **Constant speed fixed by system frequency**
- **DC for excitation and low starting torque: suited for low load applications**
- **Can improve power factor: suited for high electricity use systems**
- **Synchronous speed (N_s):**

$$N_s = 120 f / P$$

F = supply frequency



P = number of poles

Induction motor

Components

➤ Rotor

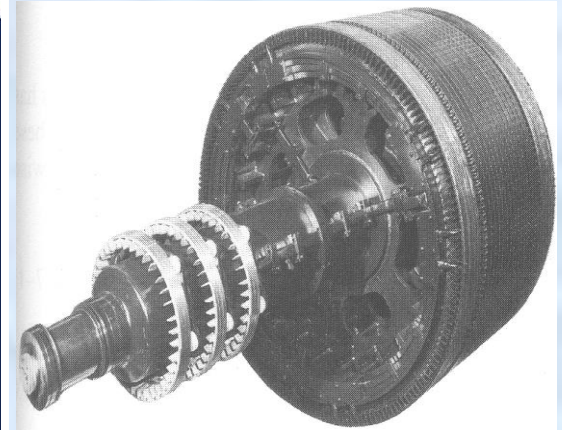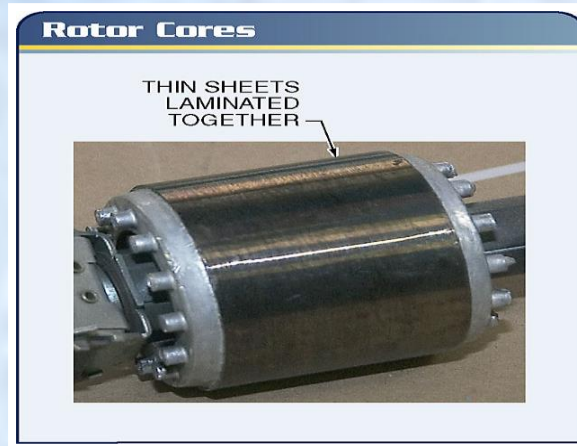- **Squirrel cage:** conducting bars in parallel slots




- **Wound rotor:** 3-phase, distributed winding



➤ Stator

- Stampings with slots to carry 3-phase
- Wound for definite number of poles



Electrical Degrees	
Poles per Phase	Electrical Degrees per Revolution
	$2 \times 180 = 360$
	$4 \times 180 = 720$

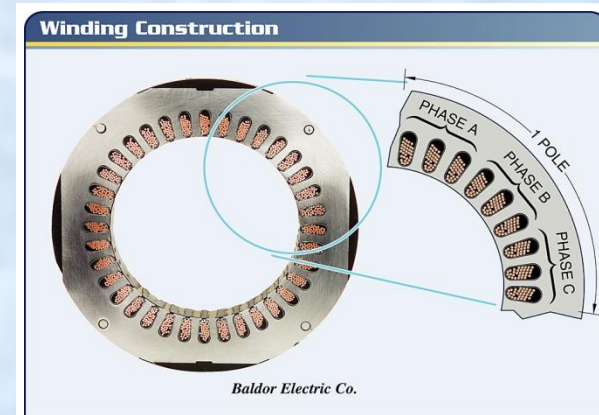

Wound rotor (Slip Ring Induction Motor)

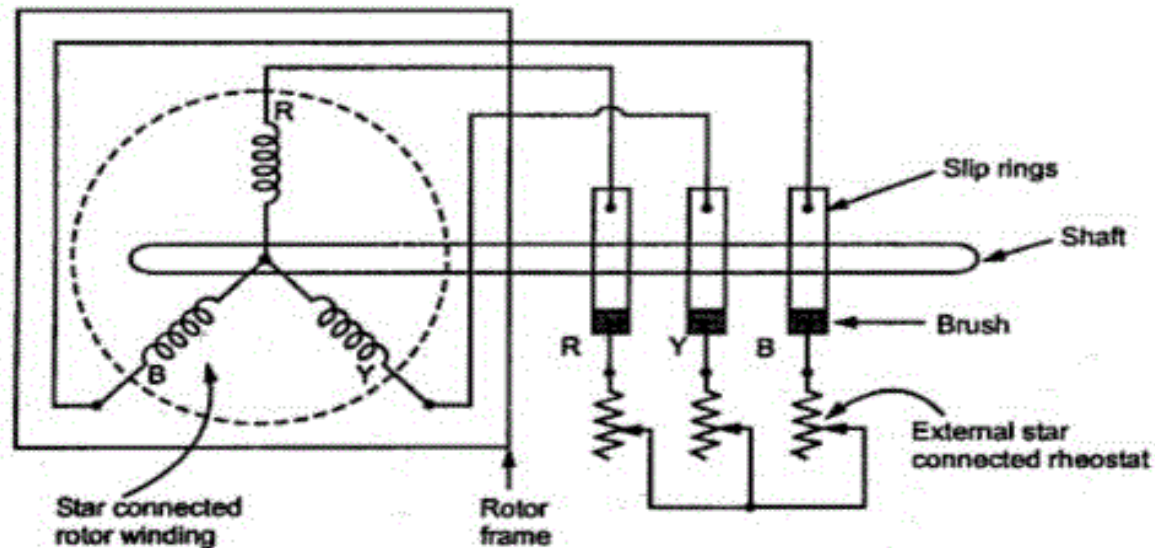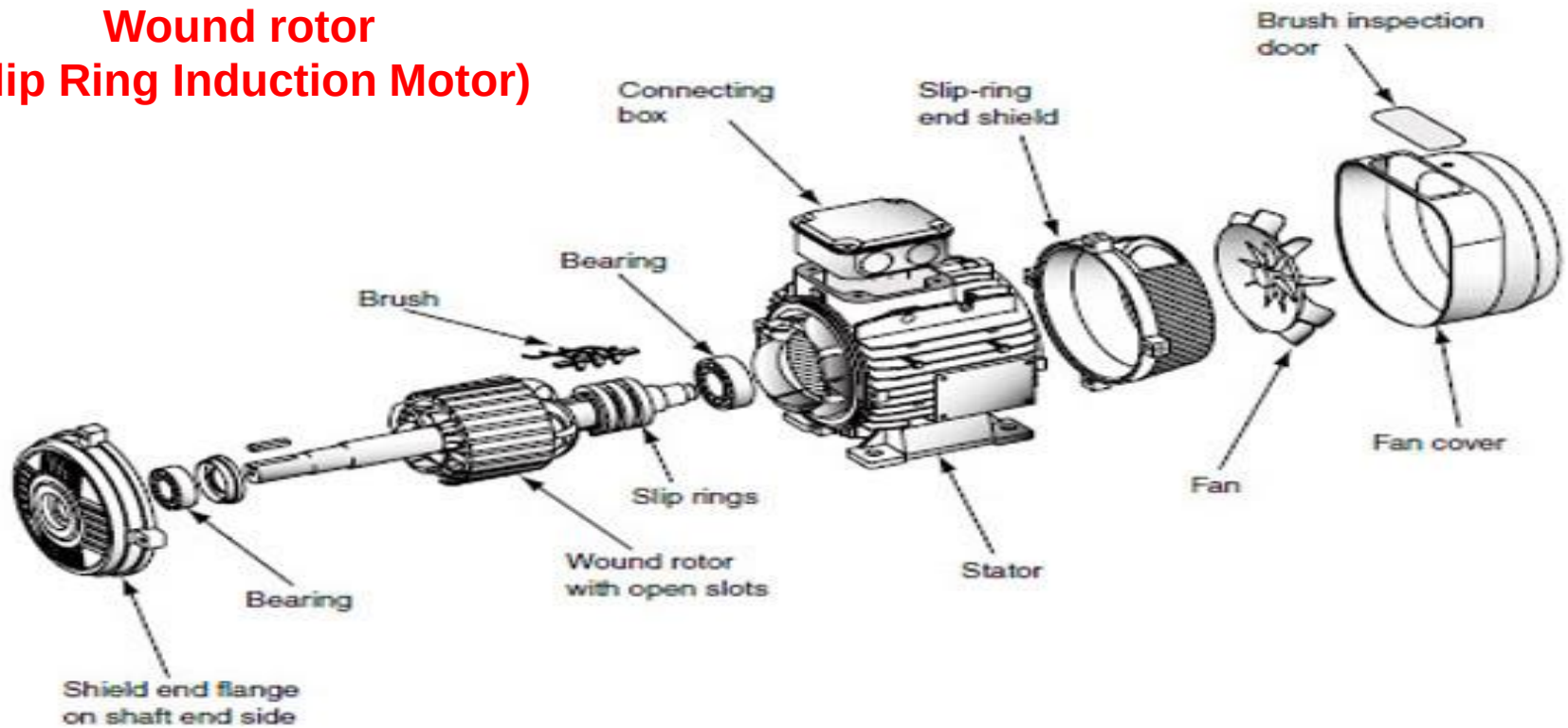

Squirrel cage Induction Motor

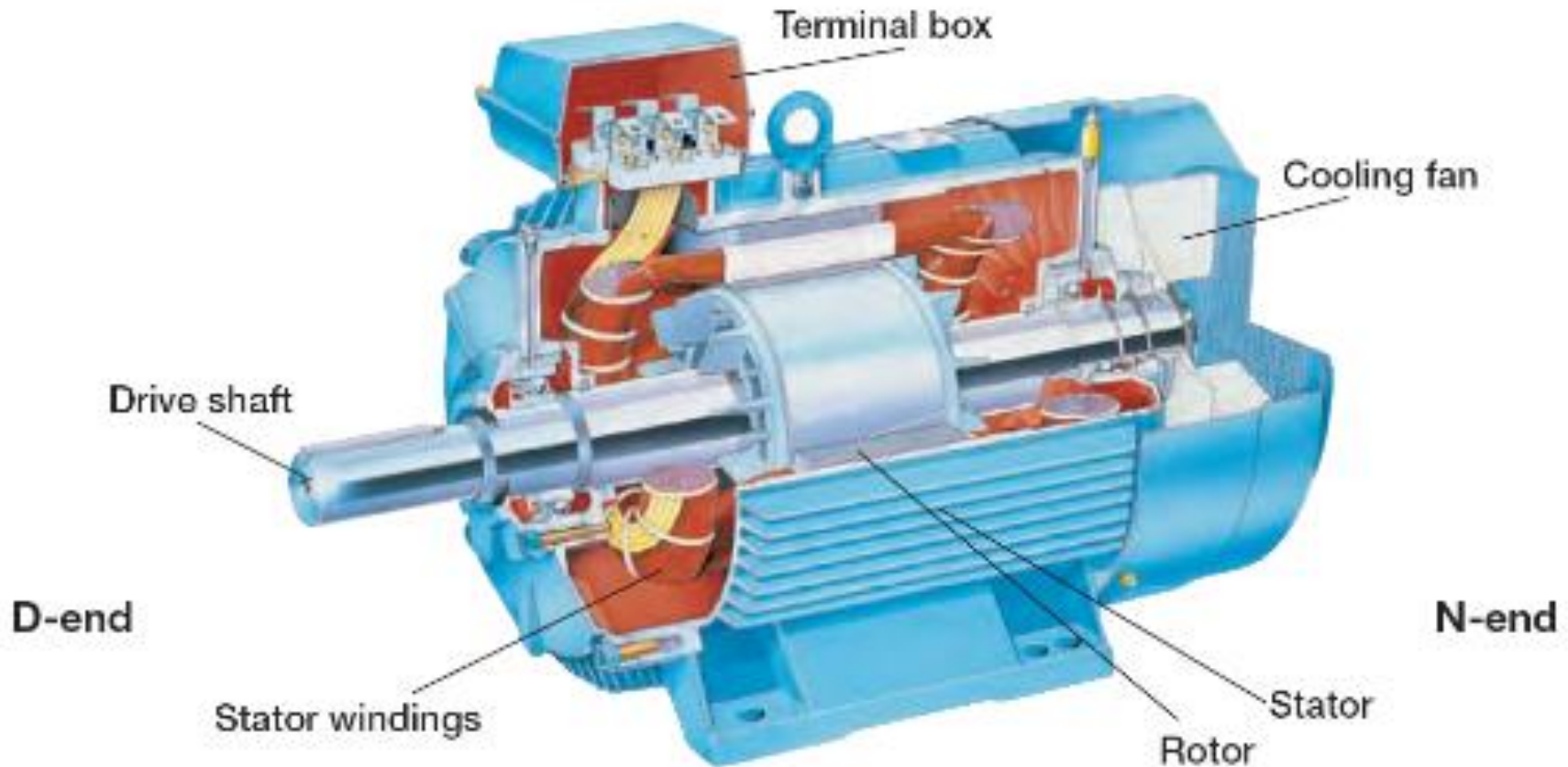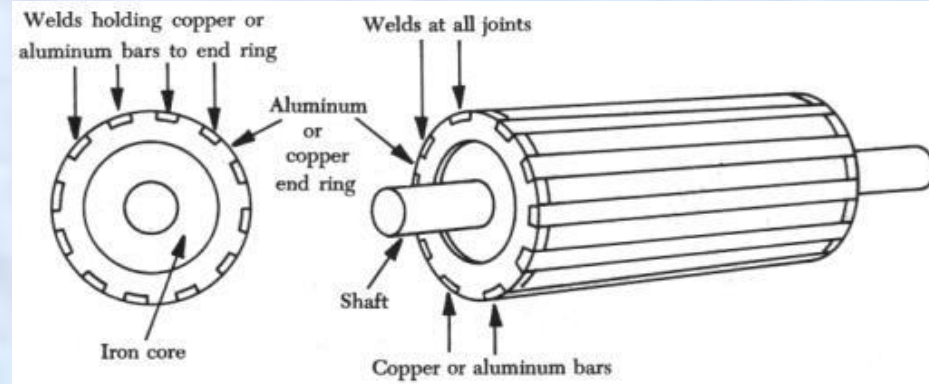

What is the difference between a slip ring and a squirrel cage?

Both are the types of Asynchronous machines (Induction Machines), difference is that in Slip ring we can change the starting torque by simply varying the external resistance connected to rotor, this is not possible in case of squirrel cage induction motor.


Although Squirrel cage is easy to maintain and cost effective as compared to slip ring as it has slip rings, brushes.

Application of slip ring: Hoist, Elevators, pumps where high starting torque is required.

Application of Squirrel cage: motor used in industries because there is need of high torque production by motor.

How induction motors work

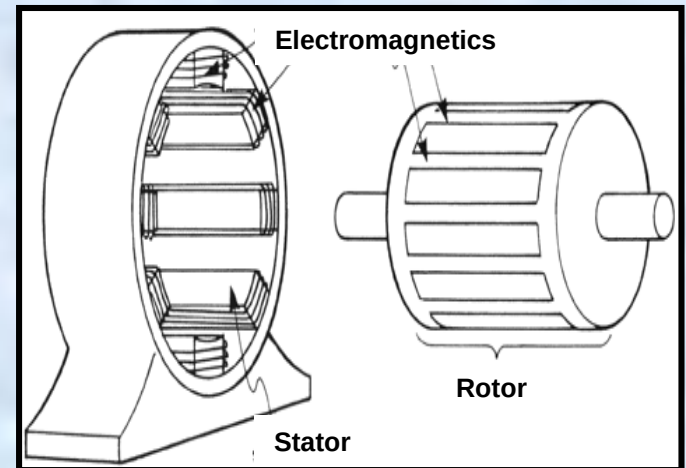- Electricity supplied to stator
- Magnetic field generated that moves around rotor
- Current induced in rotor
- Rotor produces second magnetic field that opposes stator magnetic field
- Rotor begins to rotate



Types of Induction motor

➤ Single-phase induction motor

- Single-phase power supply
- Squirrel cage rotor
- Require device to start motor
- 3 to 4 HP applications

➤ Three-phase induction motor

- Three-phase supply produces magnetic field
- Squirrel cage or wound rotor
- Self-starting
- 1/3 to hundreds HP applications: pumps, compressors, conveyor belts, grinders

Speed and slip

- Motor never runs at synchronous speed but lower “base speed”
- Difference is “slip”
- Calculate % slip:


$$\% \text{ Slip} = \frac{N_s - N_r}{N_s} \times 100$$

N_s = synchronous speed in RPM
 N_r = rotor speed in RPM

Relationship load, speed and torque

At start: high current and low “pull-up” torque

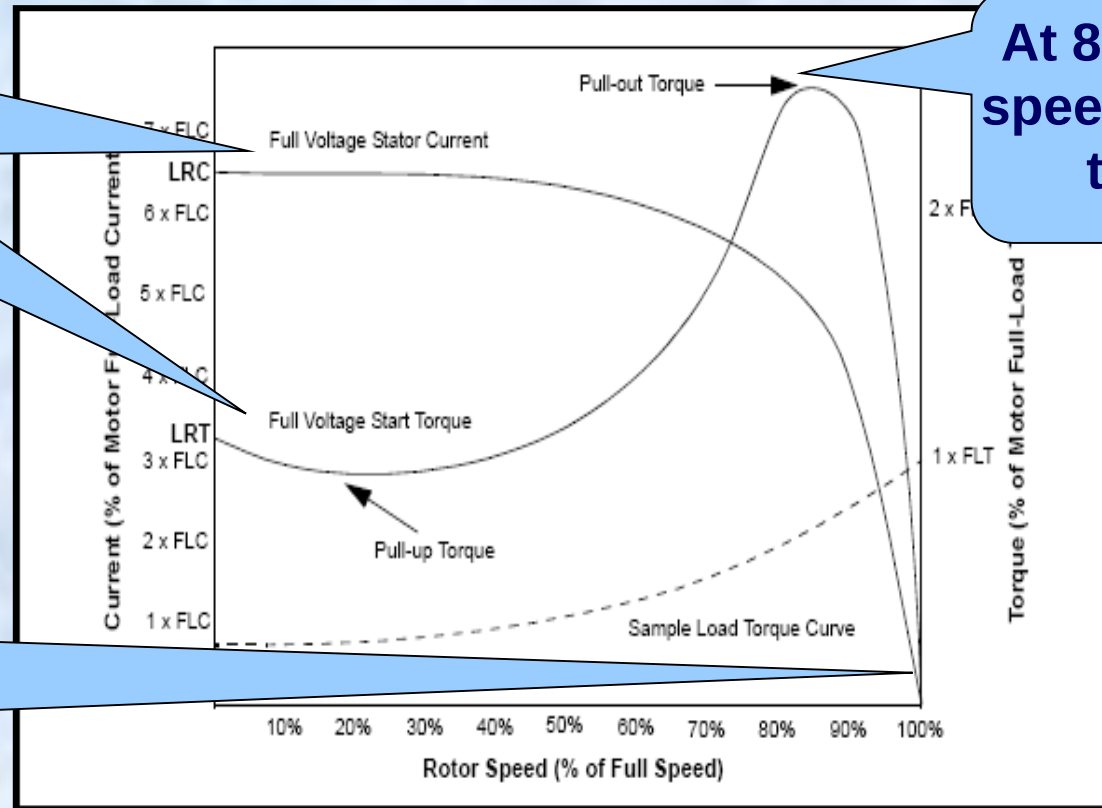At full speed: torque and stator current are zero





At 80% of full speed: highest torque

Efficiency of Electric Motors

Motors loose energy when serving a load

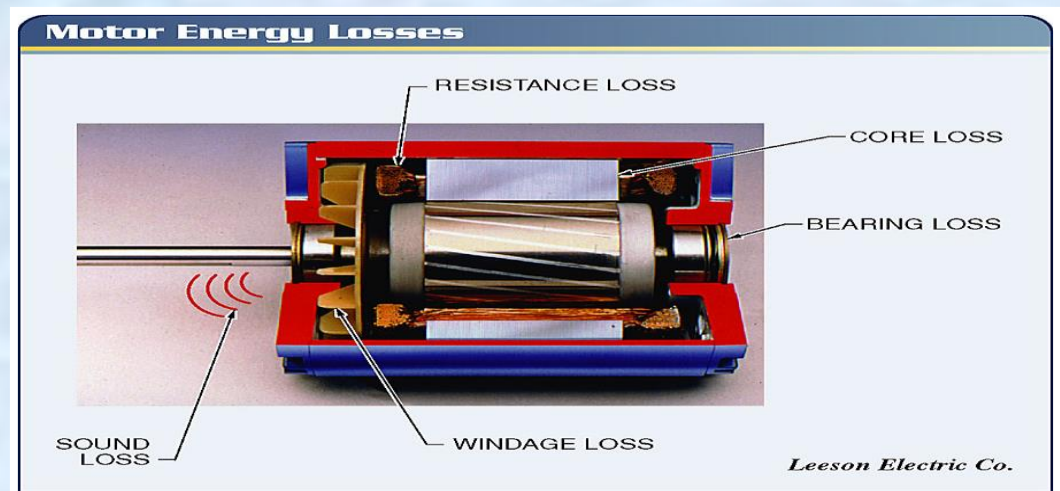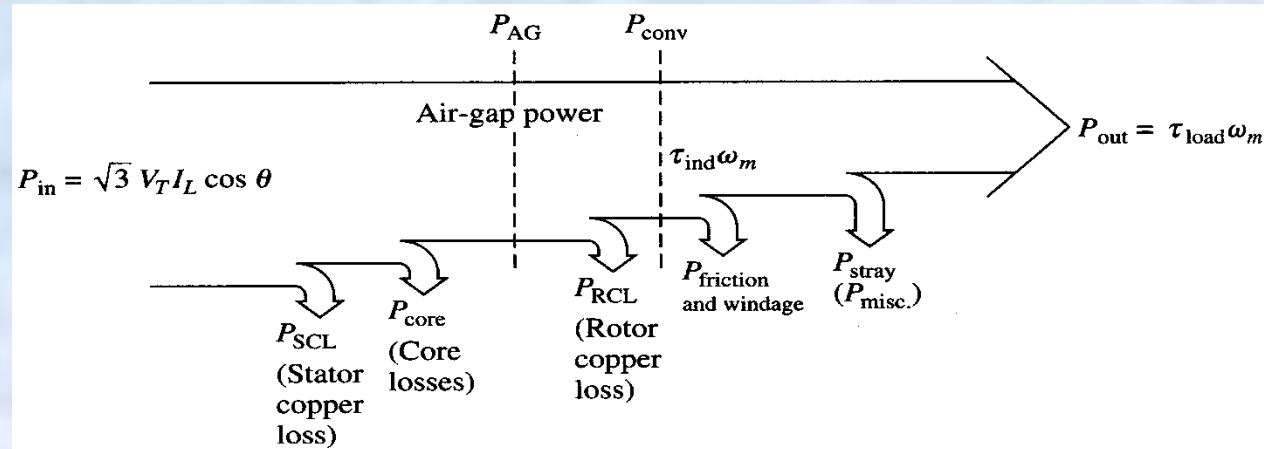- Fixed loss
- Rotor loss
- Stator loss
- Friction and rewinding
- Stray load loss



Maintenance

Checklist to maintain motor efficiency

- **Inspect motors regularly for wear, dirt/dust**
- **Checking motor loads for over loading**
- **Lubricate appropriately**
- **Check alignment of motor and equipment**
- **Ensure supply wiring and terminal box and properly sized and installed**
- **Provide adequate ventilation**

Speed & Torque control of Induction Motor

- **Multi-speed motors**

- Limited speed control: 2 – 4 fixed speeds

- **Wound rotor motor drives**

- Variable resistors to control torque performance


- **Variable speed drives (VSDs)**

- Reduce electricity by >50% in fans and pumps
 - Convert 50Hz incoming power to variable frequency and voltage: change speed


CHAPTER 6
Different types of
Motor Control
Circuit

1- Motor control circuit

1-Wire control

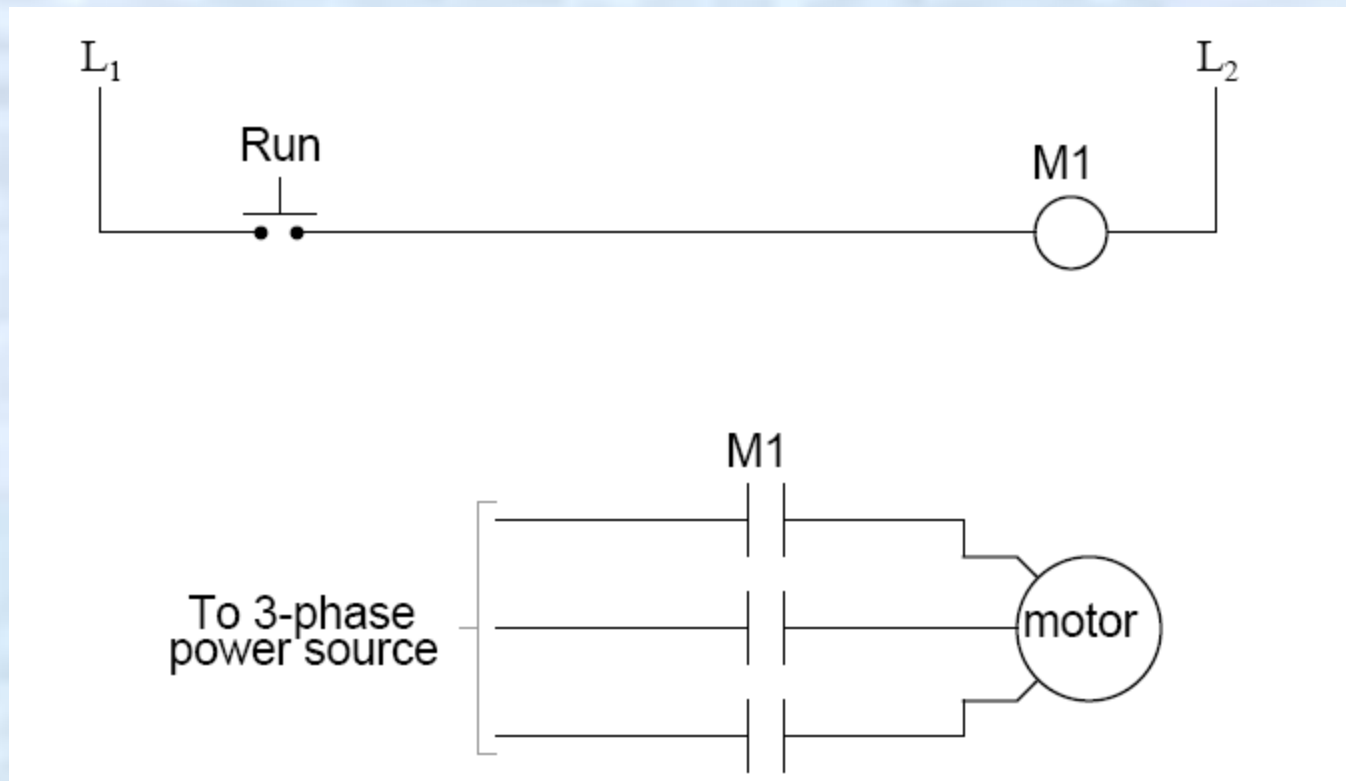


EKTS Simulation

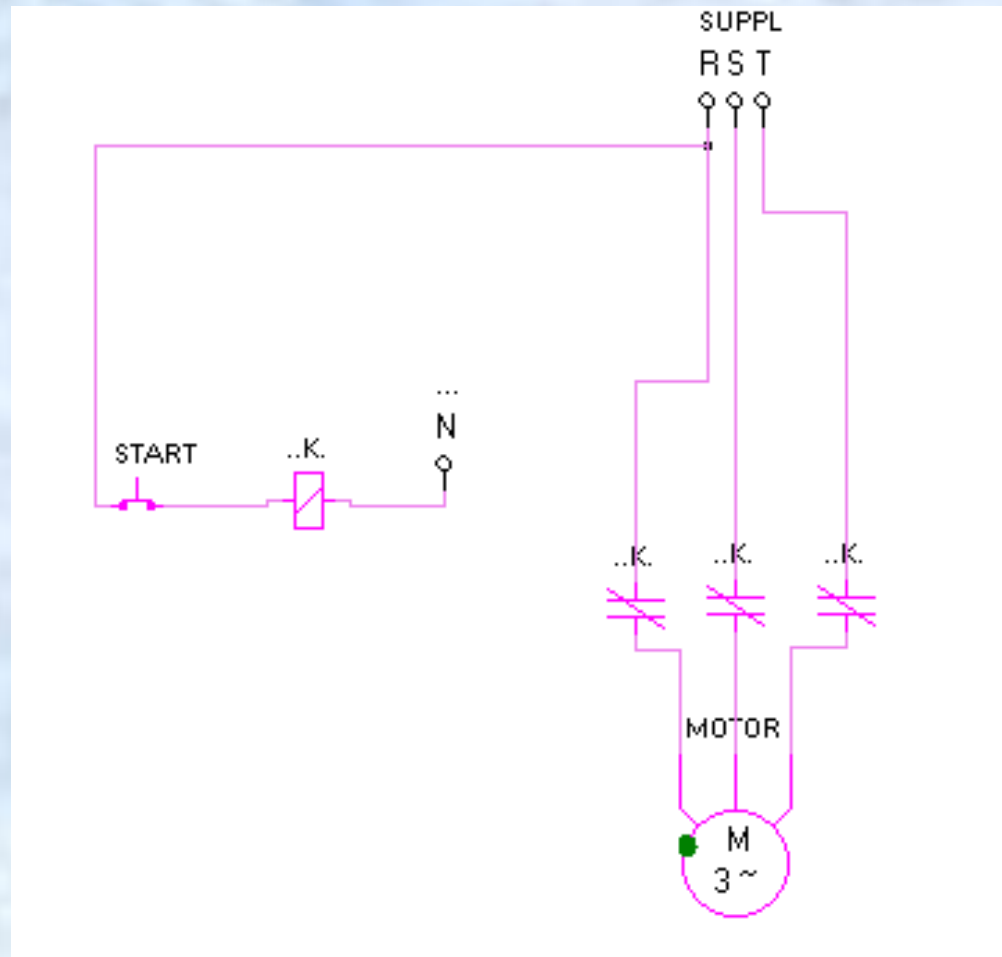



2- Motor control latched circuit

2-Wire control


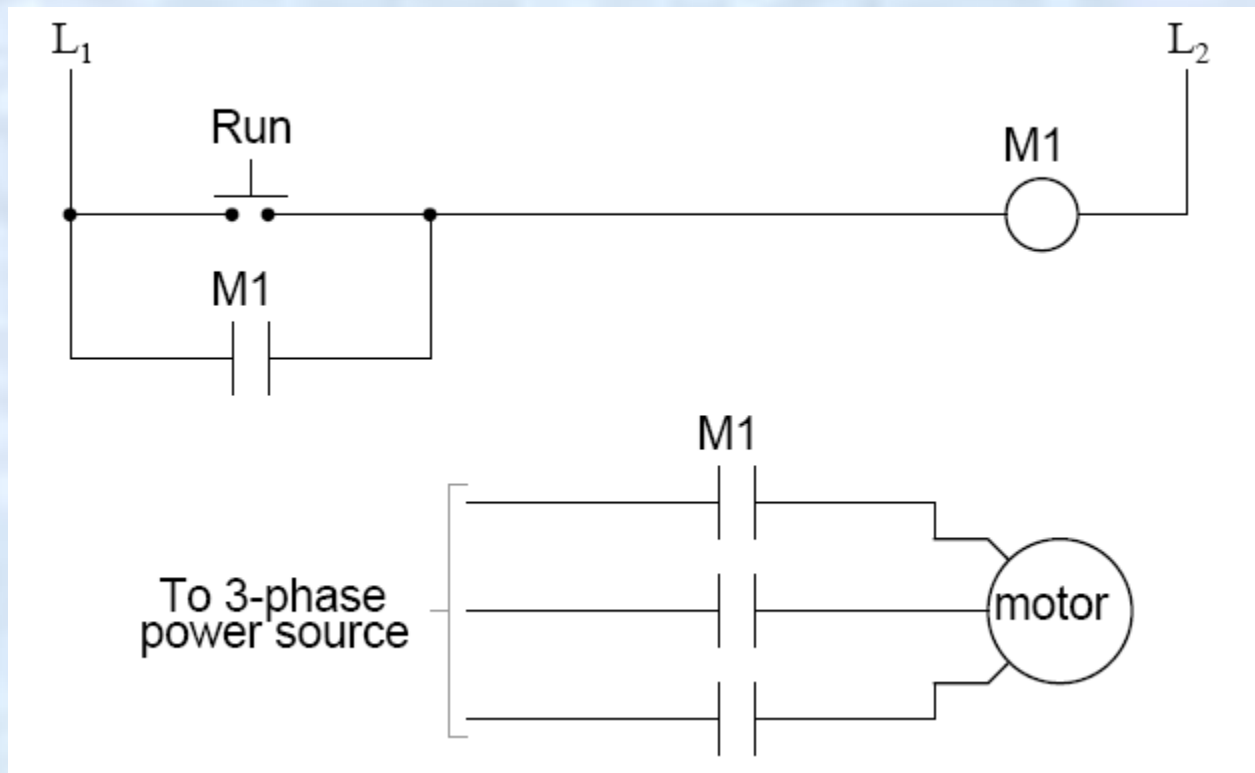


EKTS Simulation

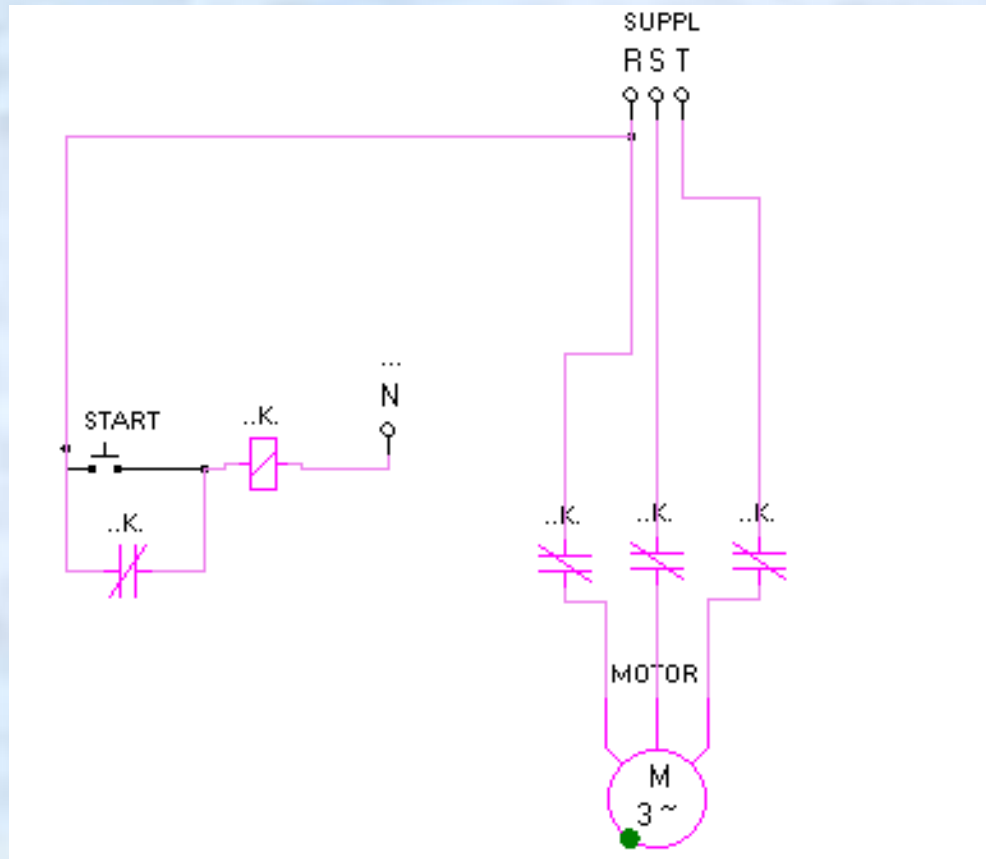


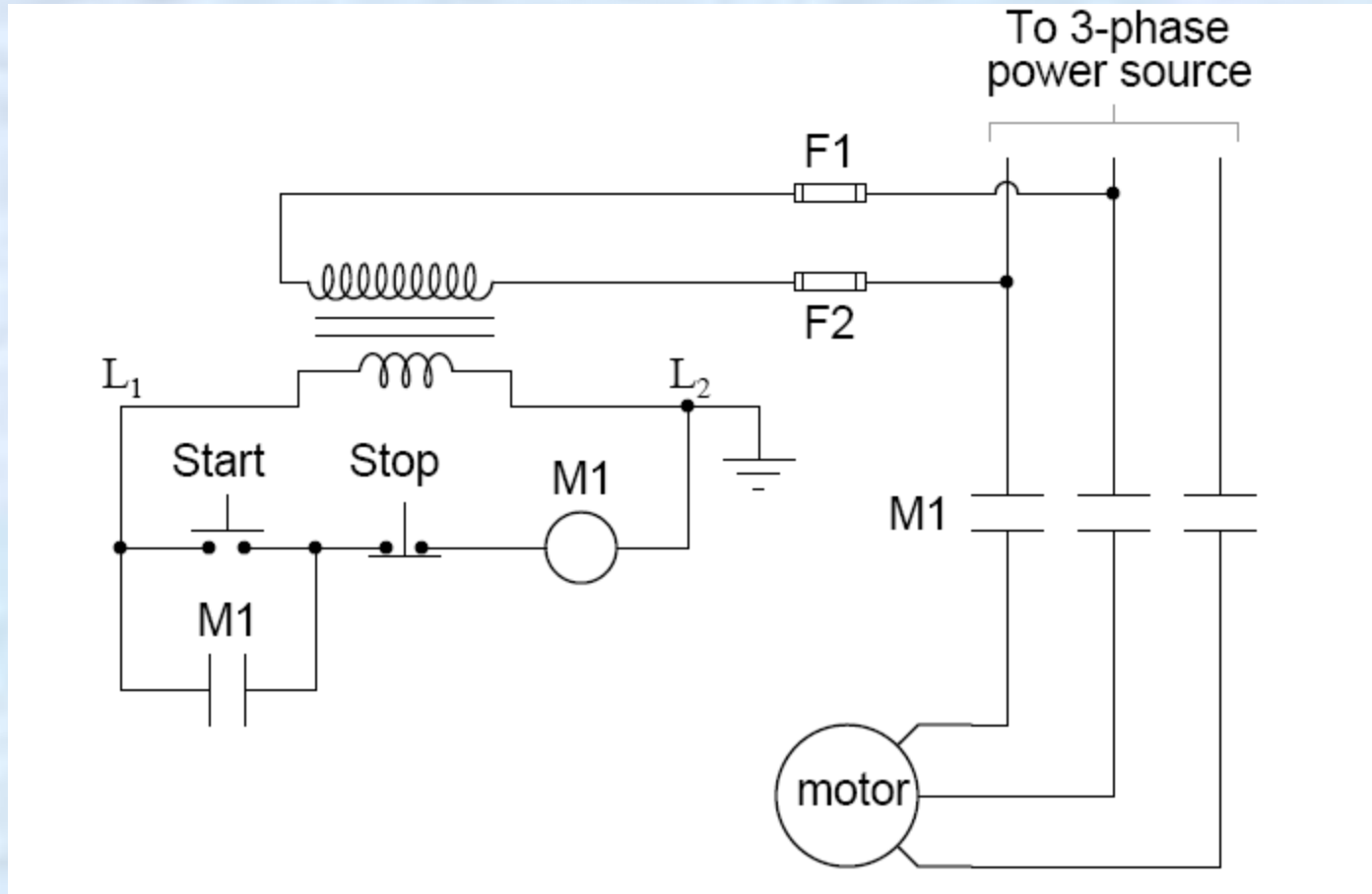



3-Wire control (220 V)

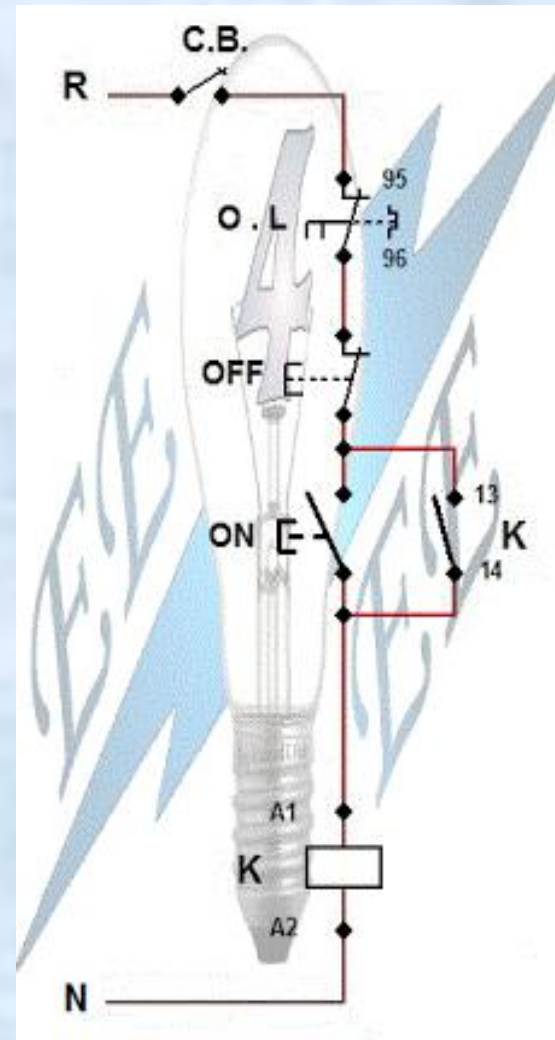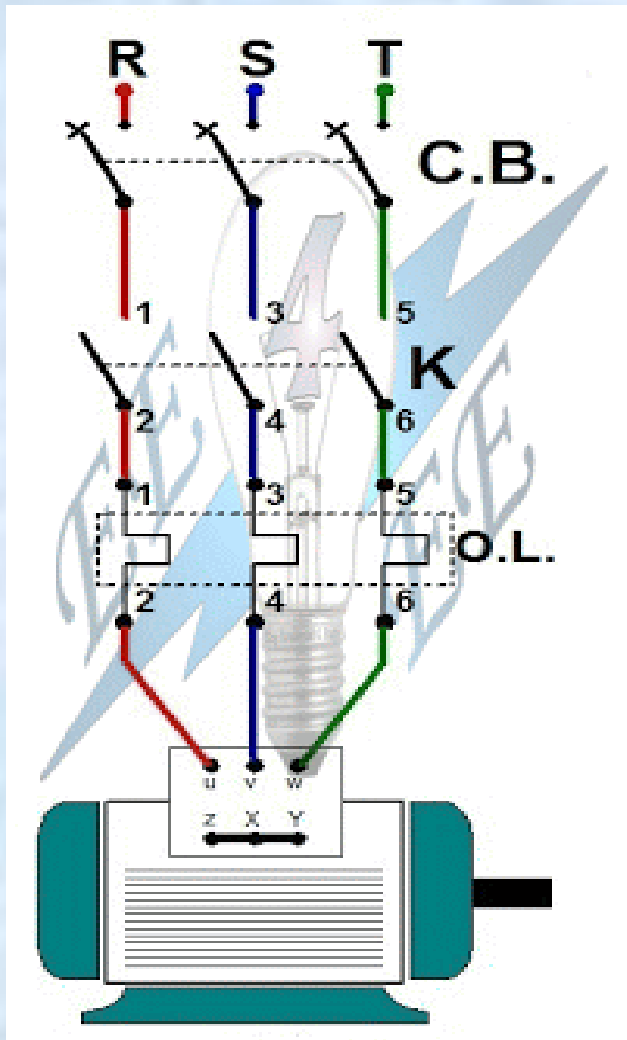



EKTS Simulation

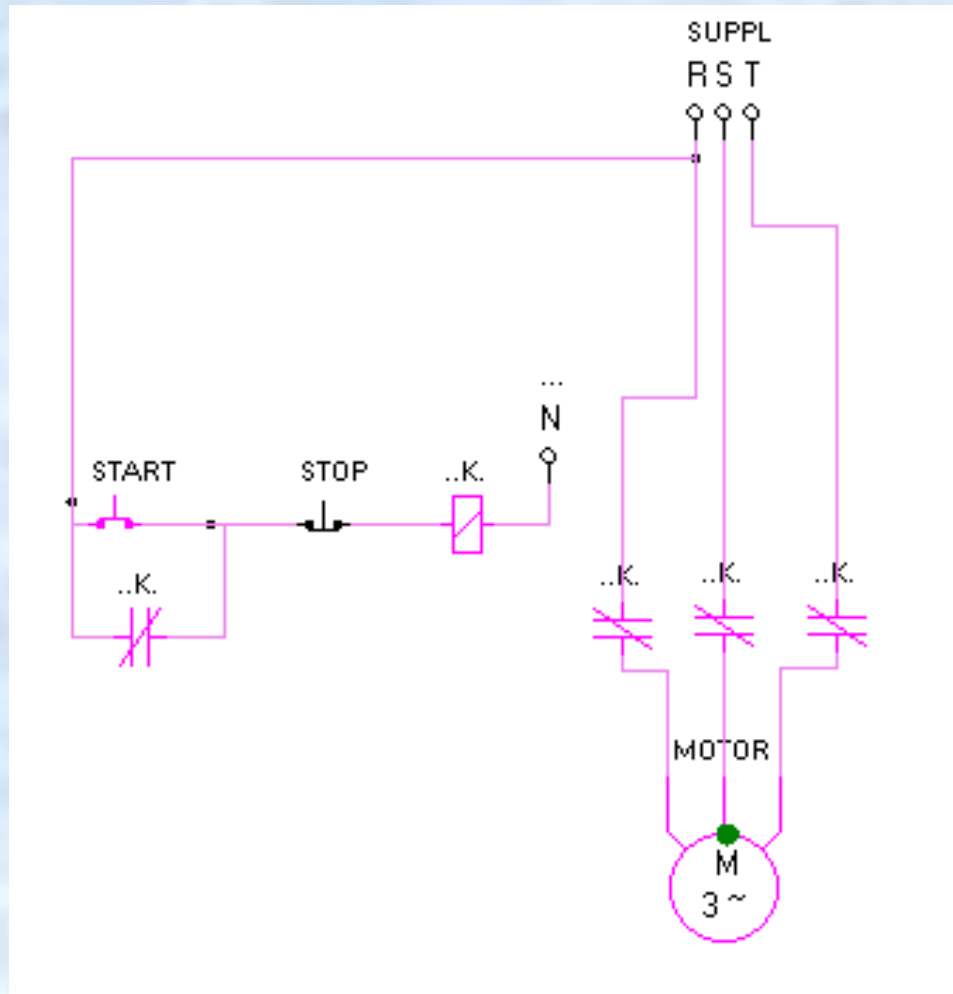



4- ON-OFF-Fault motor circuit

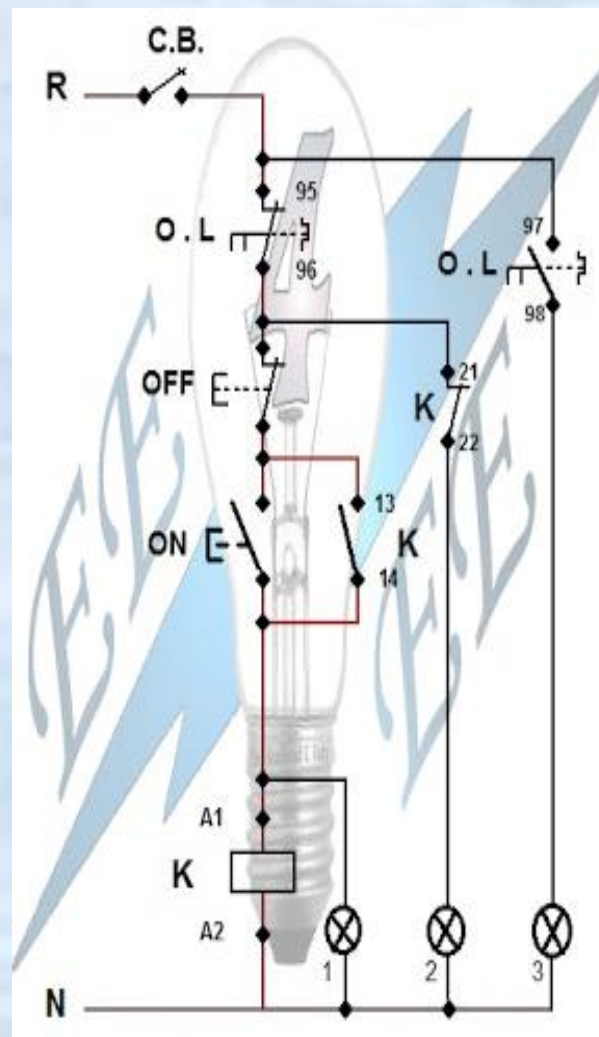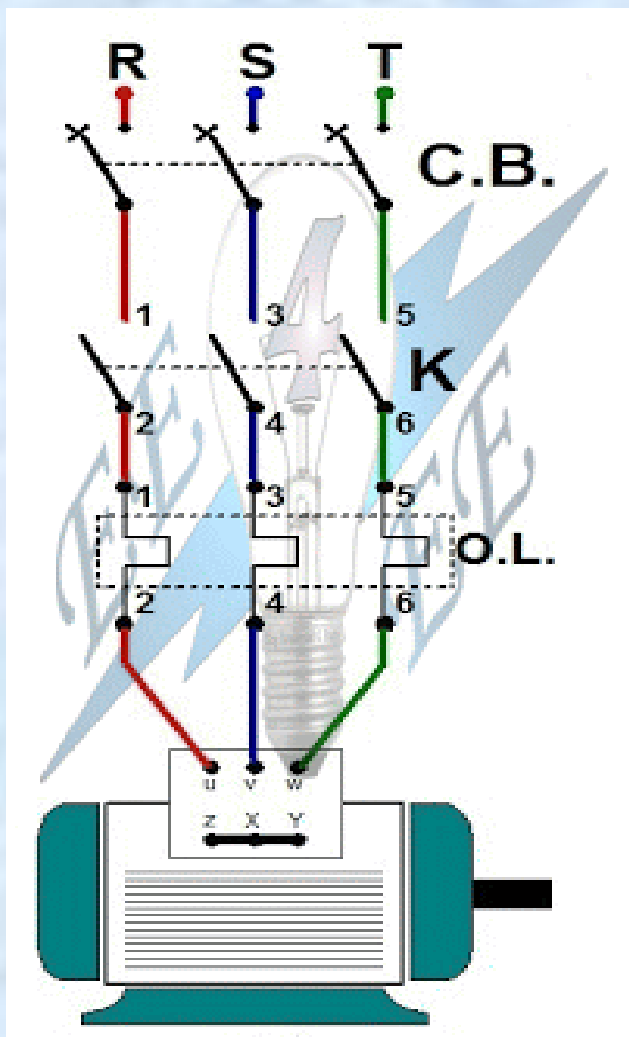



EKTS Simulation

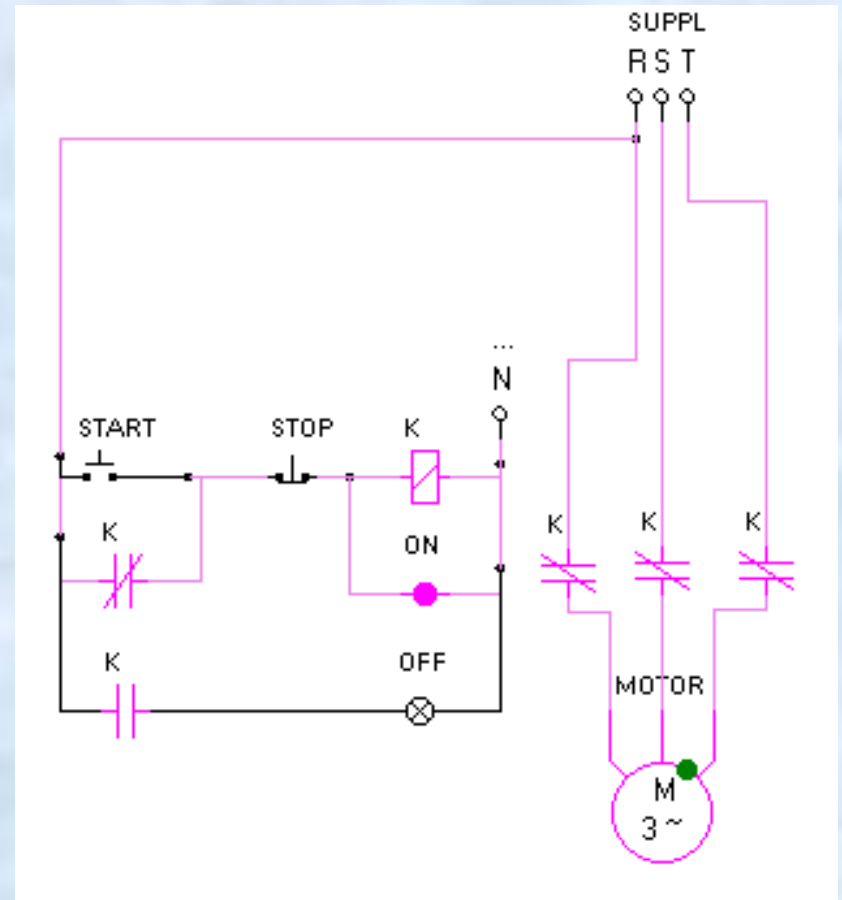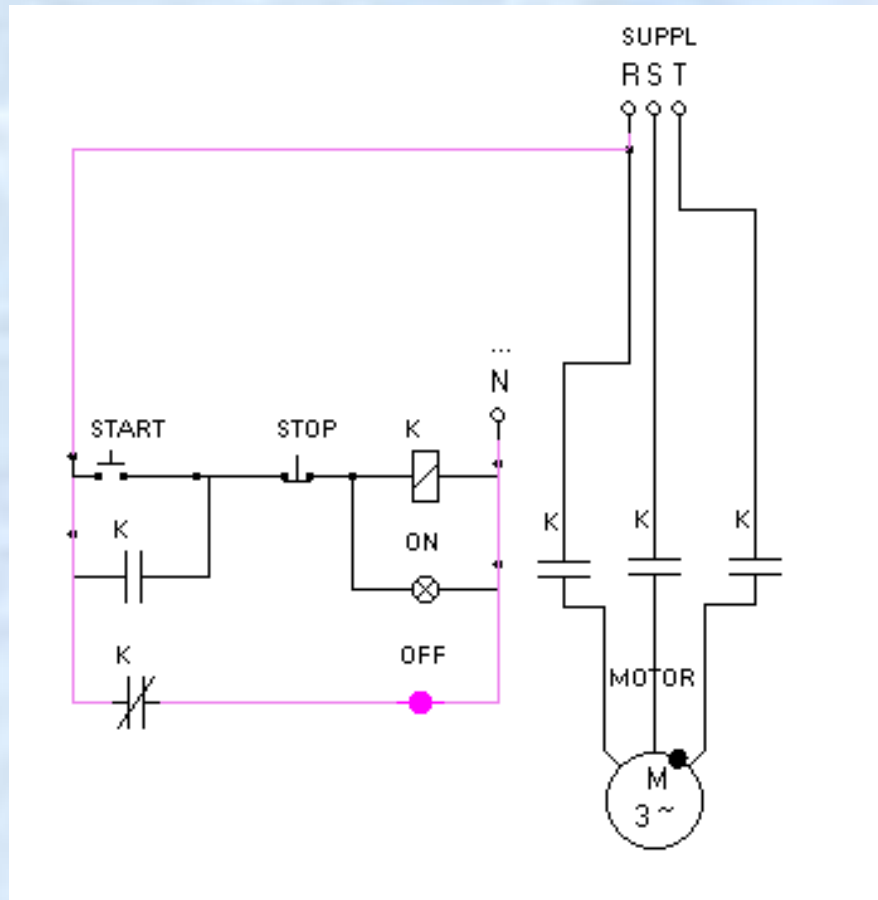

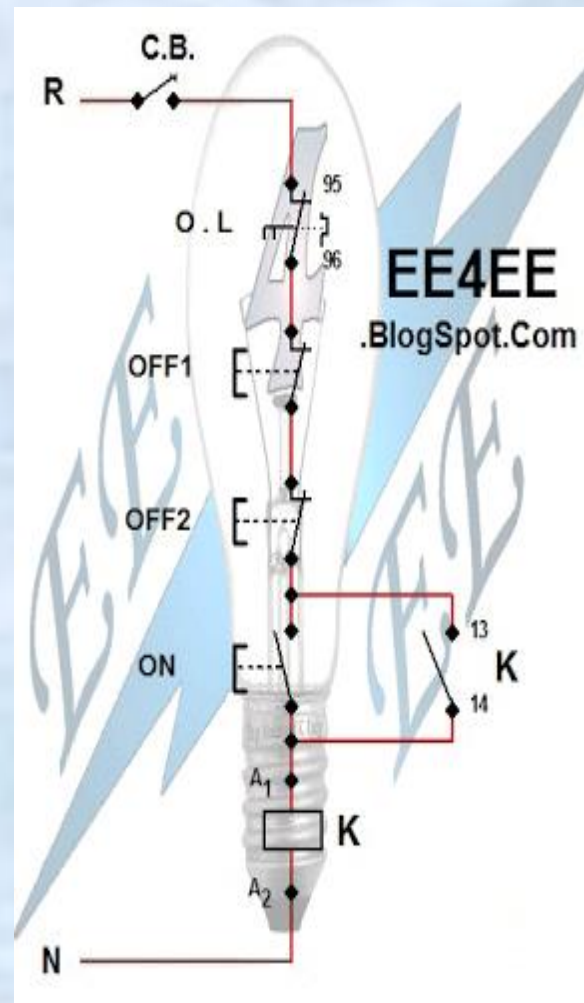
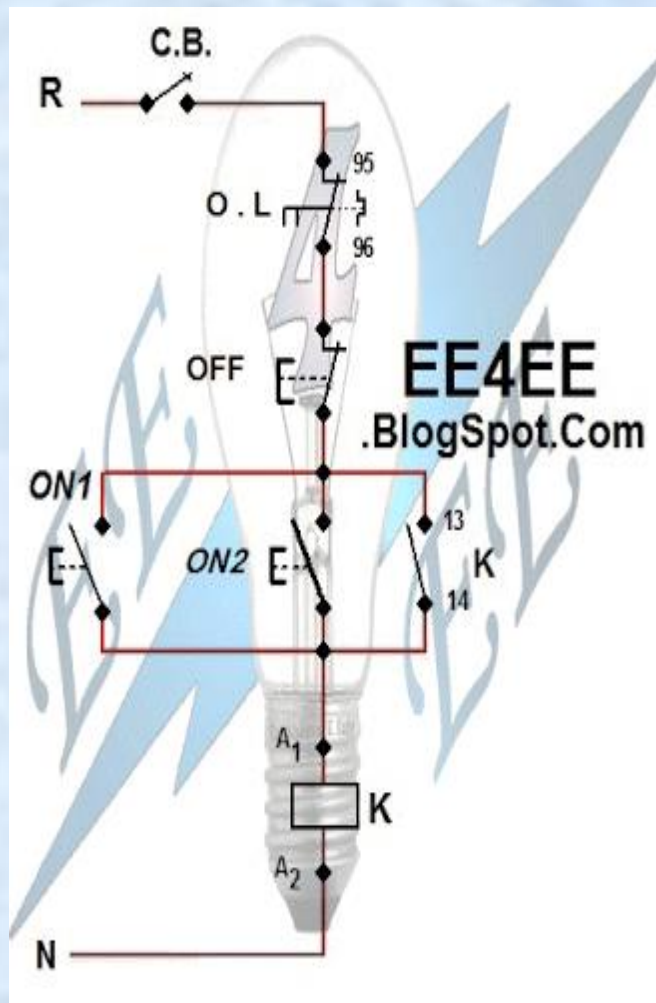
5- Different location controlling motor circuit



EKTS Simulation

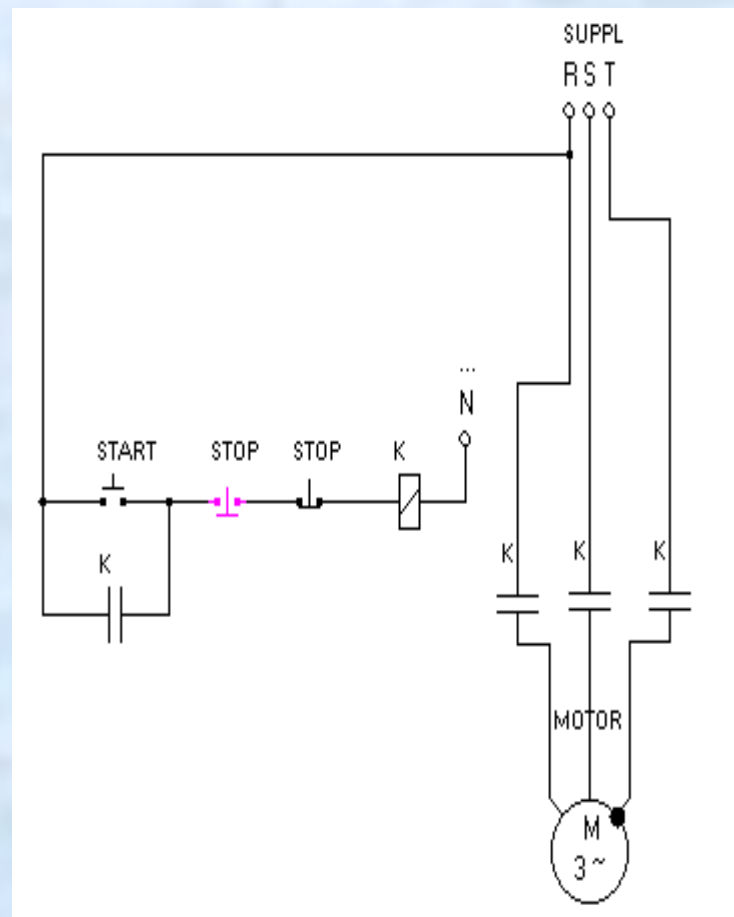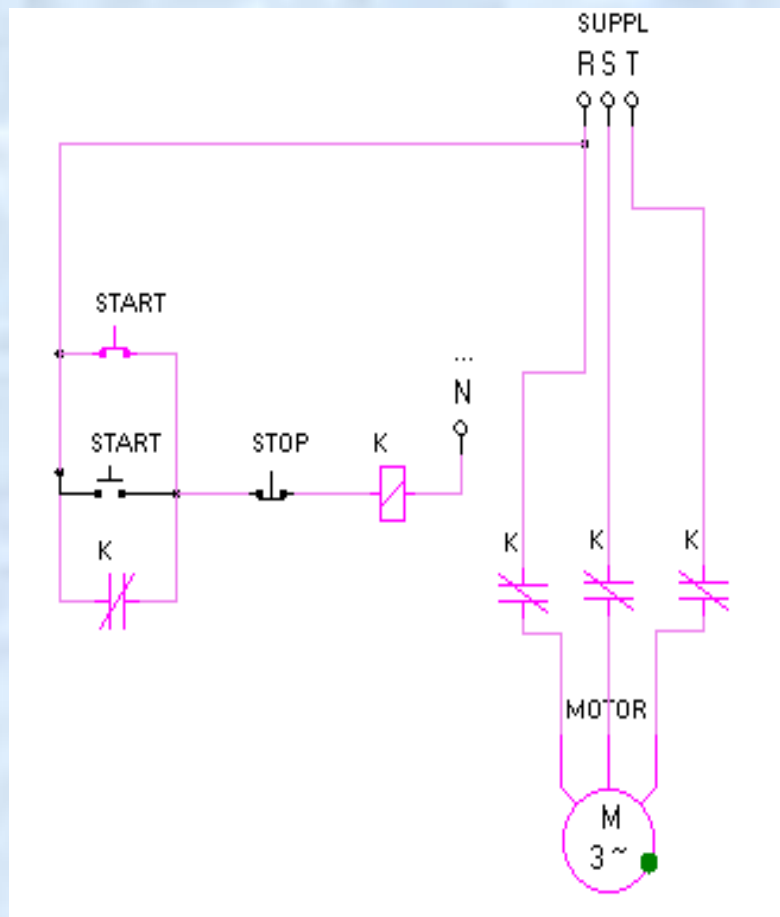

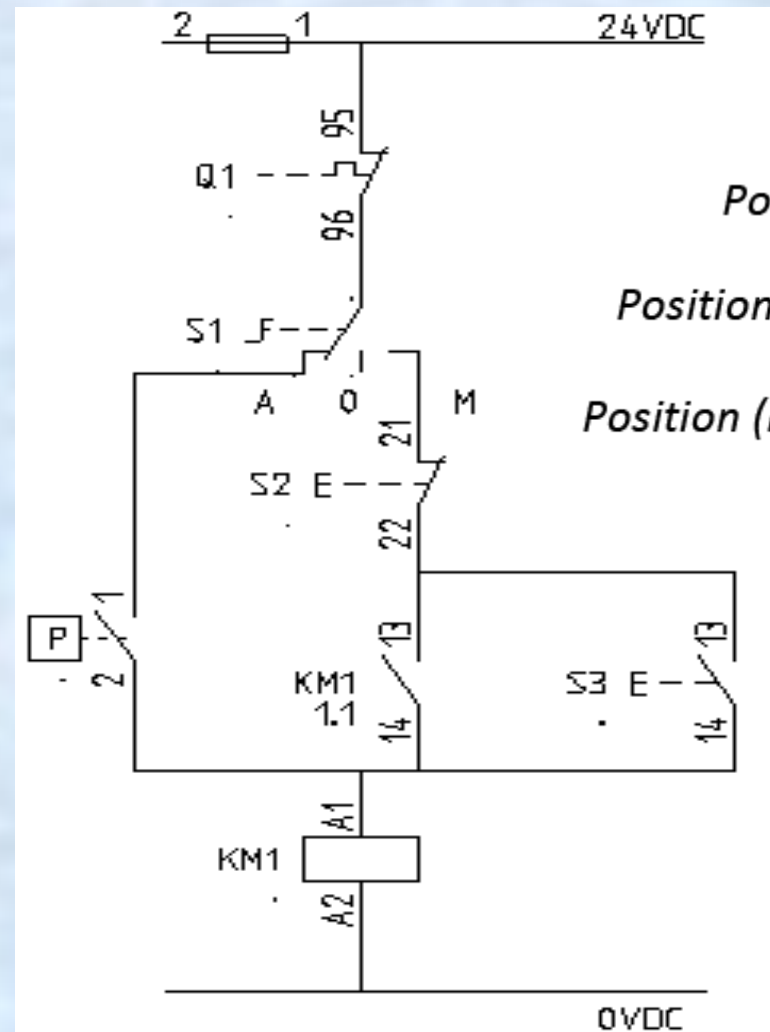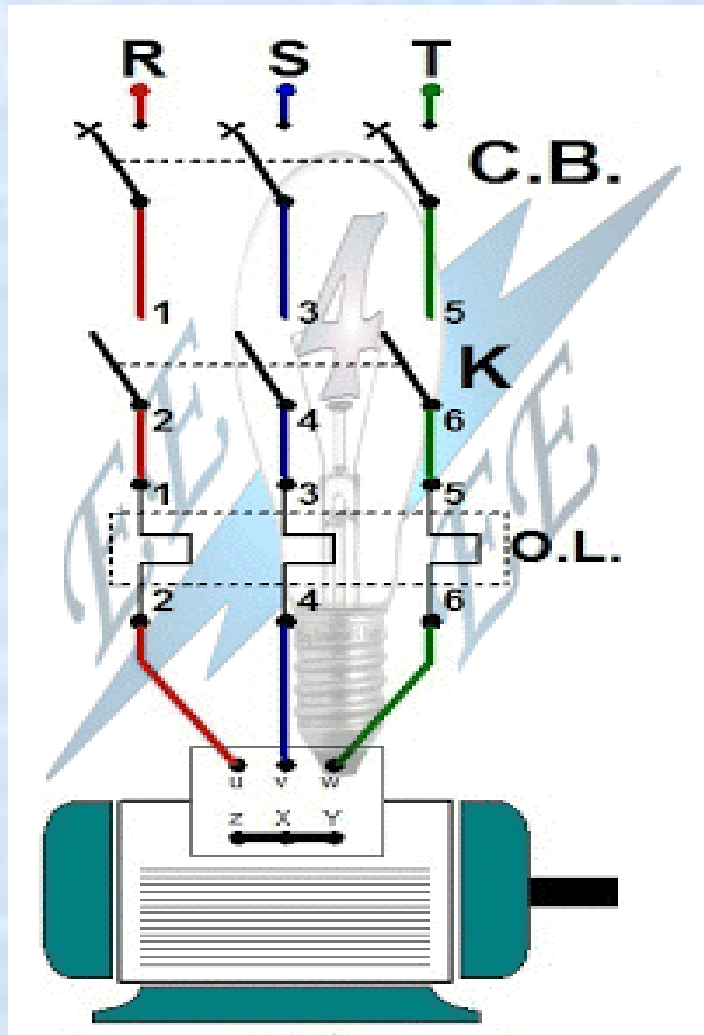6- Manual & Automatic pump control using pressure switch





Position (0): Stop


Position (A): Automatic

Position (M): Manual

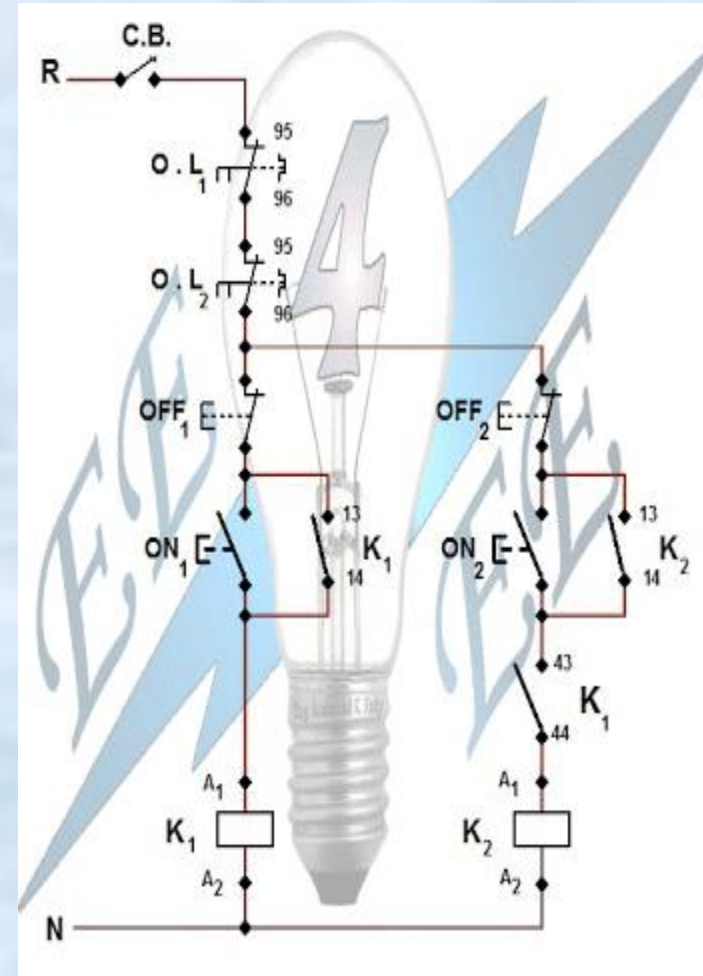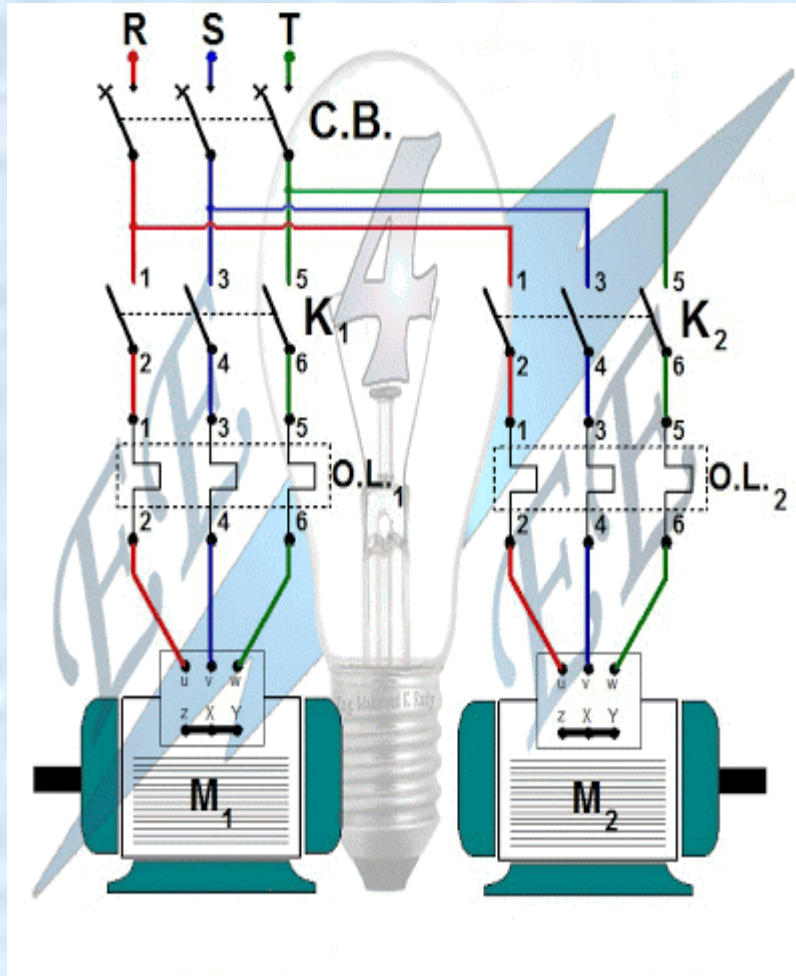
7- Second motor depend on first motor circuit





EKTS Simulation

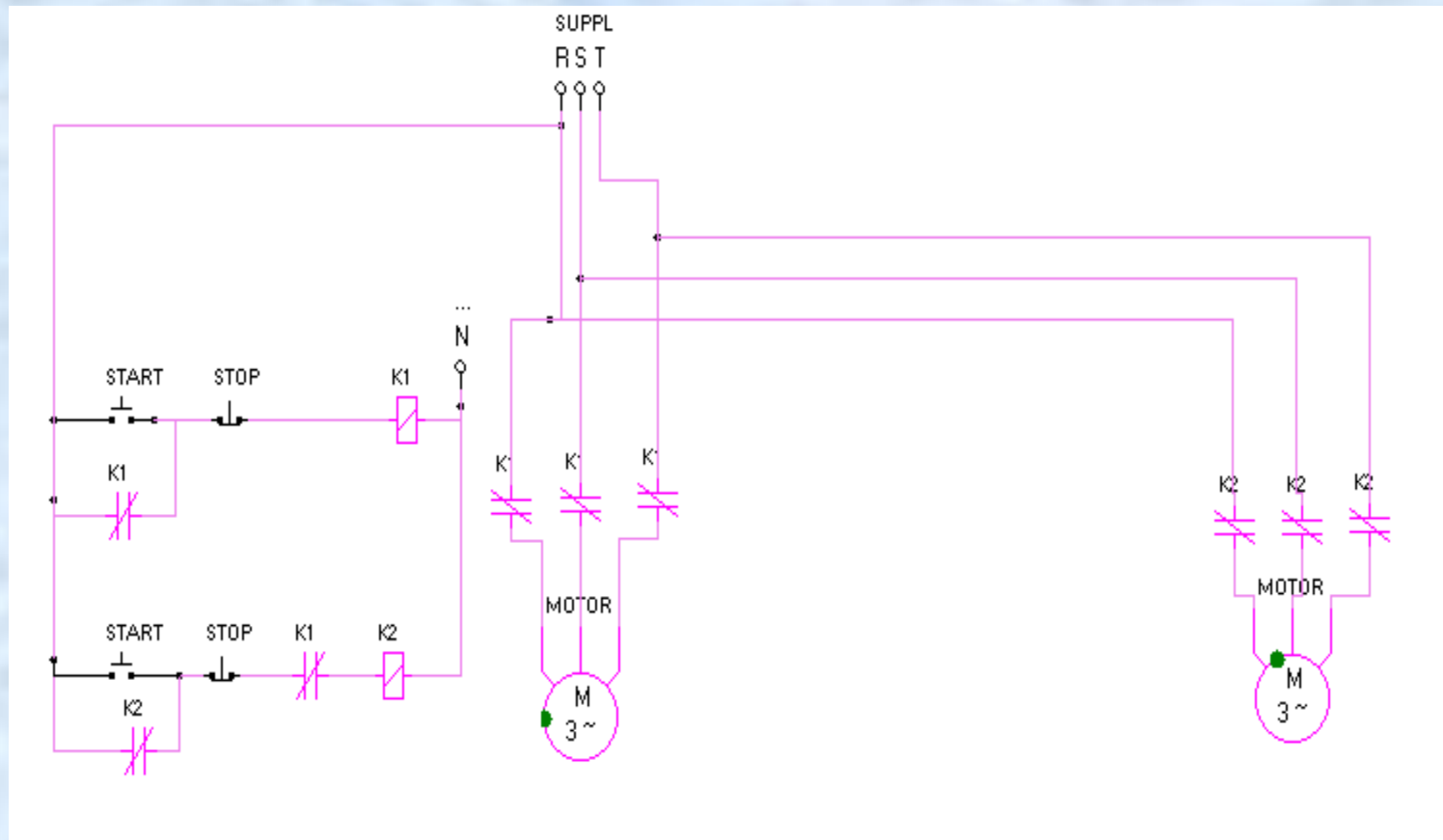


Think what does it mean ????

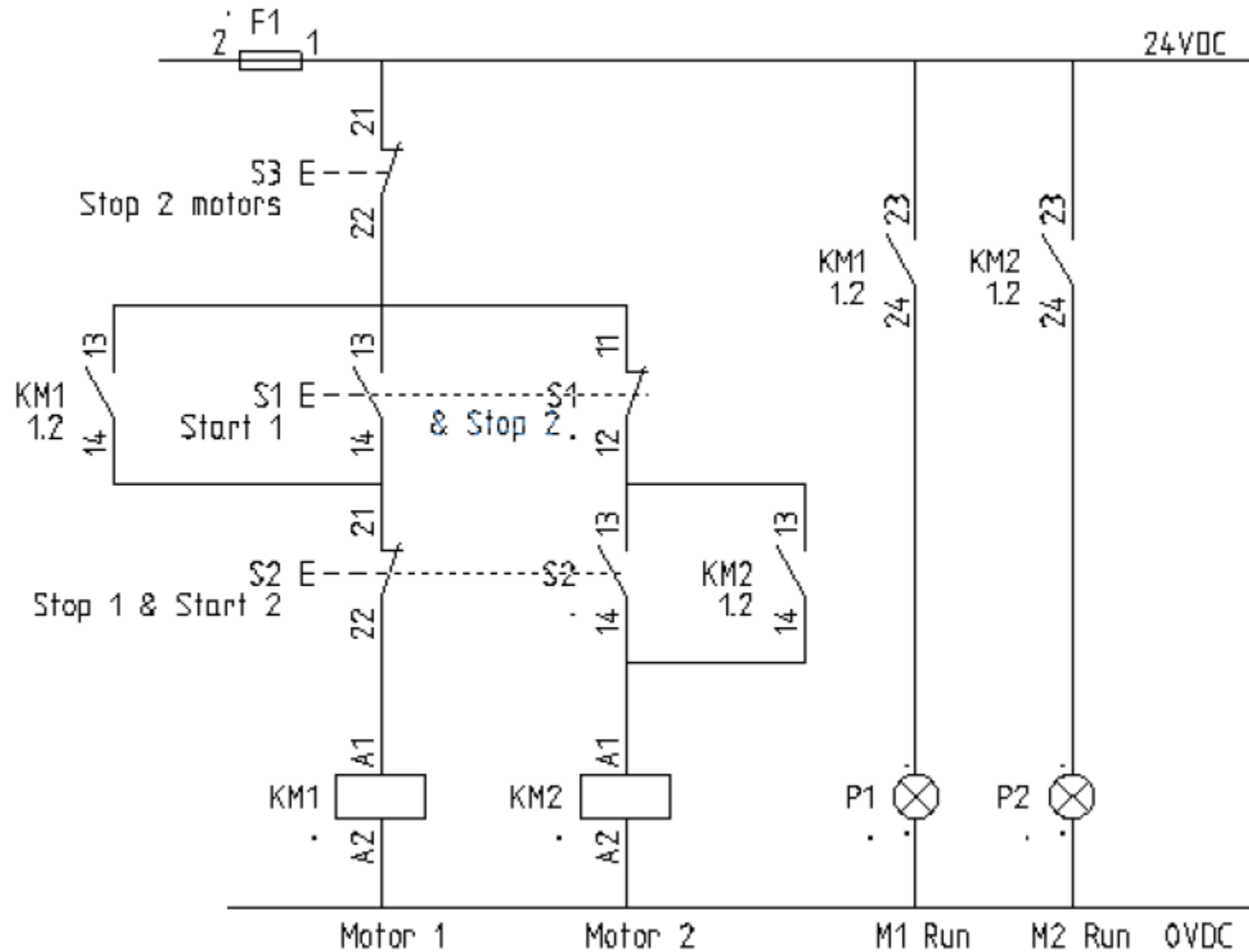



8- One out of two motor circuit

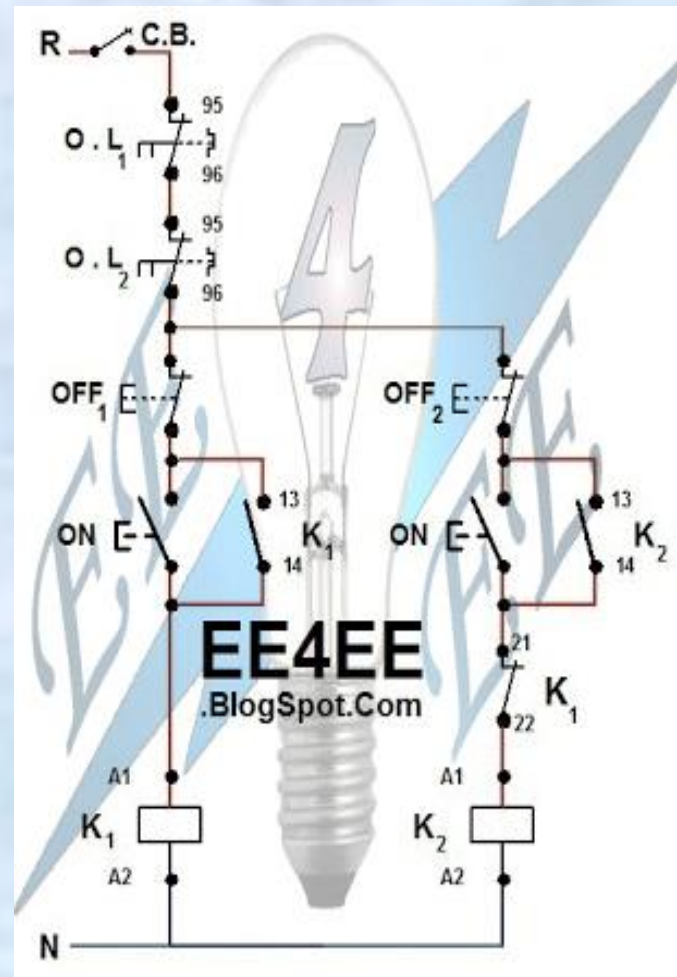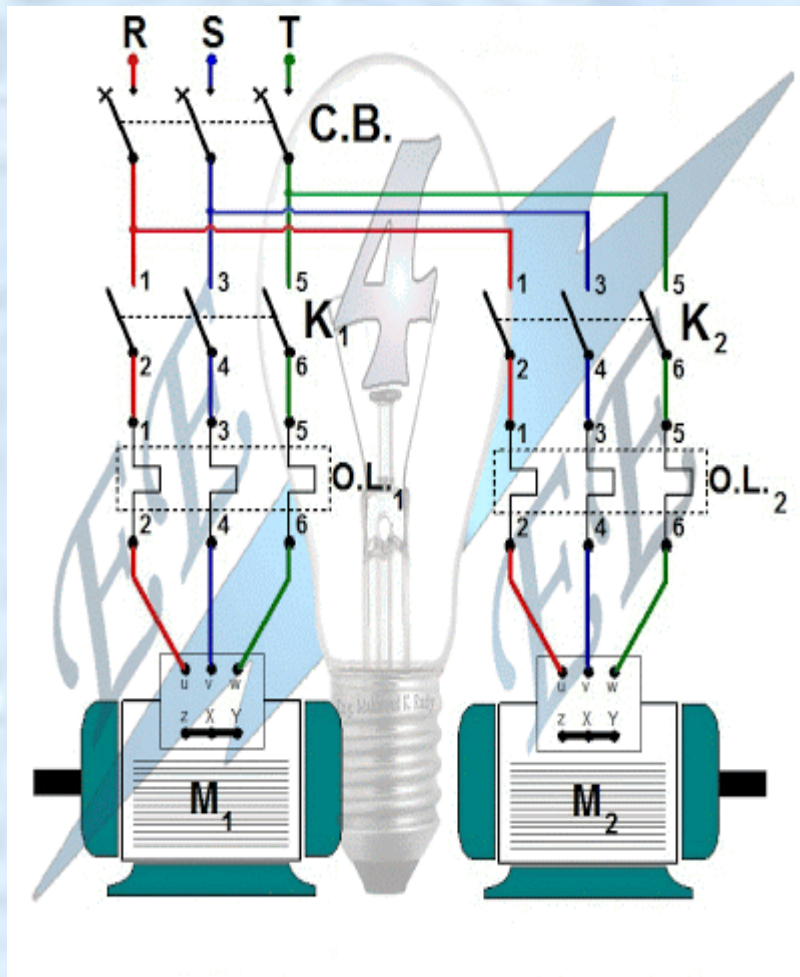


EKTS Simulation

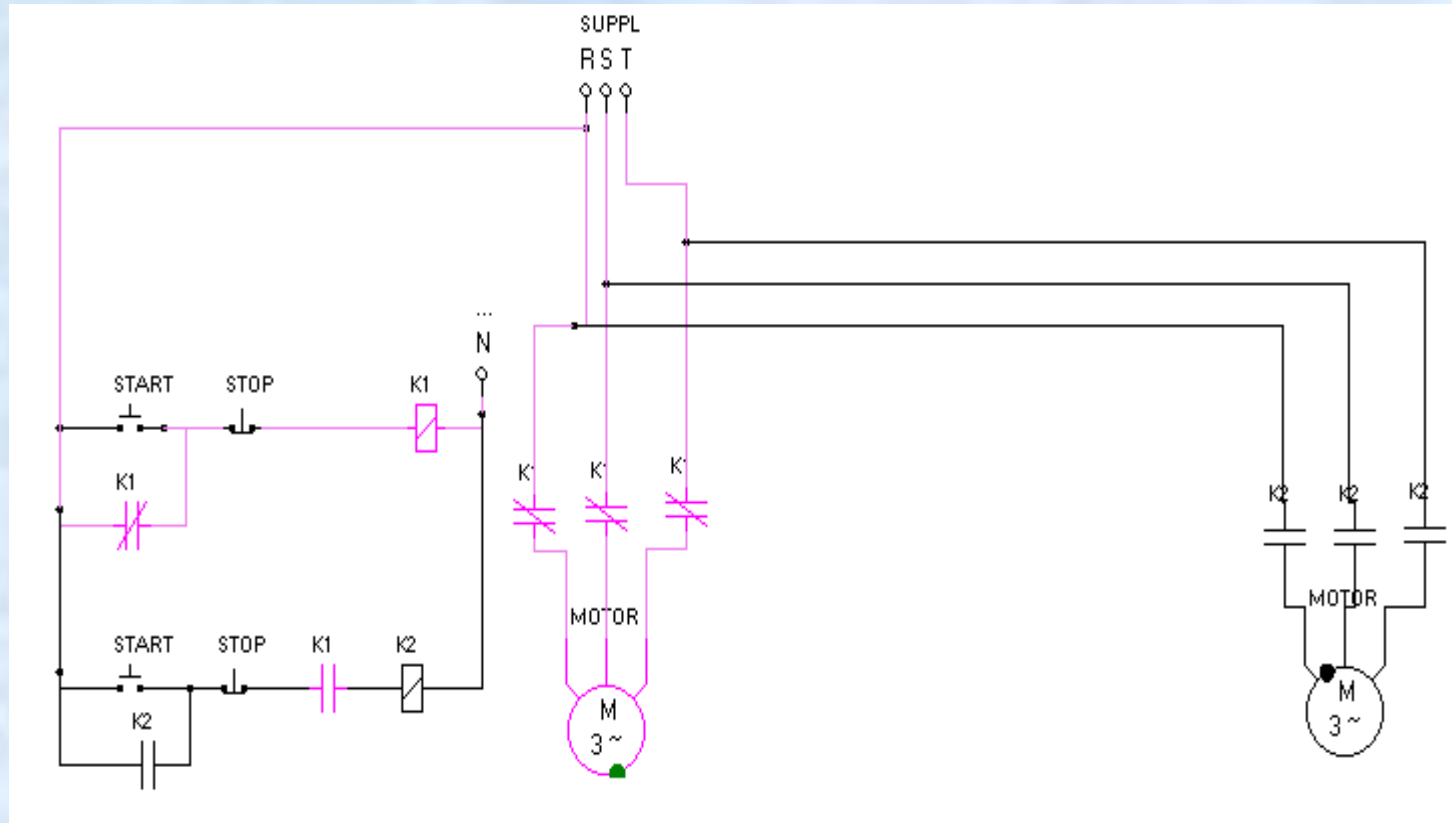



9- Sequence of conveyors motor circuit

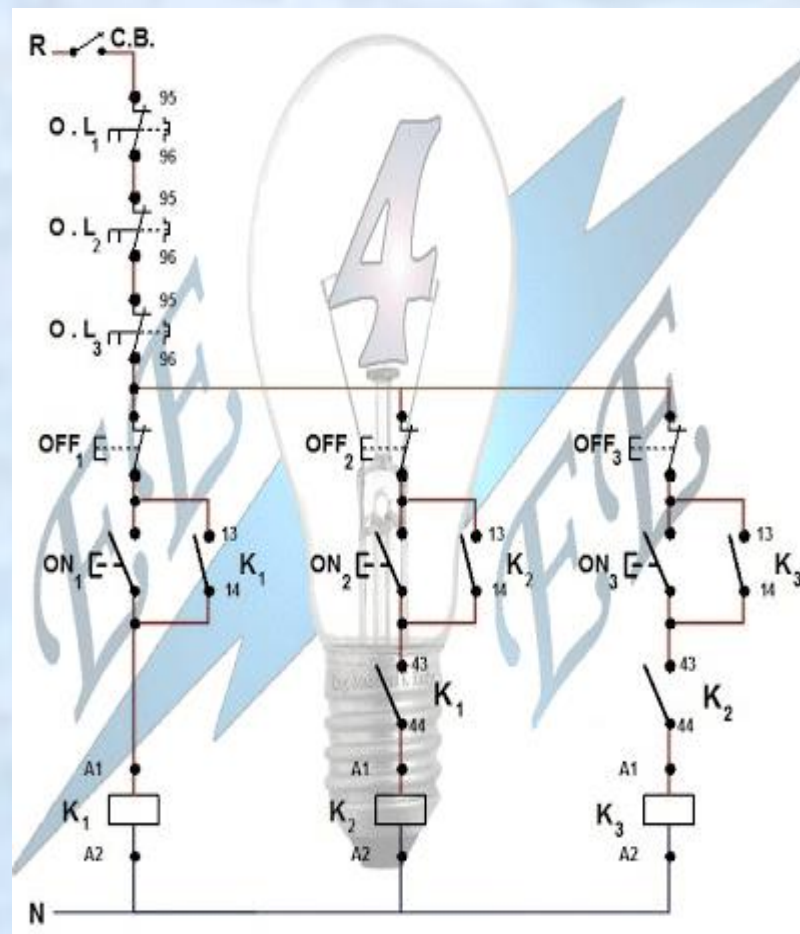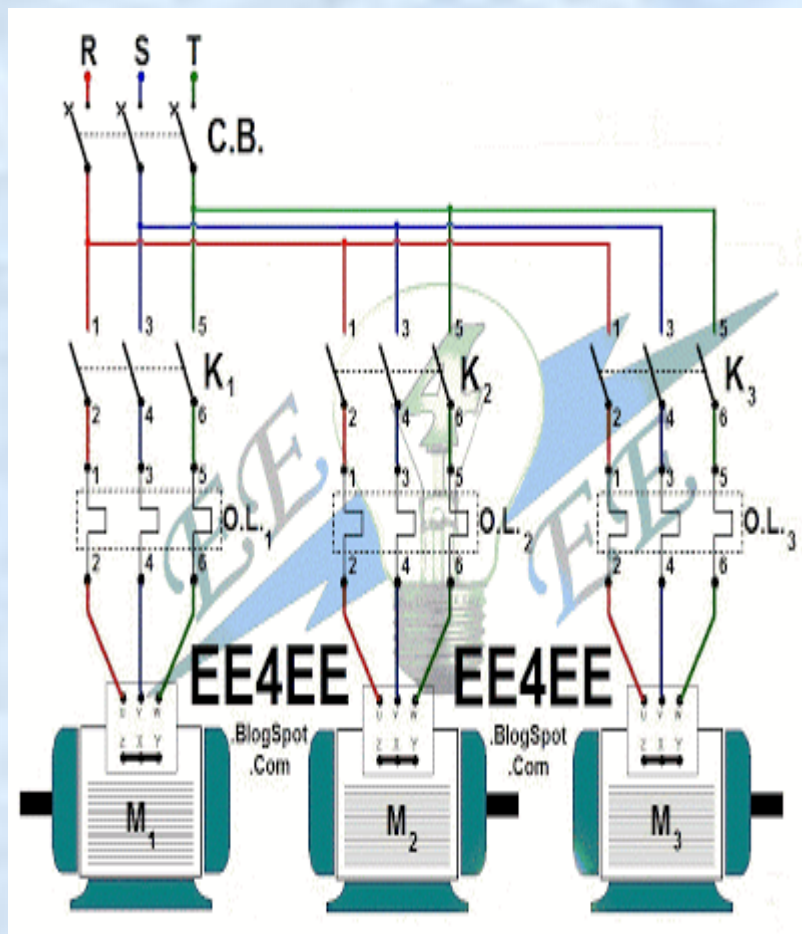


EKTS Simulation

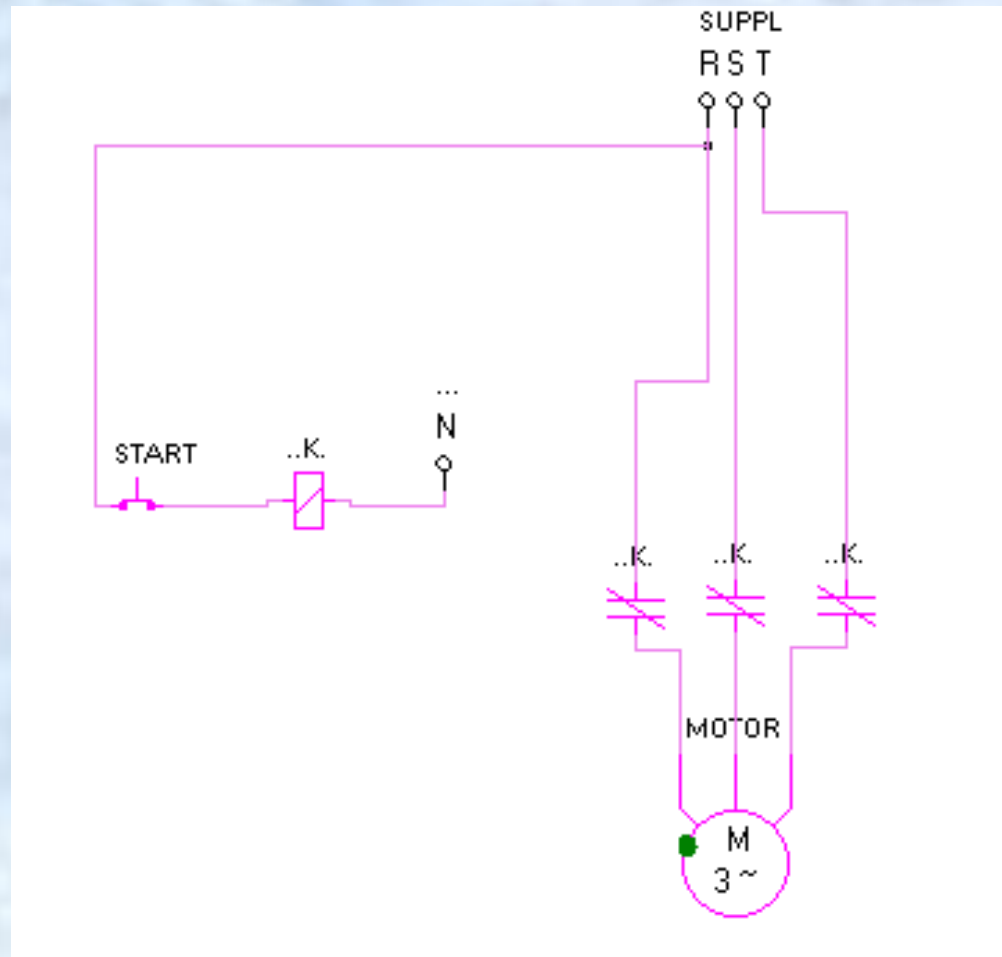

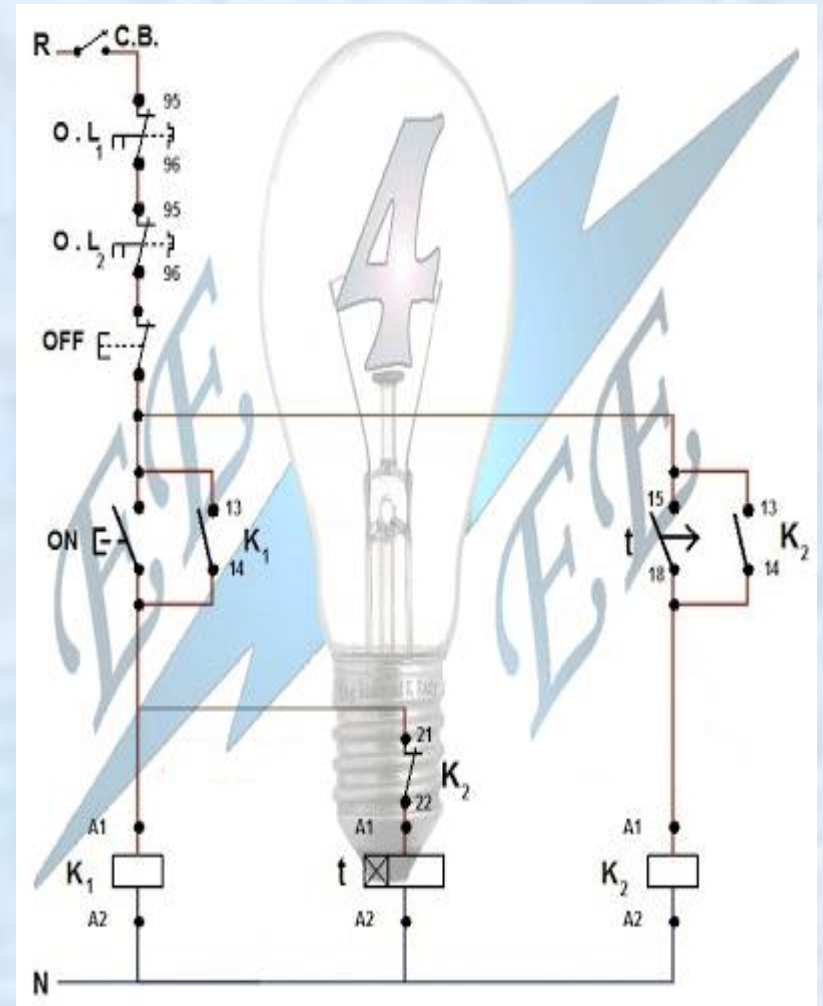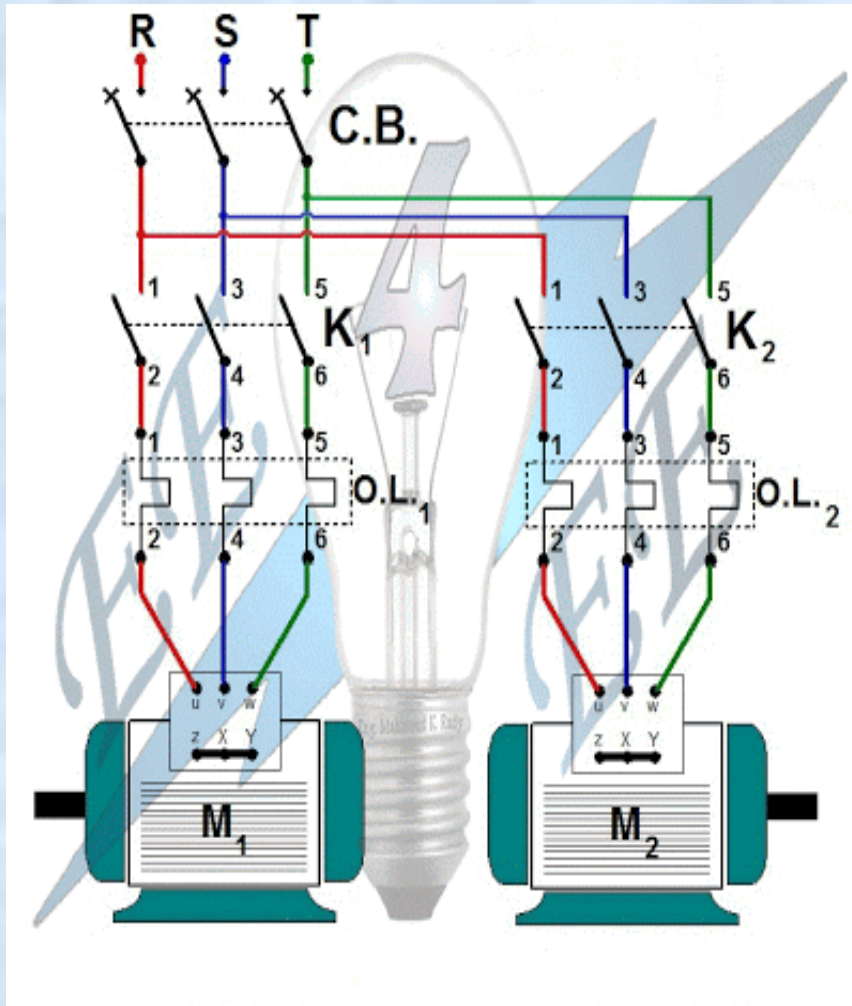
10- Automatic control with time delay motor circuit





EKTS Simulation

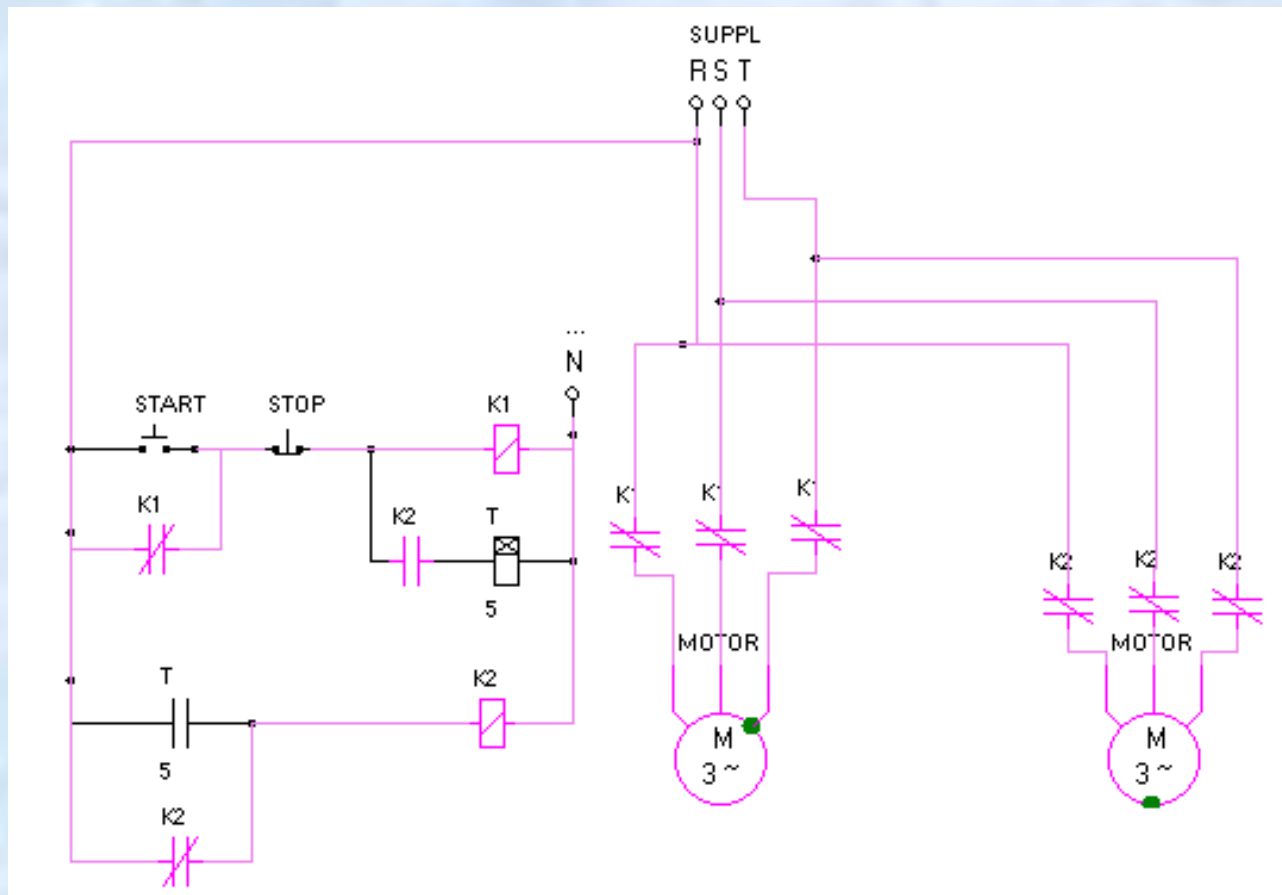

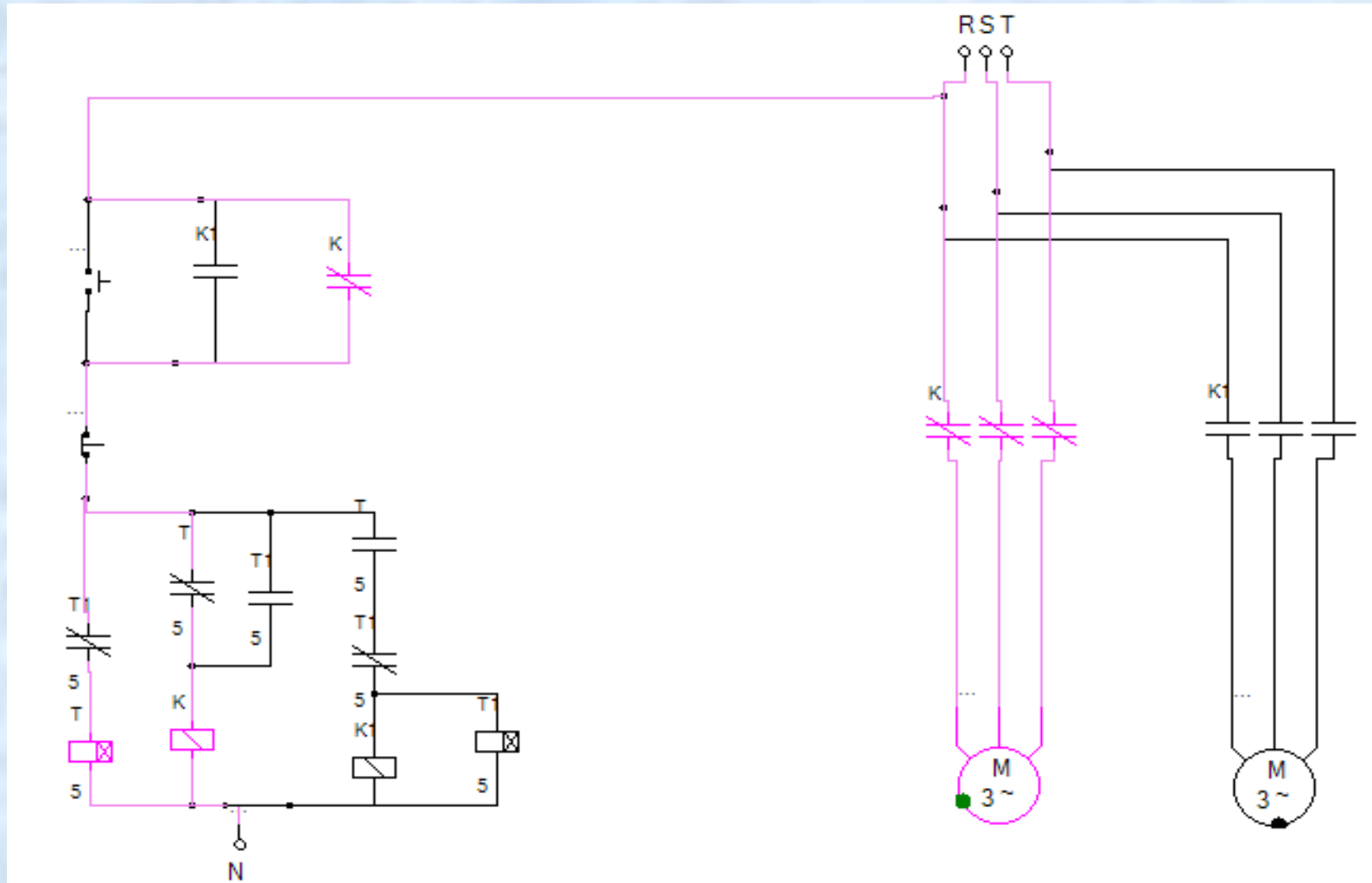
11- Automatic control of two motor with time delay motor circuit




12- Forward Reverse motor circuit

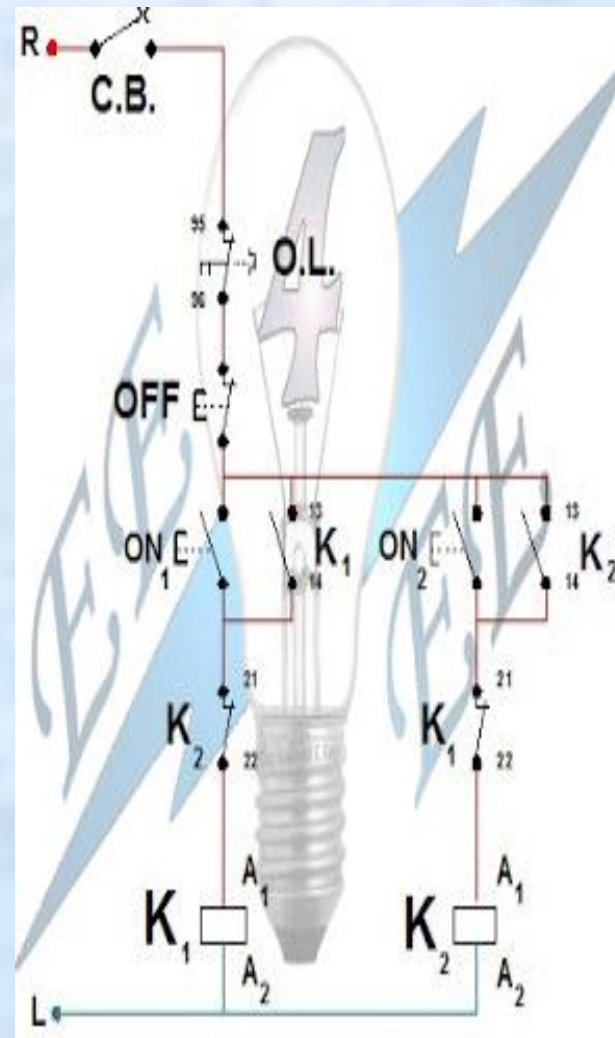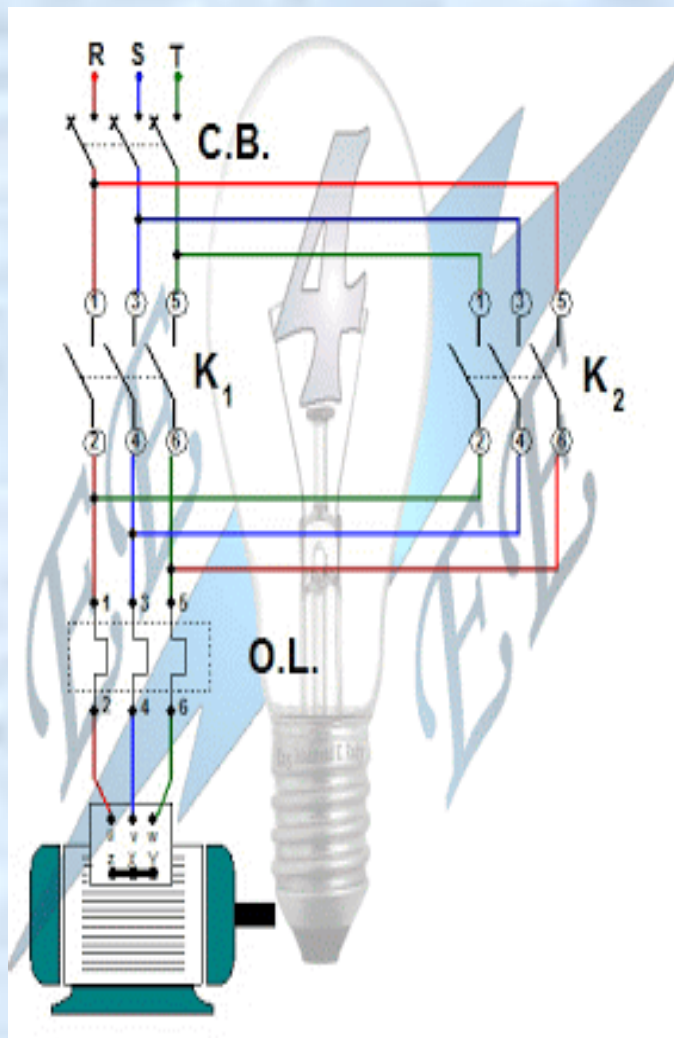


EKTS Simulation

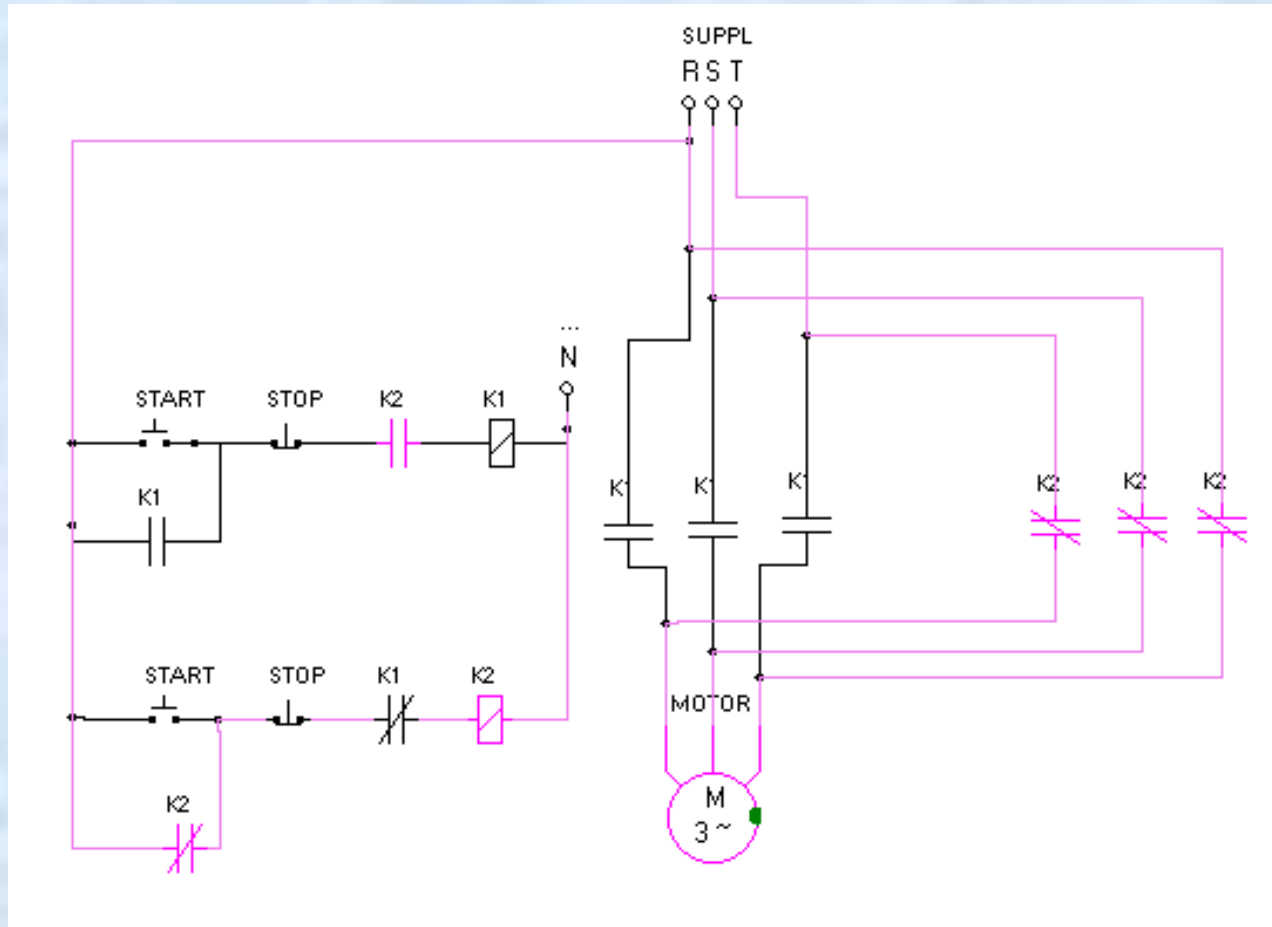

Think what does it mean ????

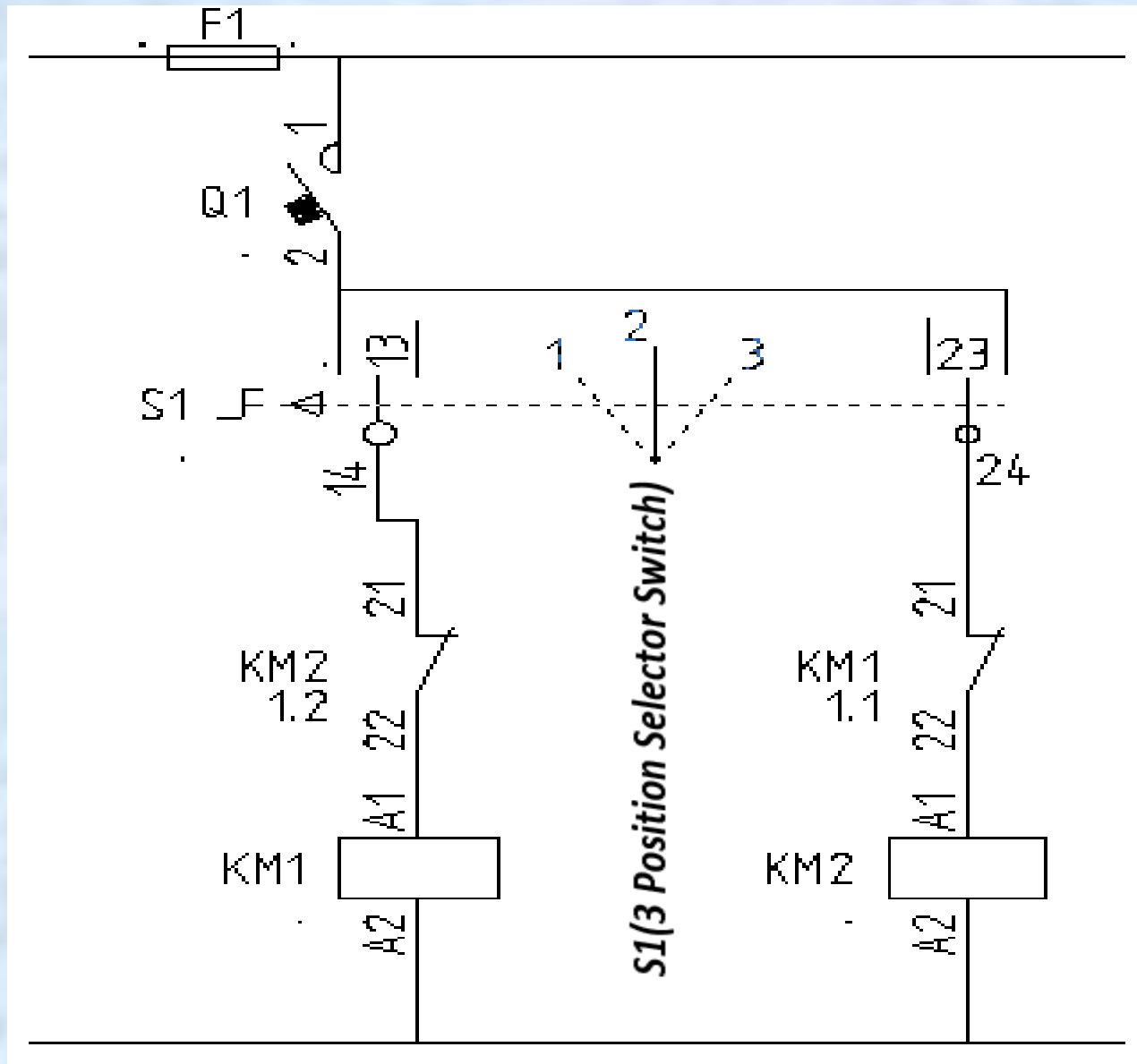

Think what does it mean ????

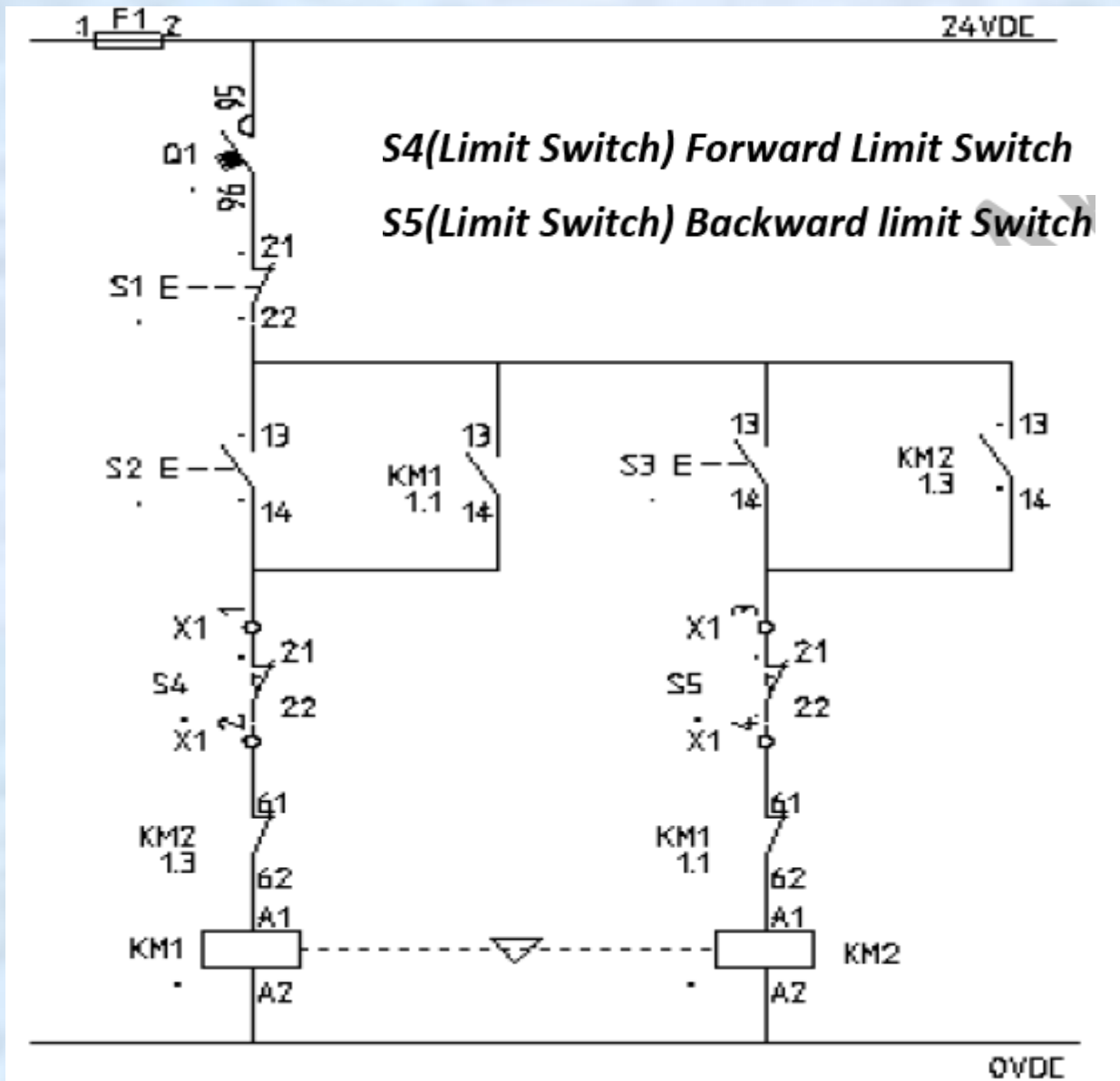

CHAPTER 7


Types of Starter for Induction motors

Function of starter


- ☐ Start and stop the motor.
- ☐ Limit inrush current where necessary.
- ☐ Permit automatic control when required
- ☐ Protect motor and other connected equipments from over voltage, no voltage, under voltage, single phasing etc.

Types of 1 Φ I.M starter

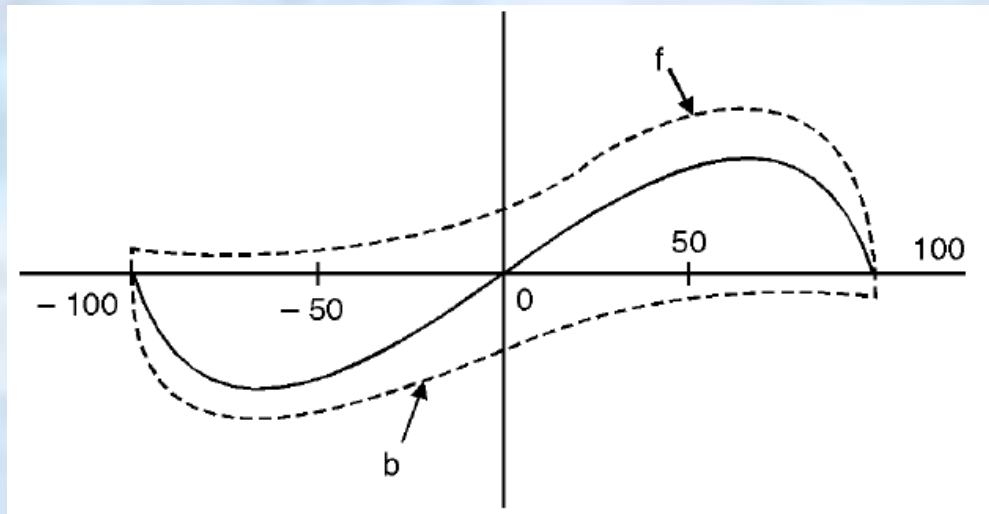- ☐ Split-phase induction motor.
- ☐ Capacitor start induction motor.
- ☐ Capacitor run induction motor.
- ☐ Capacitor start capacitor run motor.
- ☐ Shaded pole induction motor.




1- Split-phase induction motor

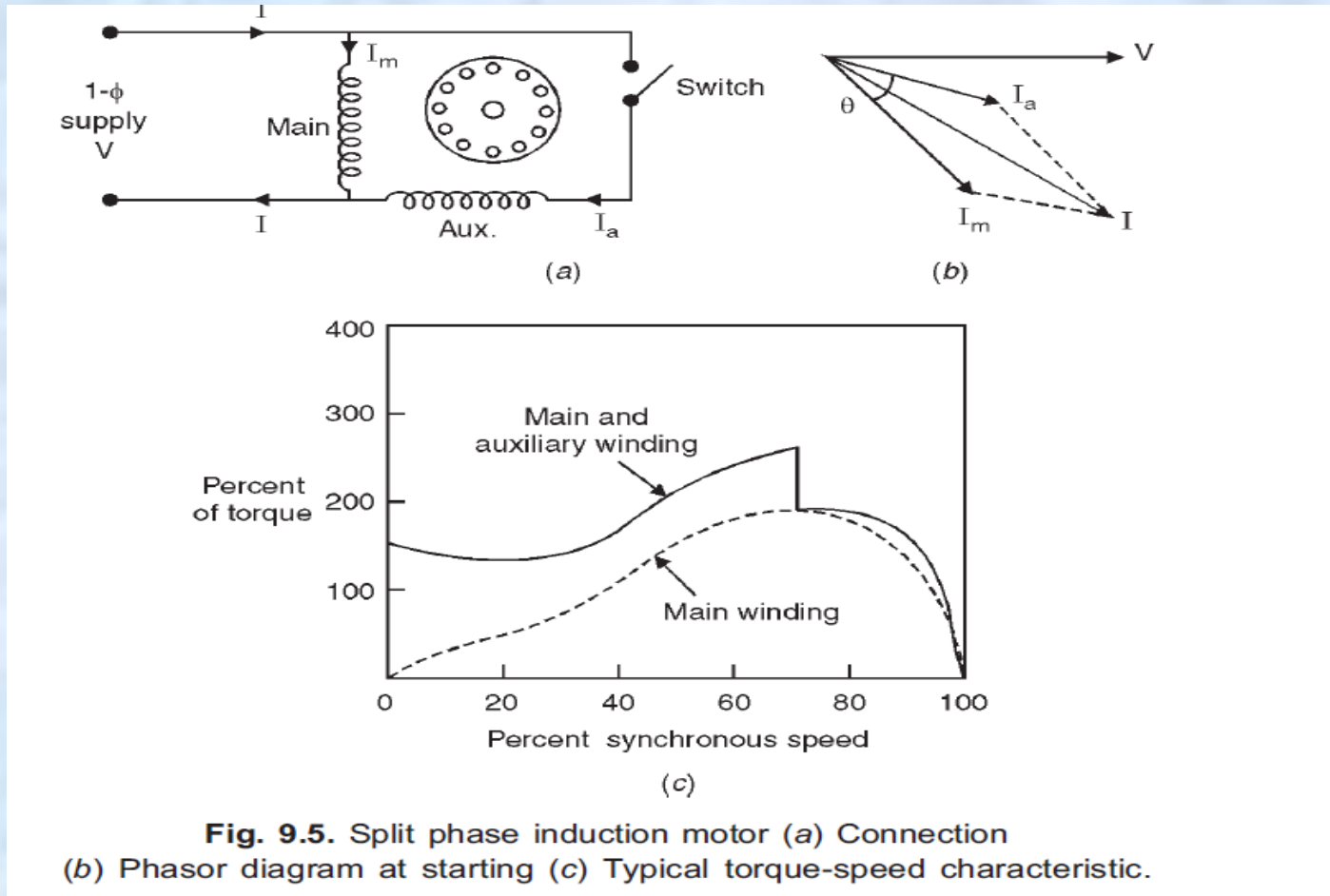


The split phase induction motors are used for fans, blowers, centrifugal pumps and office equipment.

Centrifugal Switch

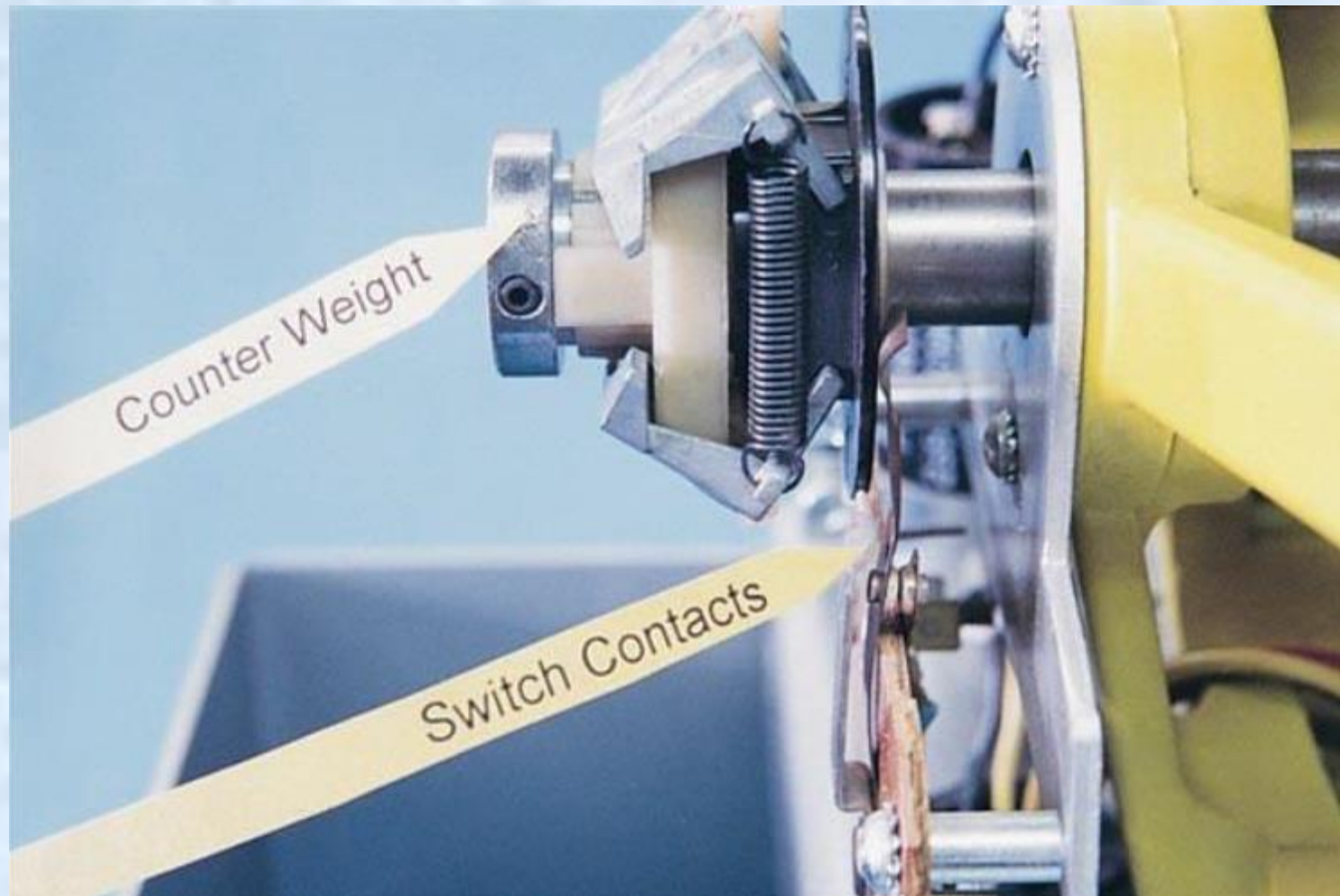


2- Capacitor start induction motor

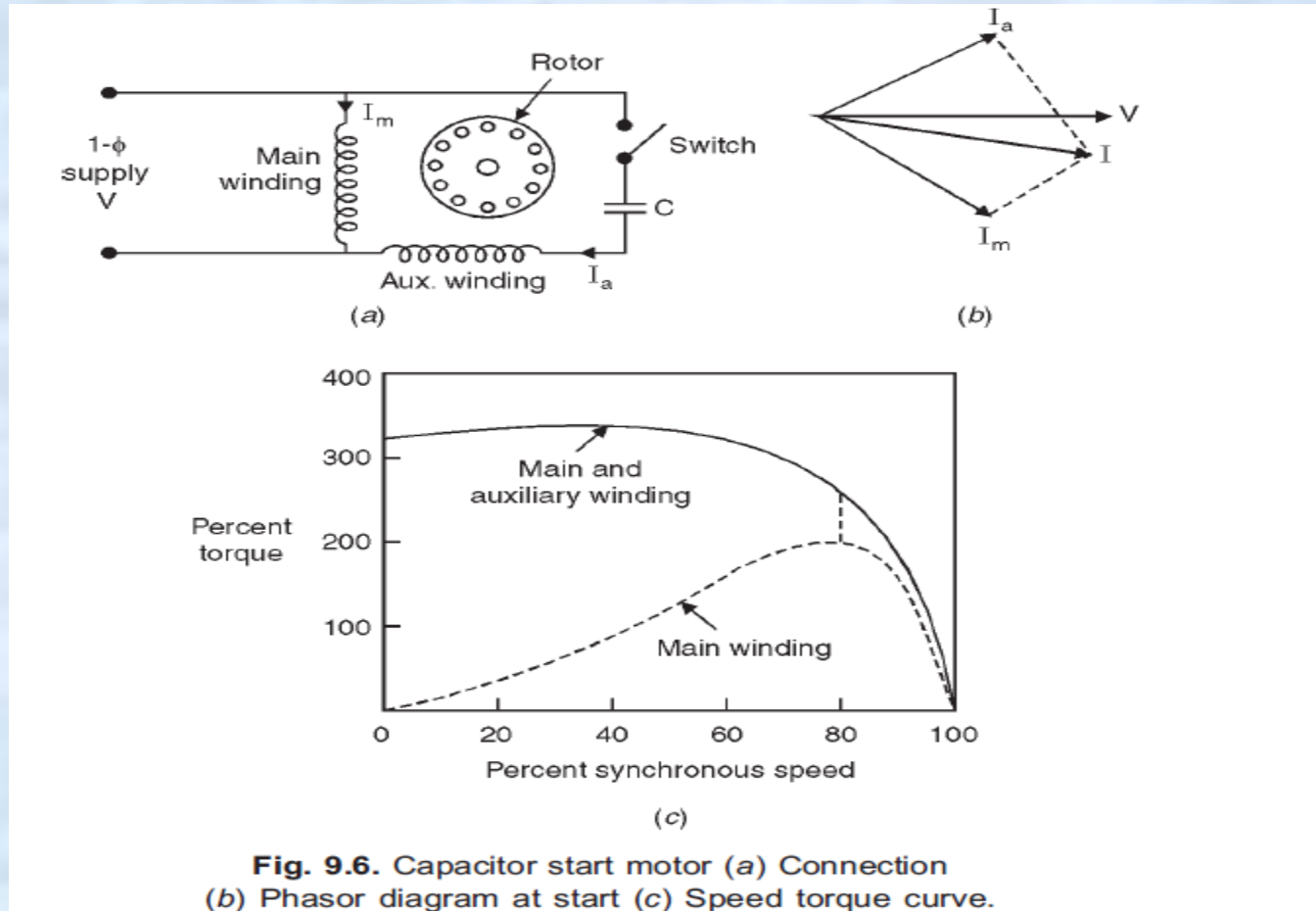


The capacitor start motors are used for compressors, pumps, refrigeration and air-conditioning equipment and other hard to start-loads (**25 μ F/HP**).

3- Capacitor run induction motor

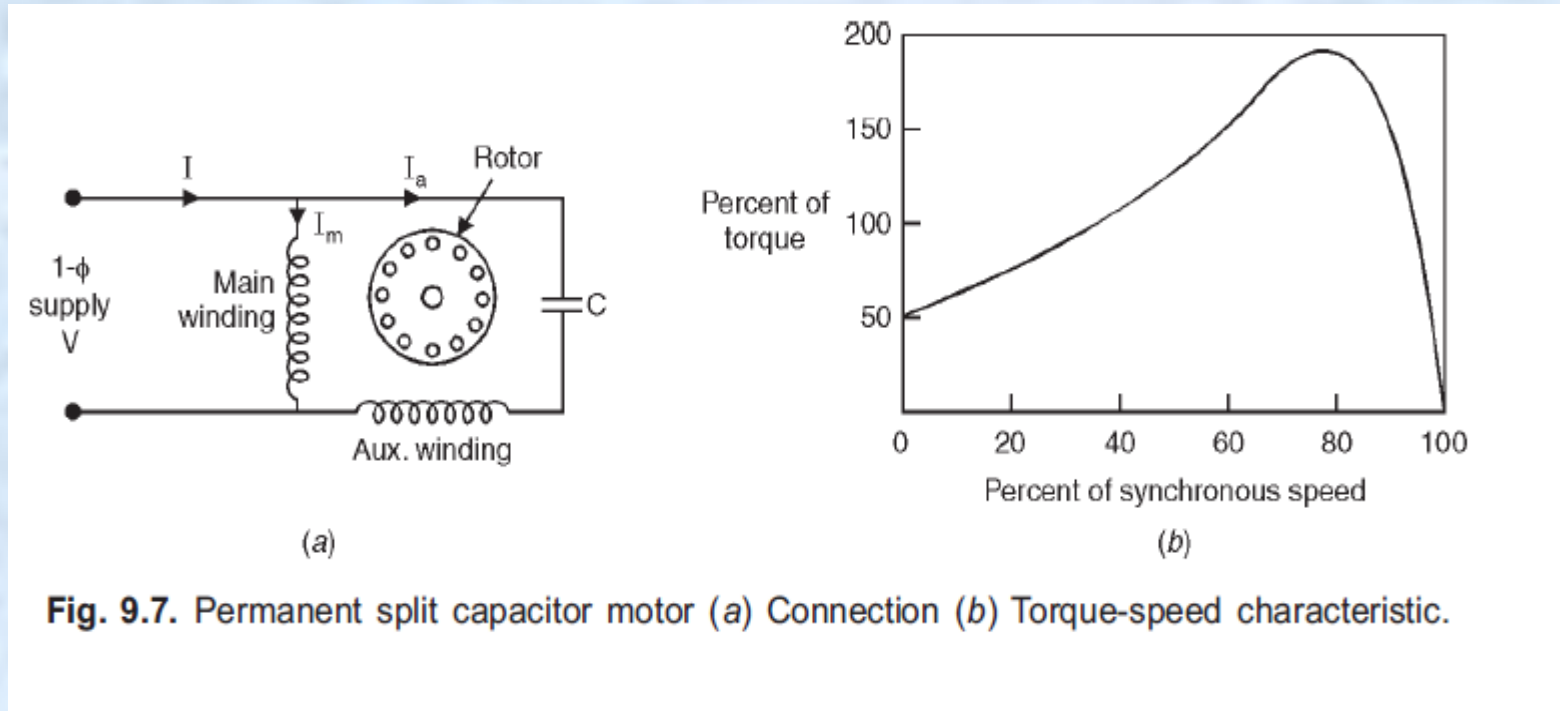

The capacitor run induction motors are used for direct connected fans, blowers, centrifugal pumps and loads requiring low starting torque **(1.5 to 100 μ F)**.

4- Capacitor start capacitor run motor

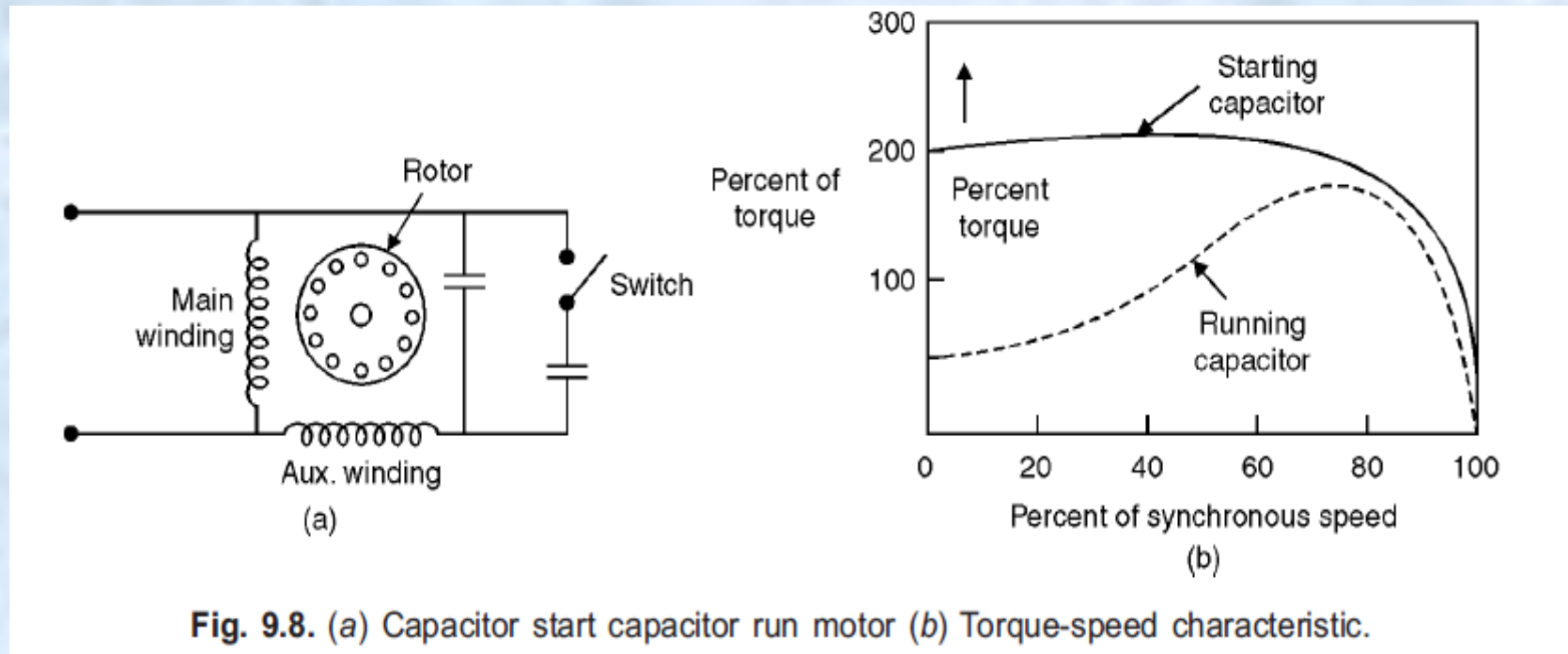

The capacitor start capacitor run motors are used in compressors, conveyors, pumps and other high torque loads.

5- Shaded pole induction motor


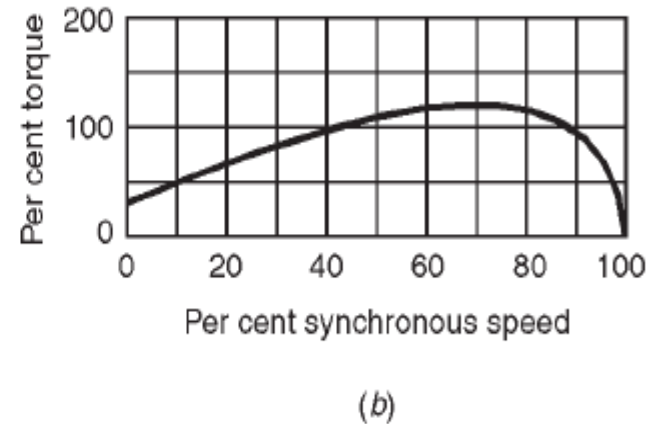
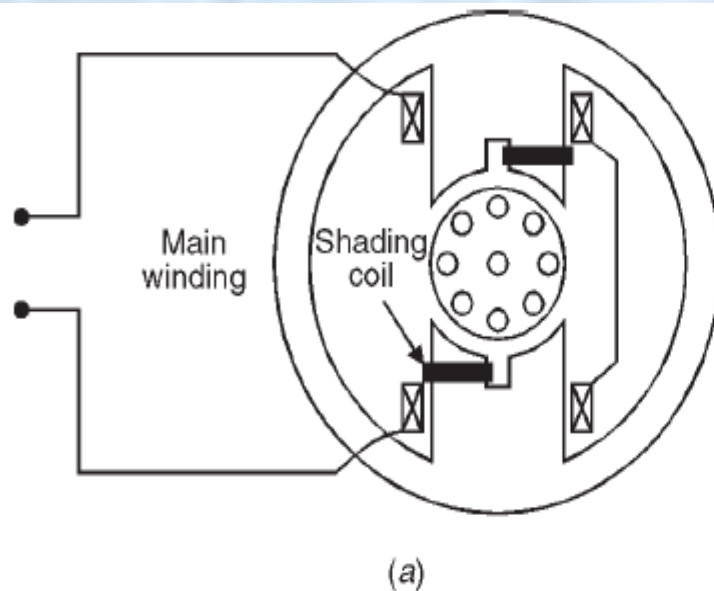
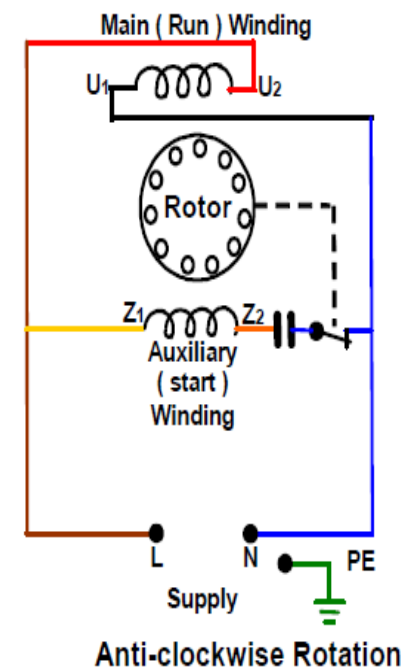
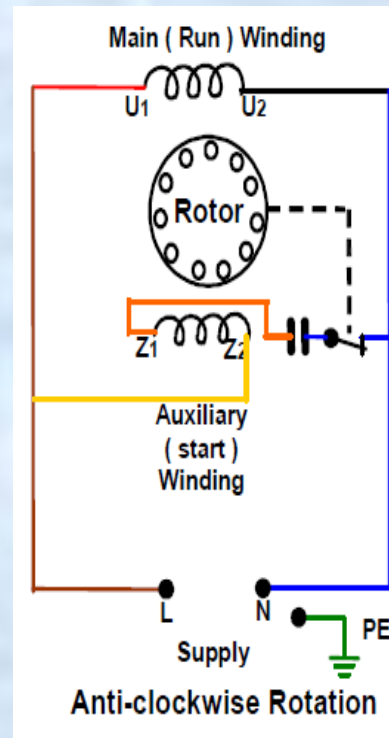


Fig. 9.9. Shaded-pole motor and typical torque-speed characteristic.

The shaded pole motors are used in toys, hair driers, desk fans etc.

Reversing the Direction of Rotation

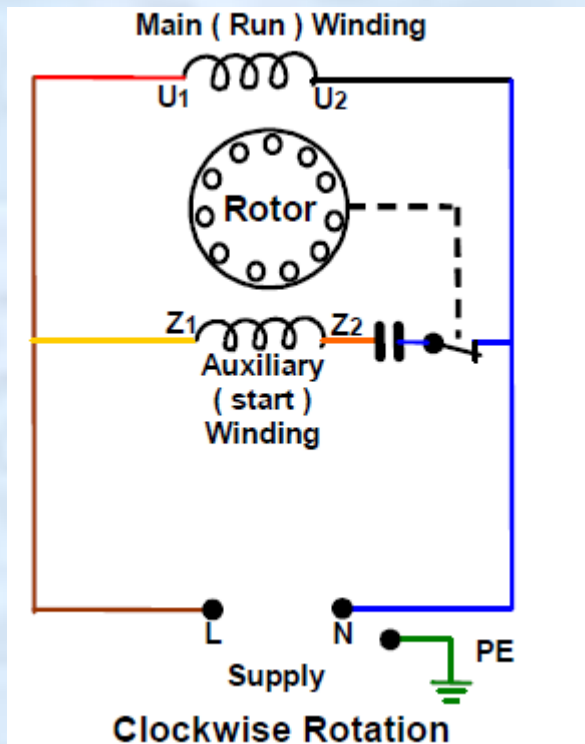- Reversing the direction of rotation can be accomplished by reversing either the run windings or the start windings
- Reversing the start winding connections is more common



Types of 3 Φ I.M starter

➤ For slip-ring induction motors:

- ☐ Rotor rheostat starter


➤ For squirrel cage induction motors:

- ☐ D.O.L starter
- ☐ Primary resistance starter
- ☐ Auto transformer starter
- ☐ Star delta starter

➤ Other starters:



- ☐ Soft starters
- ☐ Variable speed drive

1- Rotor rheostat starter

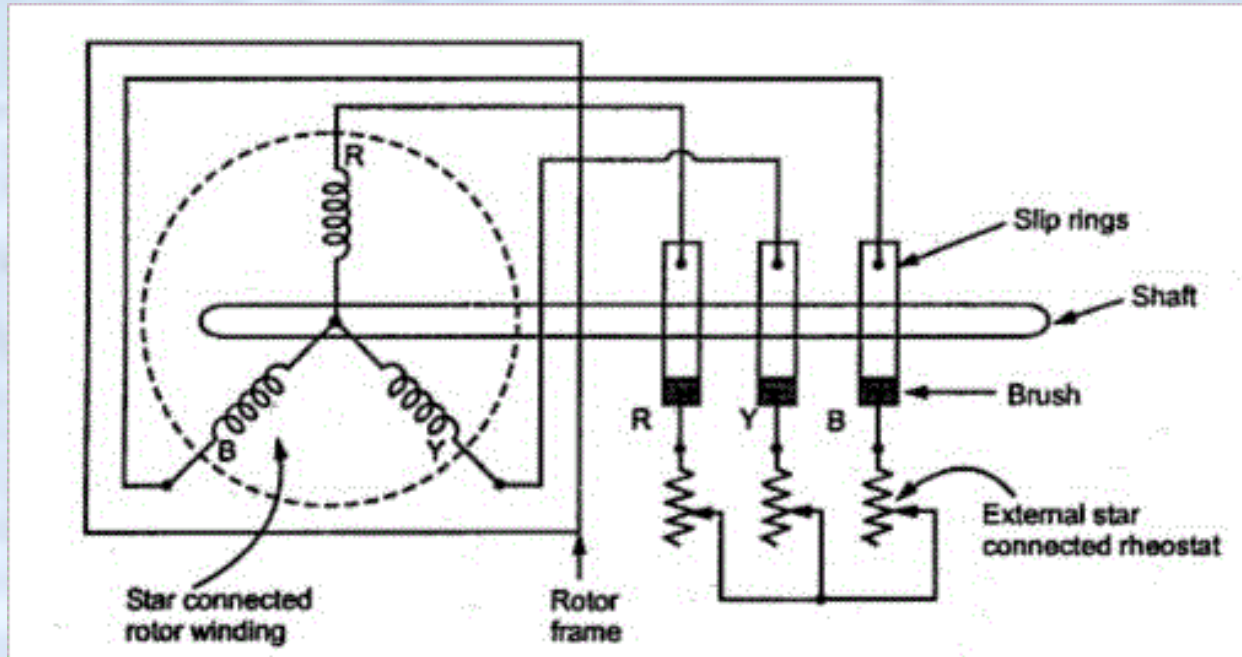


❑ The rotor circuit resistance is gradually cut out , as the motor speeds up and during normal running condition ,the rotor circuit resistance is completely cut out and the slip rings are short circuited (**Starting with high resistance value then decrease gradually T_{max} at $S=R_{ext}/X_2$**)).

2- Direct-on-Line Starter (DOL)

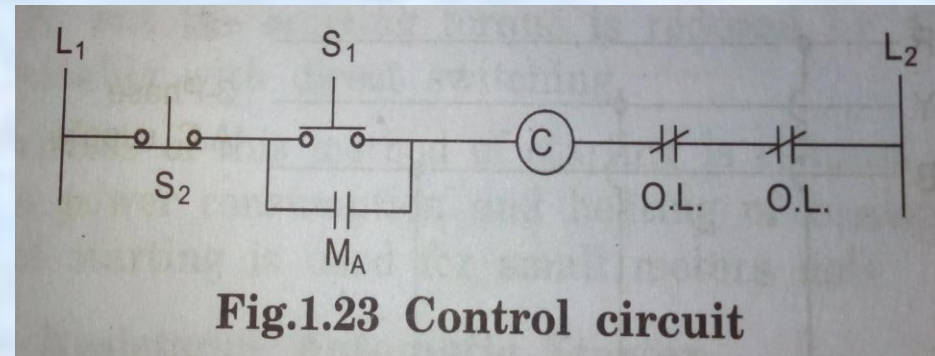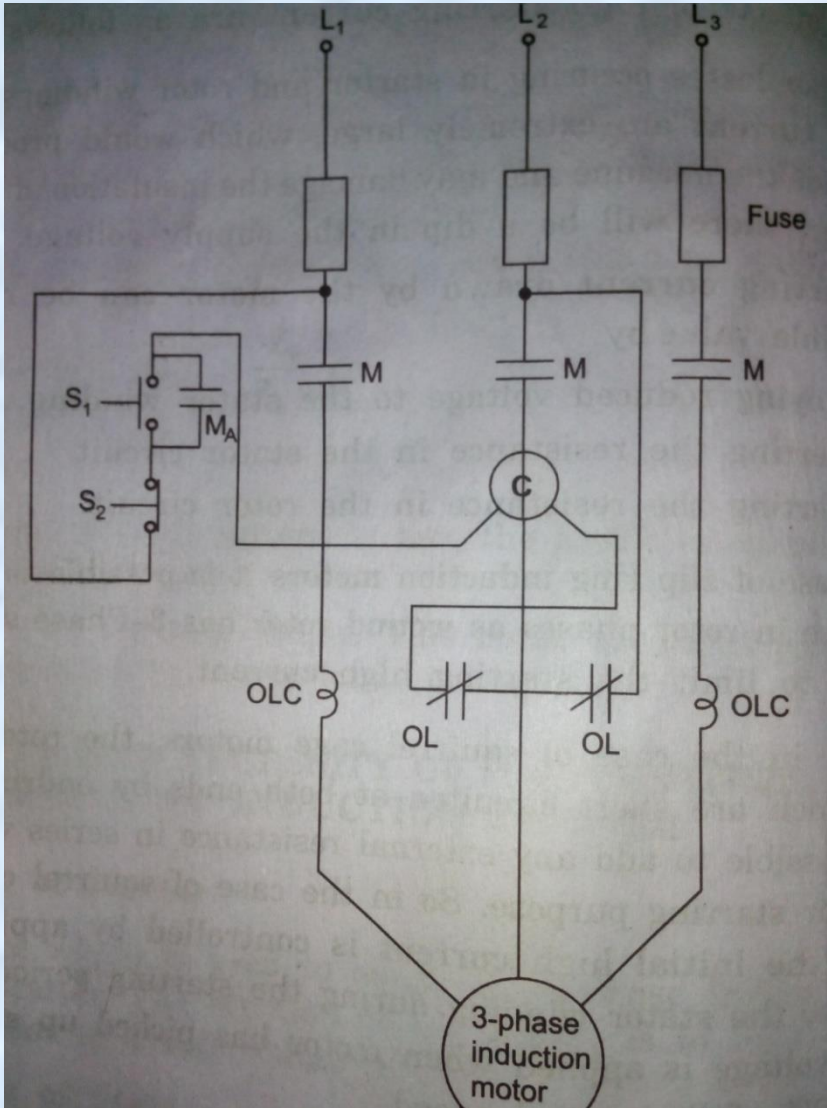


3- Primary resistance starter

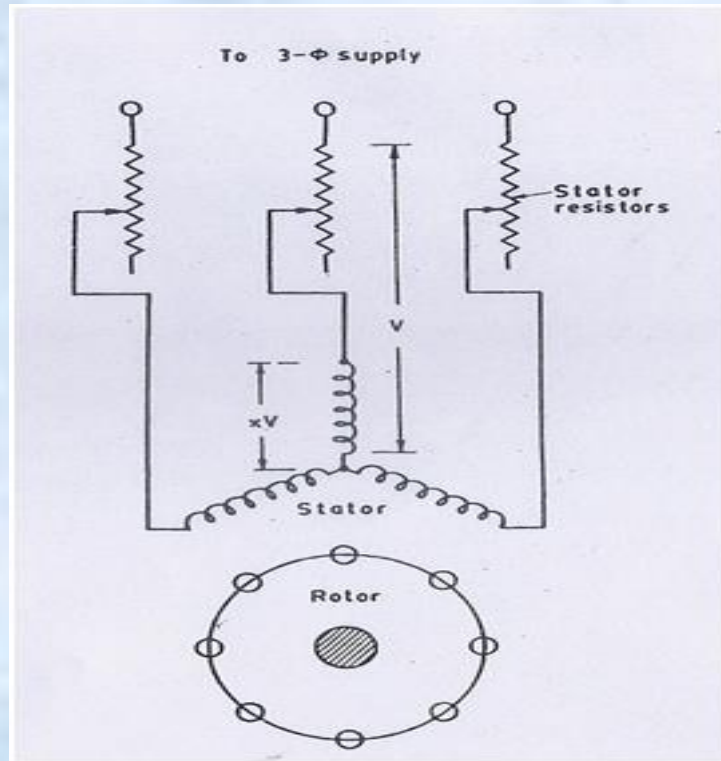




The purpose of primary or starting resistors is to drop some ☐ voltage and hence reduce the voltage applied across the motor terminals.

4- Auto-Transformer Starting

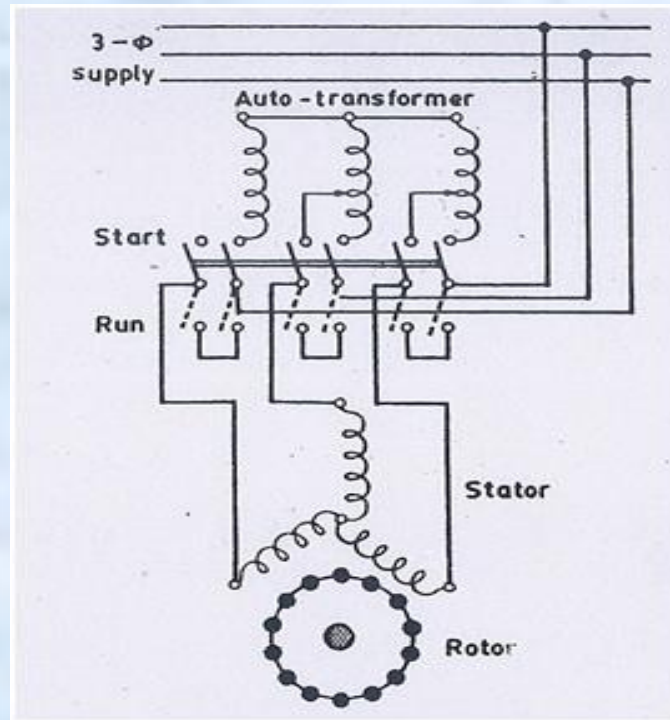


❑ An auto-transformer starter makes it possible to start squirrel-cage induction motors with reduced starting current, as the voltage across the motor is reduced during starting.

5- Star delta starting

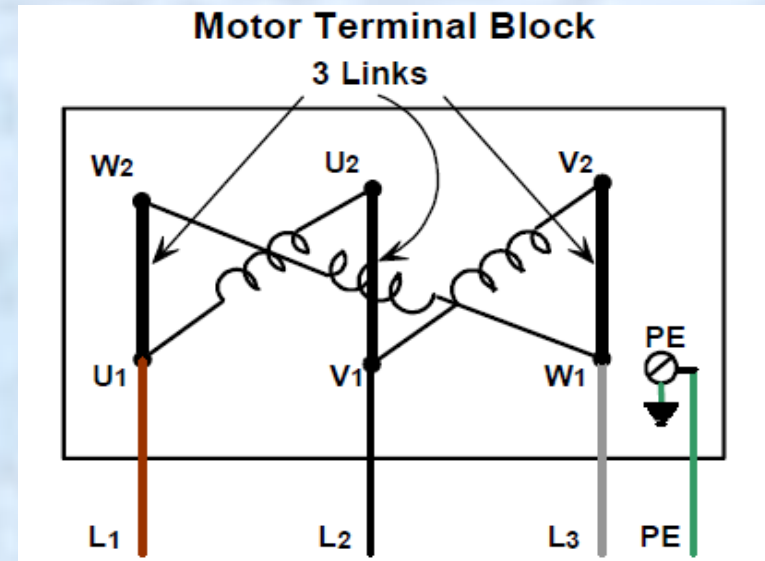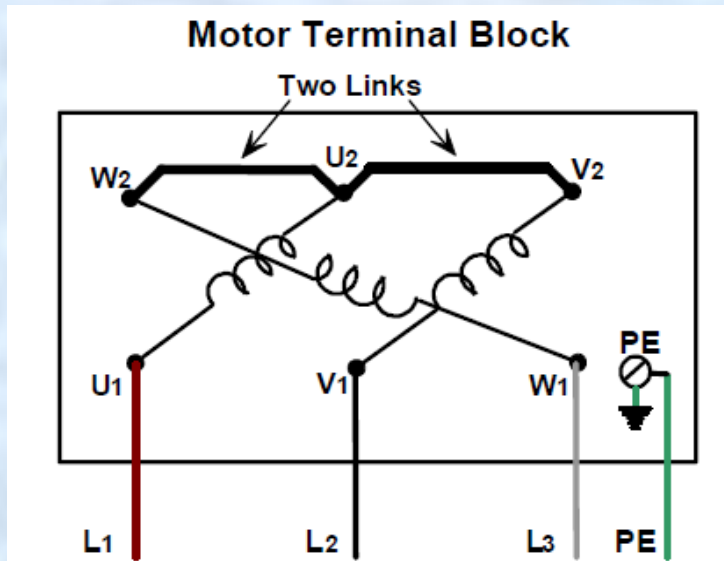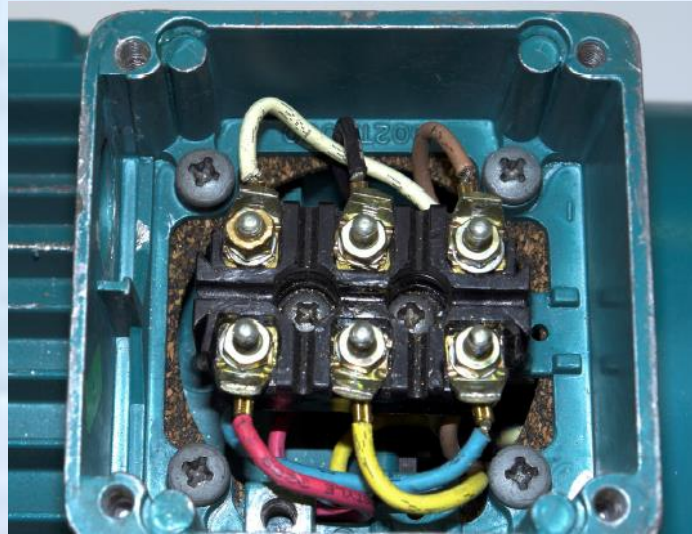


➤ Power circuit

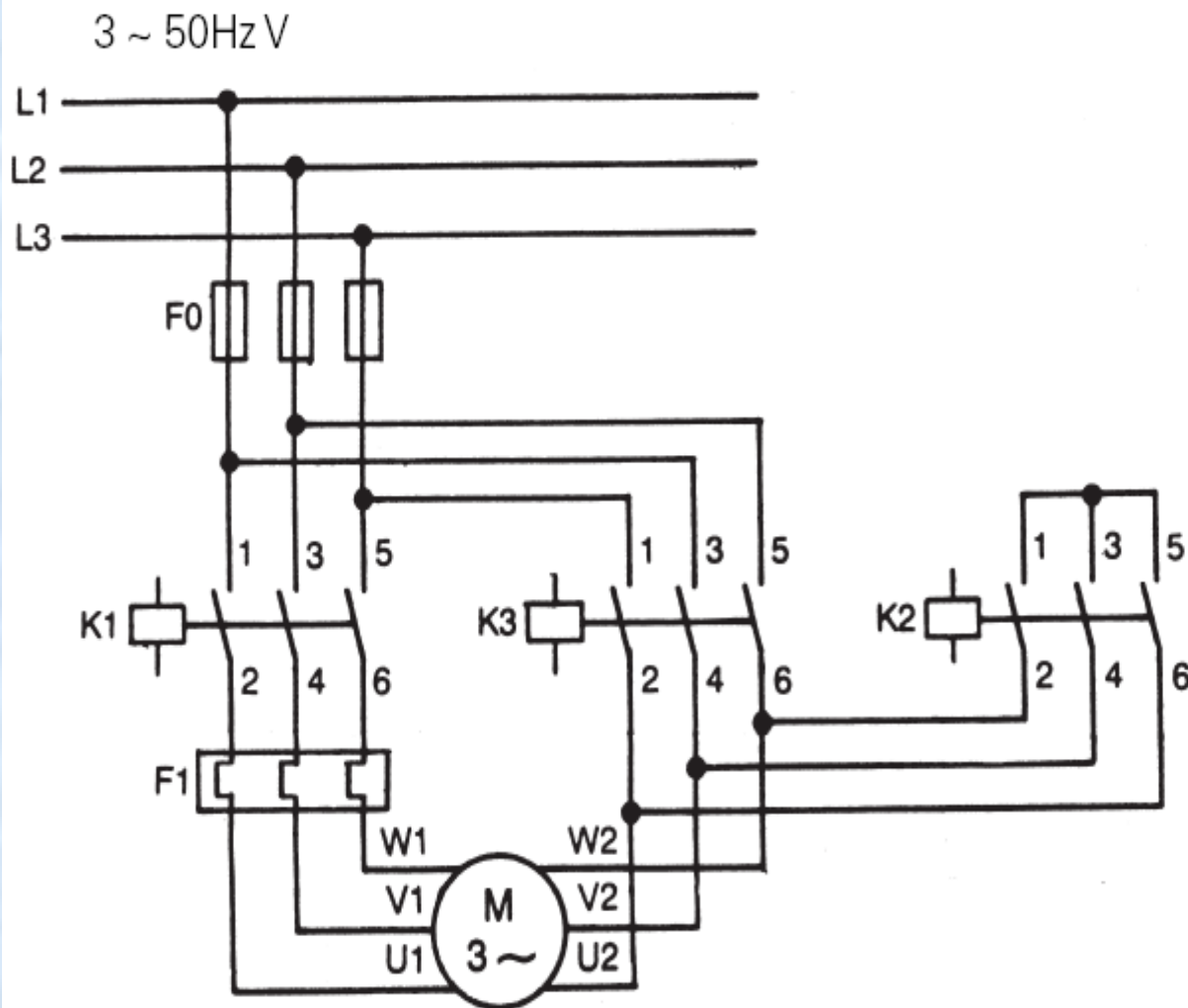

K1 = Line Contactor
K2 = Star Contactor
K3 = Delta Contactor
F1 = Overload Relay
F0 = Backup Fuse

➤ Control circuit

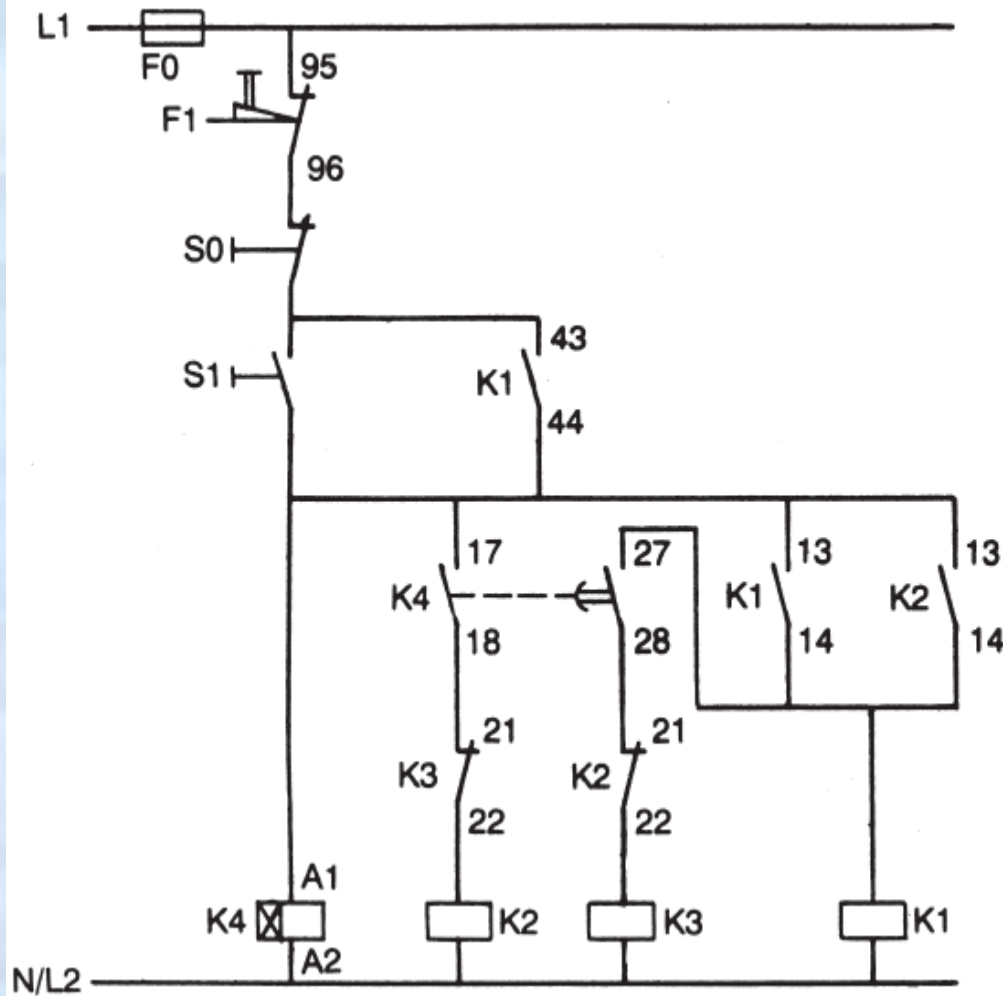


- S0 = Push Button OFF (1NC)
- S1 = Push Button ON (1NO)
- K1 = Line Contactor with 2NO Auxiliary Contacts.
- K2 = Star Contactor with 1NO + 1NC Auxiliary Contacts.
- K3 = Delta Contactor with 1 NC Auxiliary Contacts.
- K4 = Star Delta Timer with 1NO instantaneous and 1NO delayed Auxiliary Contacts.
- F1 = Overload Relay.
- F0 = Backup Fuse.

Difference between DOL/Star delta /Autotransformer

Sr.	DOL Starter	Star delta starter	Auto transformer starter
1	Used up to 5 HP	Used 5 HP to 20HP	Used above 20 HP
2	Does not decrease the starting current	Decreases the starting current by $\frac{1}{3}$ times	Decreases the starting current as required
3	It is cheap	It is costly	It is more costly
4	It connects directly the motor with supply for starting as well as for running	It connects the motor first in star at the time of starting in delta for running	It connects the motor according to the tapping taken out from the auto transformer

6- Soft starter starting

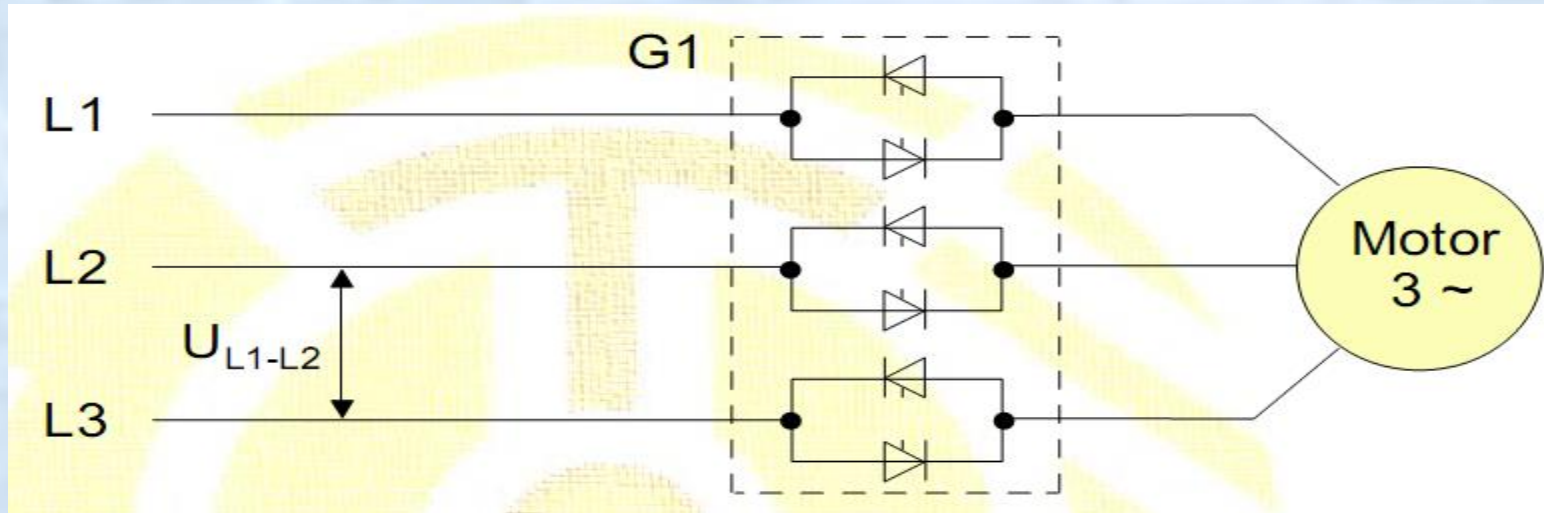


By using six SCR's in a back to back configuration , the soft starter is able to regulate the voltage applied to the motor during starting from 0 volts up to line voltage.


- ❑ **Frequency do not change as in VSD**
- ❑ **Only the voltage and current changes**

The graphics show the basic differences between direct, star-delta and soft starters with regard to motor voltage (U), motor current (I) and motor torque (T).


Motor voltage

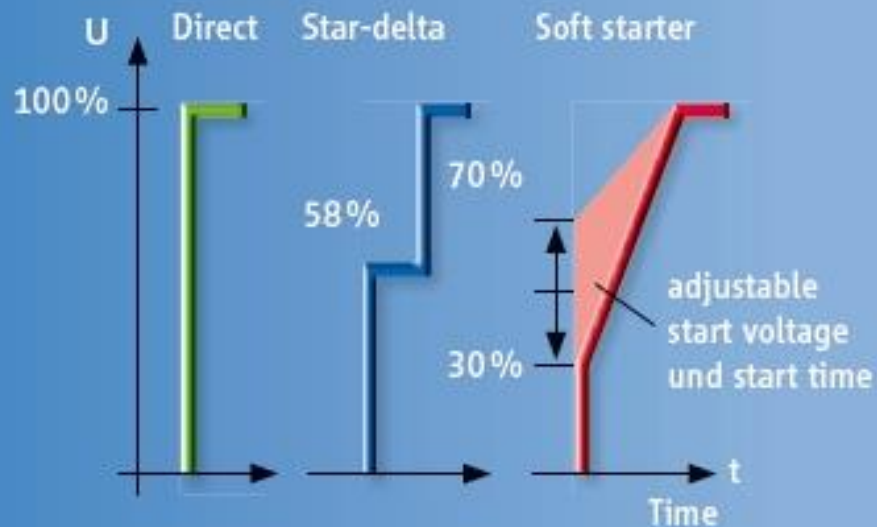



Motor current

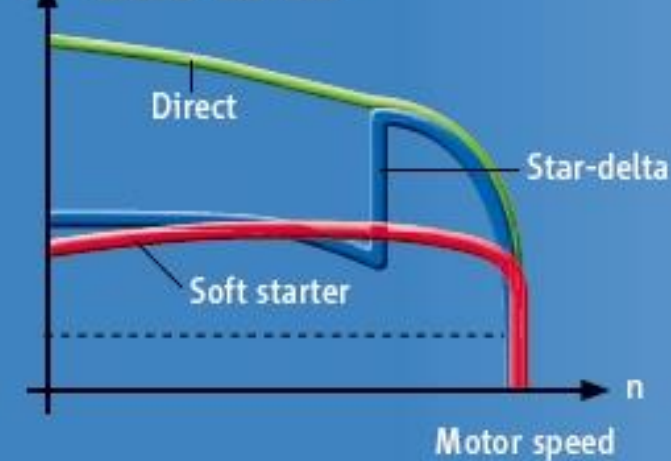

Torque

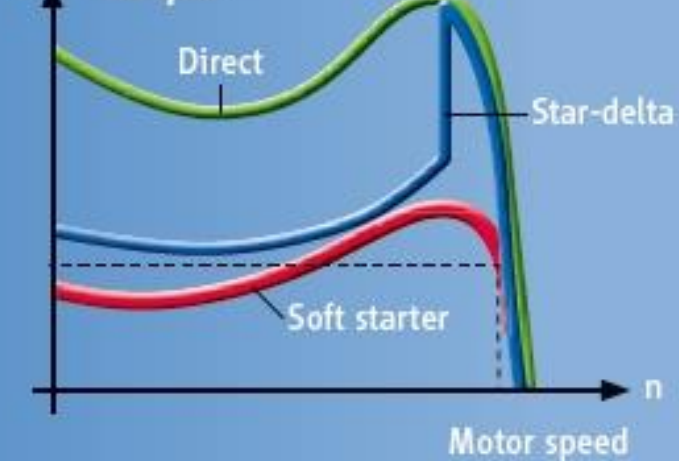

7- Variable speed drive

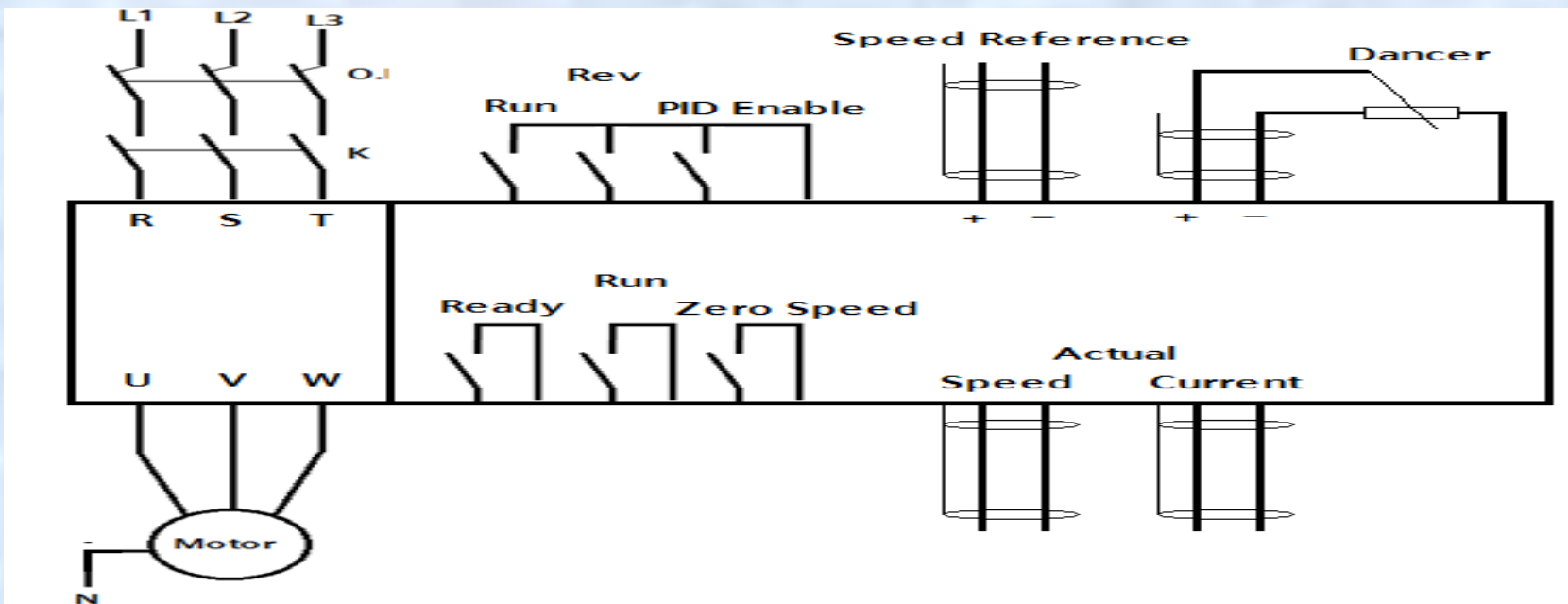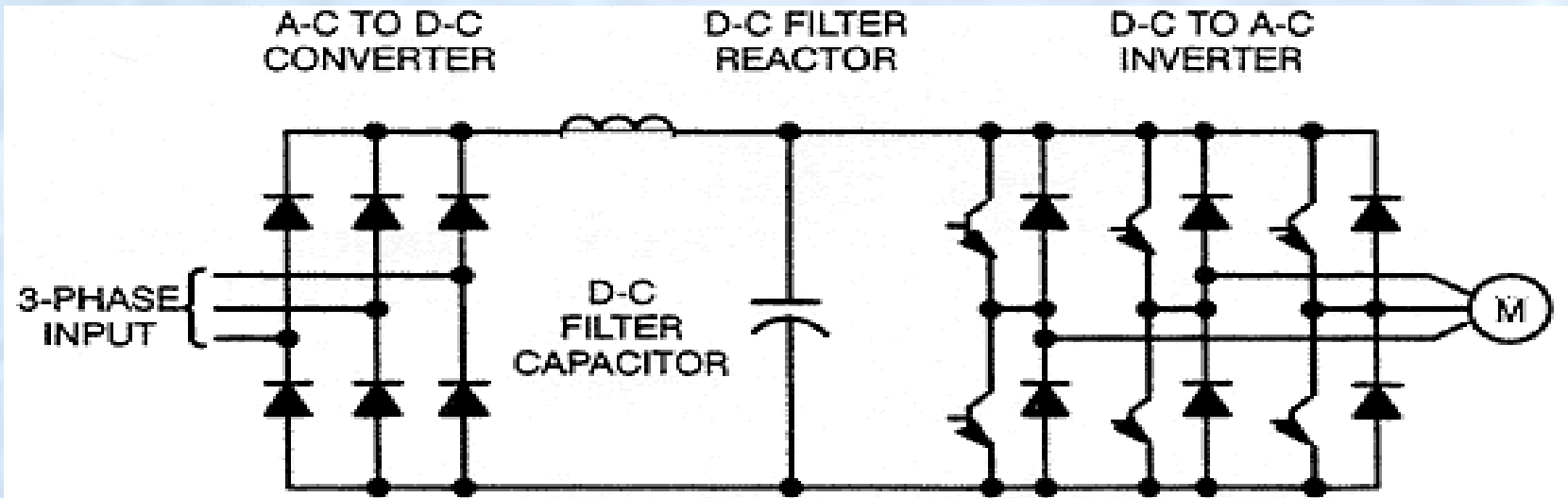

CHAPTER 8

Testing of Induction Motor

Testing of Induction Motor

Visual Tests

- Check that motor frame is mechanically sound.
- Remove terminal cover plate and check for ingress of foreign material, moisture etc.
- Check for signs of overheating, arcing or burning.
- Check ventilation is clear.

Electrical Tests

- Identify windings using a continuity tester.
- Measure the resistance of the windings (3 identical readings).
- Measure the insulation resistance between each winding and between windings and frame.

Mechanical Tests

- Check that the rotor is free to rotate and does so smoothly / quietly.
- Check that motor interior is free of dirt, dust, water and oil.
- Check for play in bearings.


Tests when Running

- Check run currents (If uneven check voltage at motor terminals).
- Check speed of motor at no load and full load.
- Check vibration levels and noise levels.
- Check for temperature hot spots.


Testing of Three-Phase Stator Windings

- **Step 1:** Isolate the motor electrically, and if necessary, mechanically.
- **Step 2:** Identify the way the motor terminal block is connected.
- **Step 3:** Identify the 3 stator windings - usually labelled U1-U2, V1-V2, and W1-W2.
- **Step 4:** Measure and record the resistance of each winding.


Resistance Test on Winding U

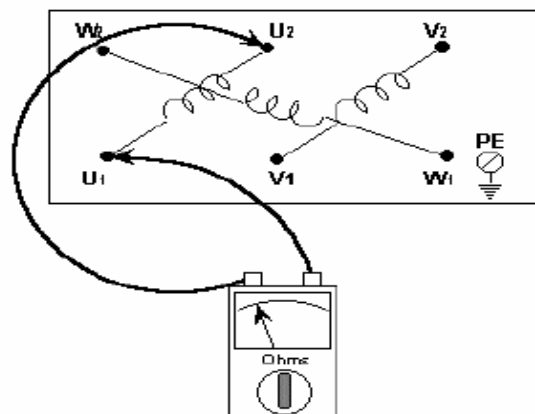


Resistance Test on Winding V

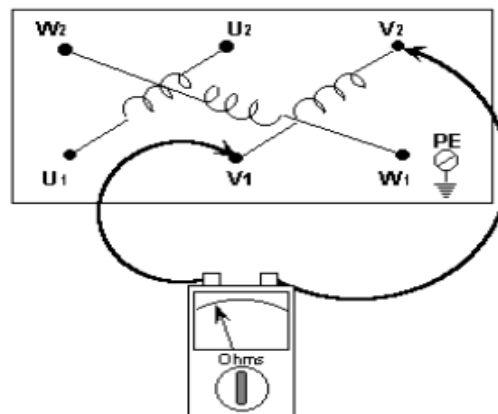


Resistance Test on Winding W

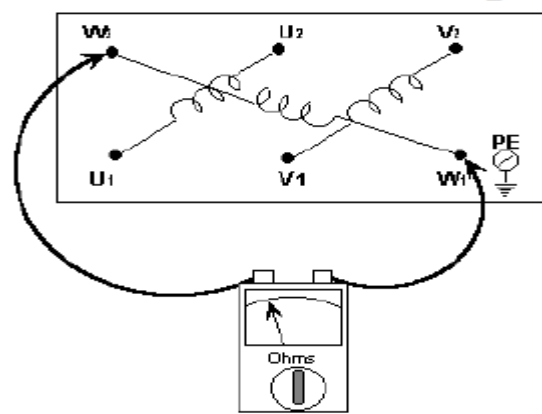





Metallic Frame of Motor

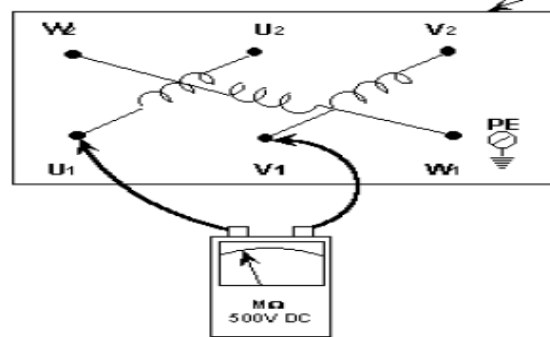

Metallic Frame of Motor





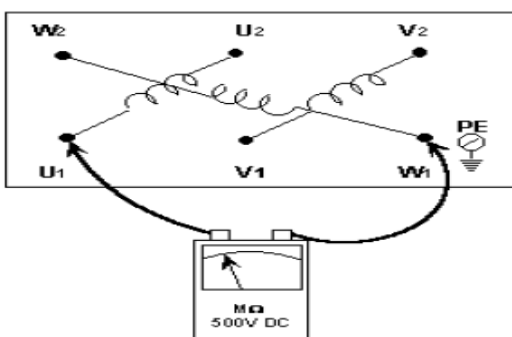


Metallic Frame of Motor

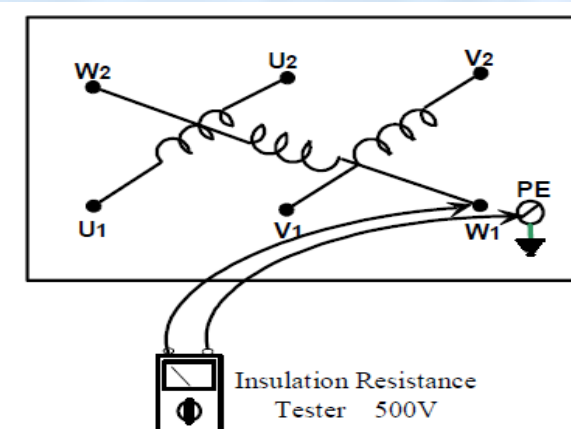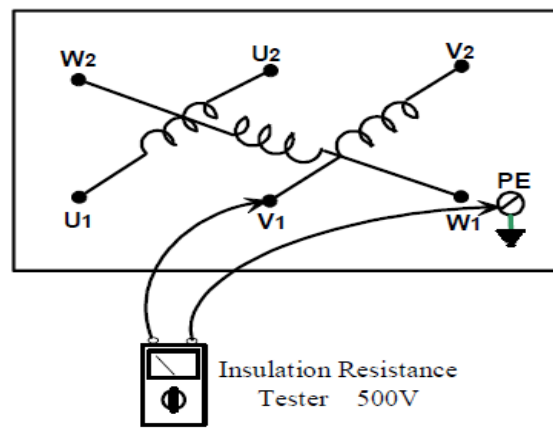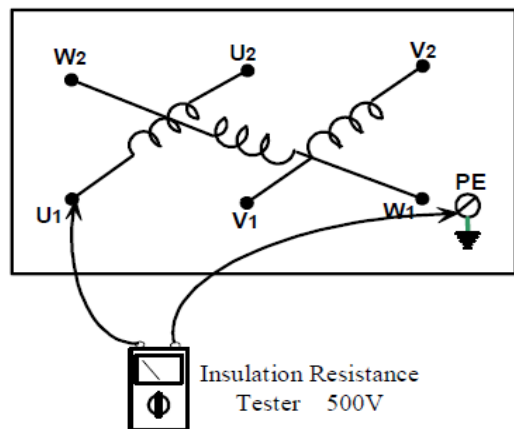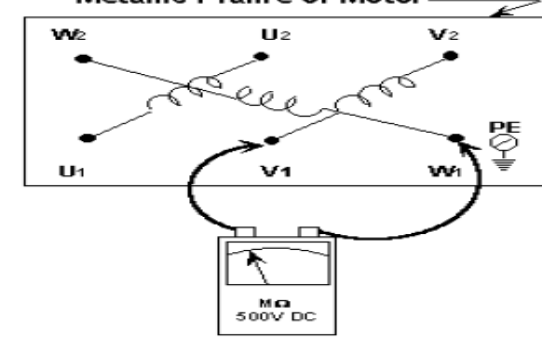


Testing of Single Phase Stator Windings

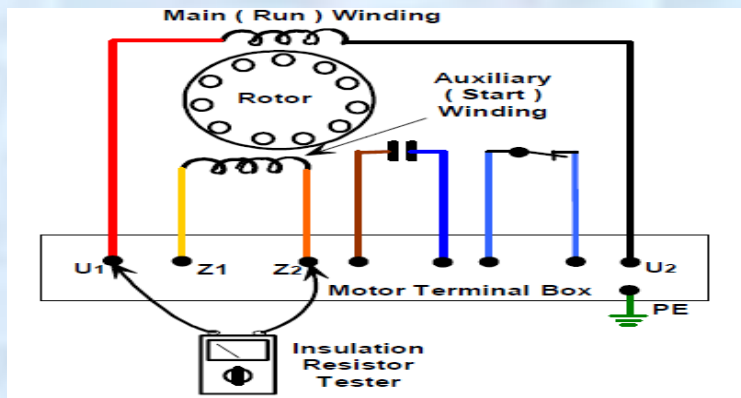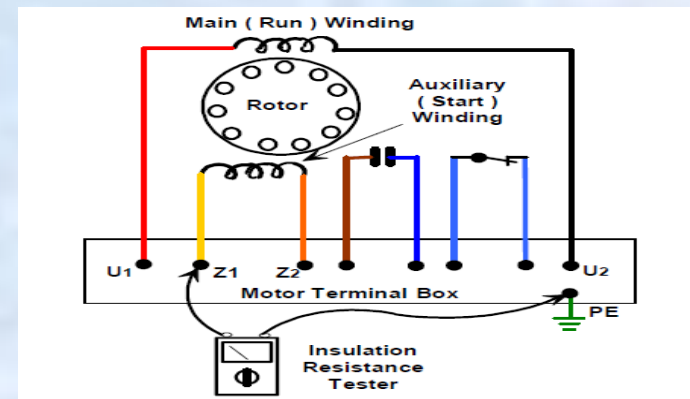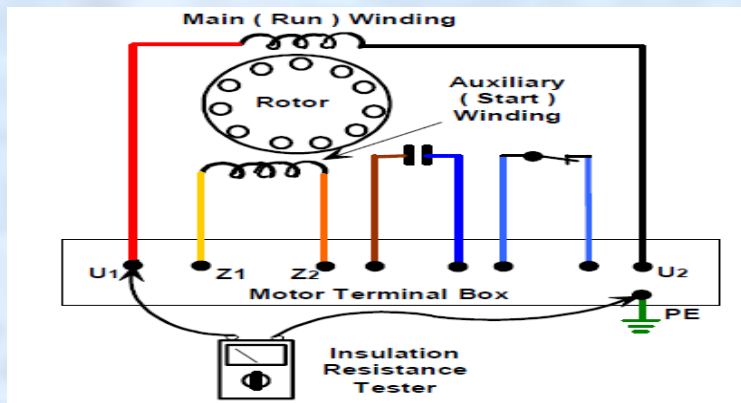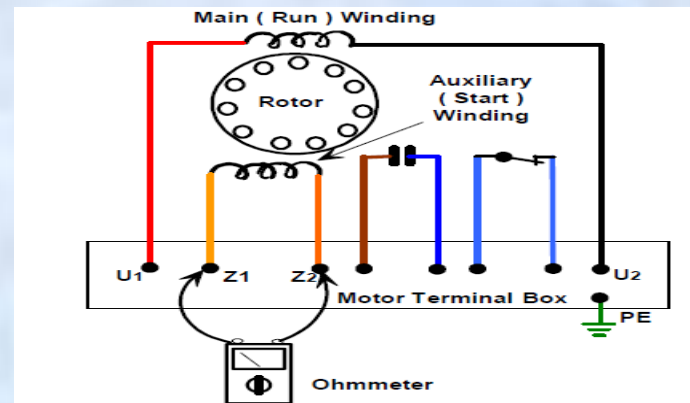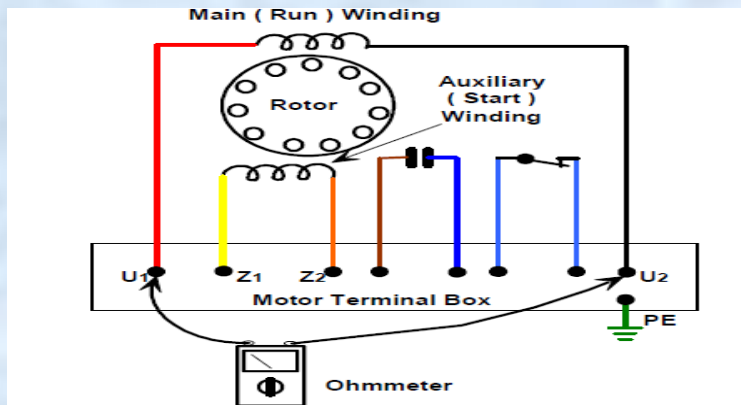- **Step 1:** Isolate the motor electrically, and if necessary, mechanically.
- **Step 2:** Identify the way the motor terminal block is connected.
- **Step 3:** Identify the 2 stator windings - usually labelled U1-U2 and Z1-Z2.
- **Step 4:** Measure and record the resistance of each winding.



Determination Of Equivalent Circuit Parameters Of Three Phase Induction Motor

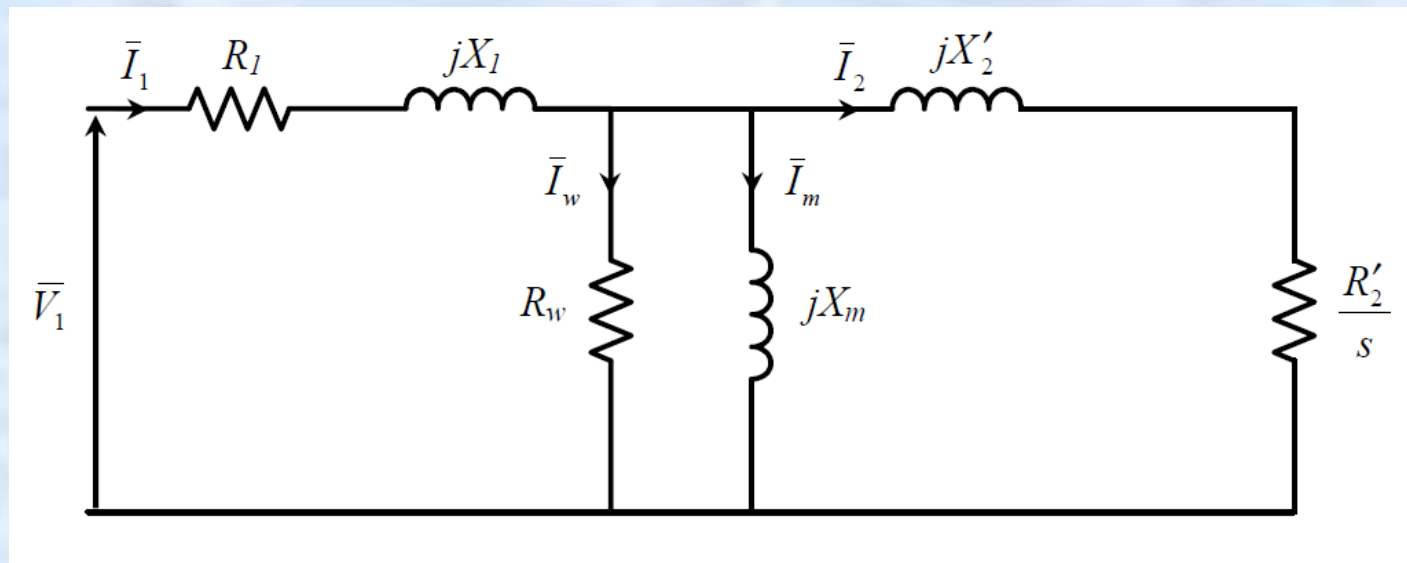- It is possible to find the parameters of the equivalent circuit of the three phase induction motor experimentally



1- The DC Test:

The DC resistance of the stator can be measured by applying DC current to the terminals of the winding of each phase and taking the reading of the voltage and the current (or using ohmmeter) and determine the DC resistance as follows:

$$R_{iDC} = \frac{V_{iDC}}{I_{iDC}}, \text{ where } i \text{ represents the number of the winding } i (i = 1, 2, 3). \quad (1)$$

After that, the average of the readings can be calculated as:

$$R_{DC} = \frac{R_{1DC} + R_{2DC} + R_{3DC}}{3} \quad (2)$$

Then, the AC resistance is given by:

$$R_1 = 1.15 R_{DC} \quad (3)$$

2- The Locked Rotor Test

When the rotor is locked (i.e. prevented from running), s is equal to 1. The secondary impedance becomes much less than the magnetizing branch and the corresponding equivalent circuit becomes that of Fig.2. The readings to be obtained from this test are:


- a) Three phase power $P_{3\phi_BL}$
- b) Line voltage V_{L_BL}
- c) Line current I_{BL}

Then, R_{eq} , Z_{eq} , and X_{eq} can be obtained using the following equations:

$$R_{eq} = \frac{P_{BL}}{I_{BL}^2}$$

$$Z_{eq} = \frac{V_{BL}}{I_{BL}}$$

$$X_{eq} = \sqrt{Z_{eq}^2 - R_{eq}^2}$$

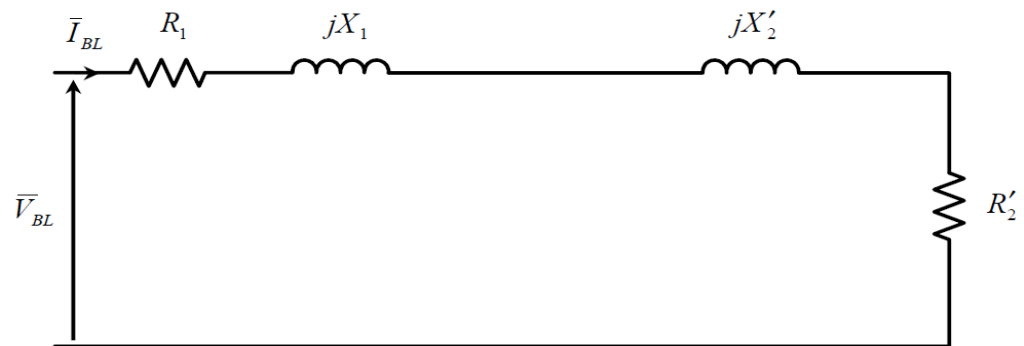

Separation of X_1 , X'_2 , R_1 , and R'_2 can be done as follows:

$$X_1 = X'_2 = \frac{1}{2} X_{eq}$$

$$R'_2 = R_{eq} - R_1$$

3- The No Load Test

d) Three phase power $P_{3\phi_NL}$

e) Line voltage V_{L_NL}

f) Line current I_{NL}

Then, R_w , and X_m , can be obtained as fallows:

$$P_{core+mechanical} = P_{NL} - I_{NL}^2 R_1$$

$$\bar{E}_1 = \bar{V}_{NL} - \bar{I}_{NL} (R_1 + jX_1)$$


Note: $(\bar{I}_{NL} = I_{NL} \angle -\theta, \quad \theta = \cos^{-1} \frac{P_{NL}}{V_{NL} I_{NL}})$

$$R_w = \frac{|E_1|^2}{P_{core+mechanical}}$$

$$I_w = \frac{|E_1|}{R_w}$$

$$I_m = \sqrt{I_{NL}^2 - I_w^2}$$



$$X_m = \frac{|E_1|}{I_m}$$

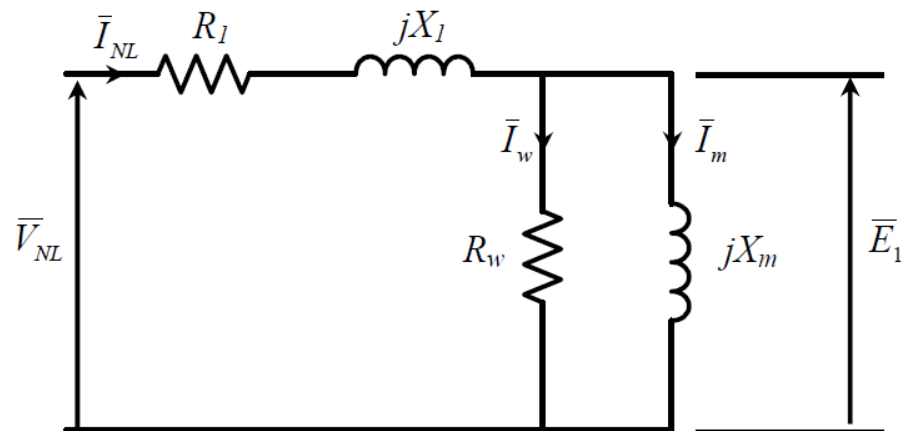

CHAPTER 9


Typical Motor Failure & Protection

Typical motor failures

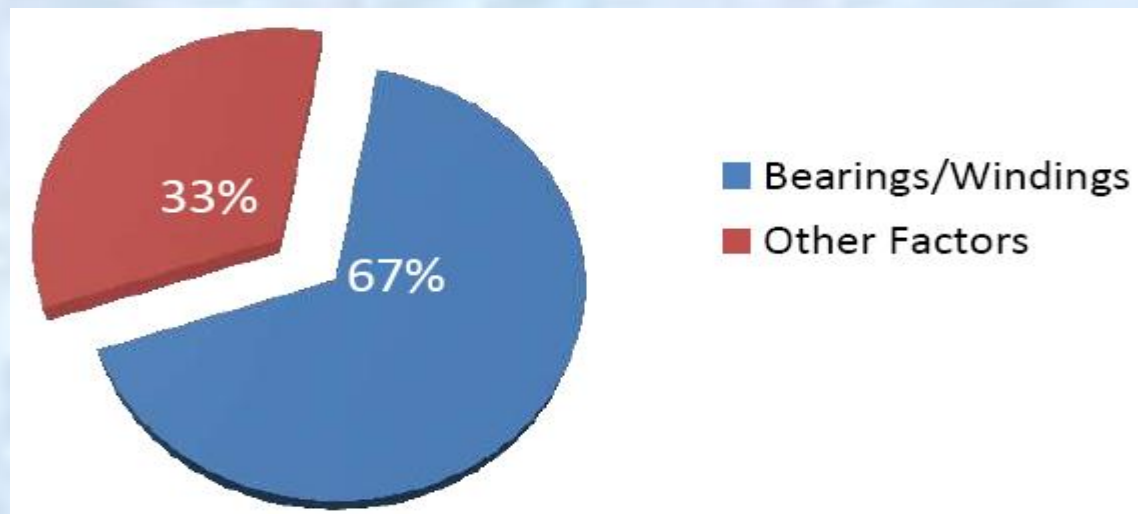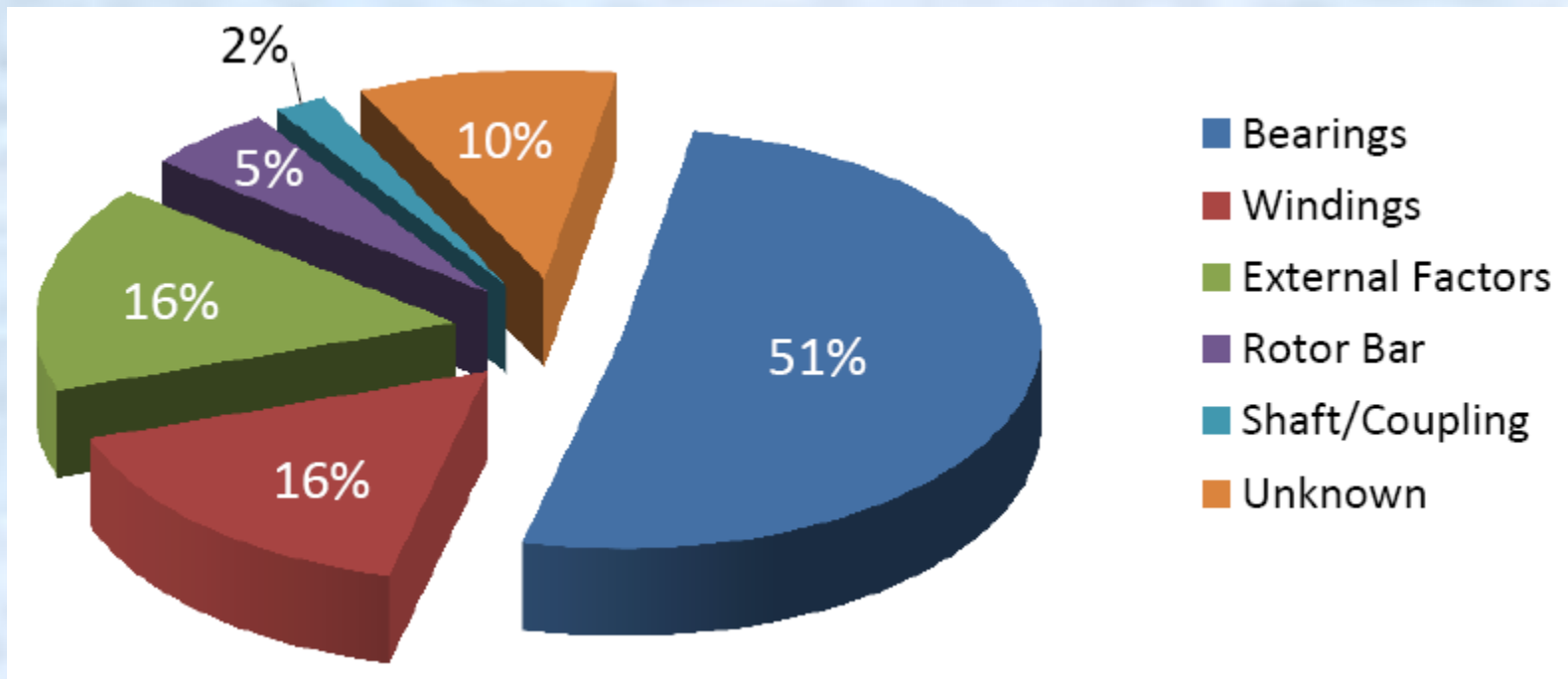

Motor failures by component

Component	% Failures	Potential Cause
Bearings	51%	Lubrication, mechanical, shaft currents, contamination
Windings	16%	Overvoltage, water, overload, undervoltage, environment
External Factors	16%	Environmental or load related
Rotor Bar	5%	Overload, locked rotor, vibration
Shaft/Coupling	2%	Mechanical, overload
Unknown	10%	No root cause determined

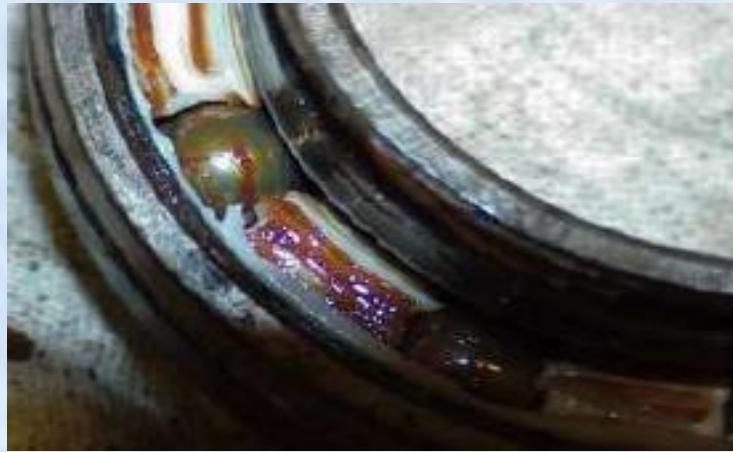

Bearing



Cooling




Ventilation

Motor Protection

1- Thermal Overload

- Process Caused (Excessive load)
- High Ambient Conditions (Hot, Blocked Ventilation)
- Power Supply Issues (Voltage/Current Unbalance, Harmonics)

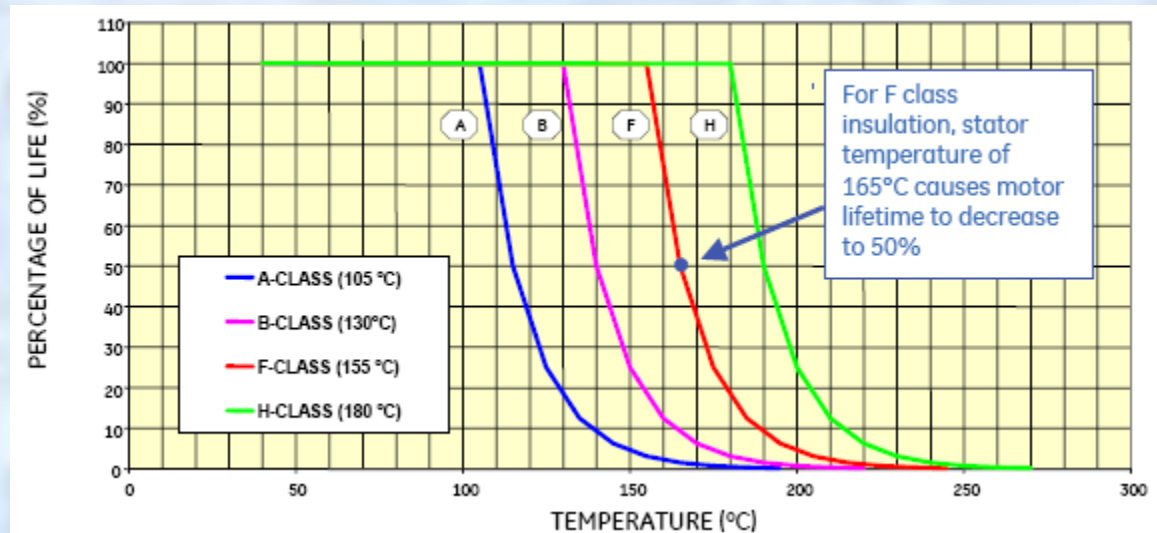Insulation lifetime decreases by half if motor operating temperature exceeds thermal limit by 10°C for any period of time



2- Overvoltage Protection

- The overall result of an overvoltage condition is a decrease in load current and poor power factor.
- The overvoltage element should be set to 110% of the motors nameplate.

3- Undervoltage Protection


- The overall result of an undervoltage condition is an increase in current and motor heating and a reduction in overall motor performance.
- The undervoltage trip should be set to 80-90% of nameplate.

Over/Under voltage relay



4- Ground Fault Protection

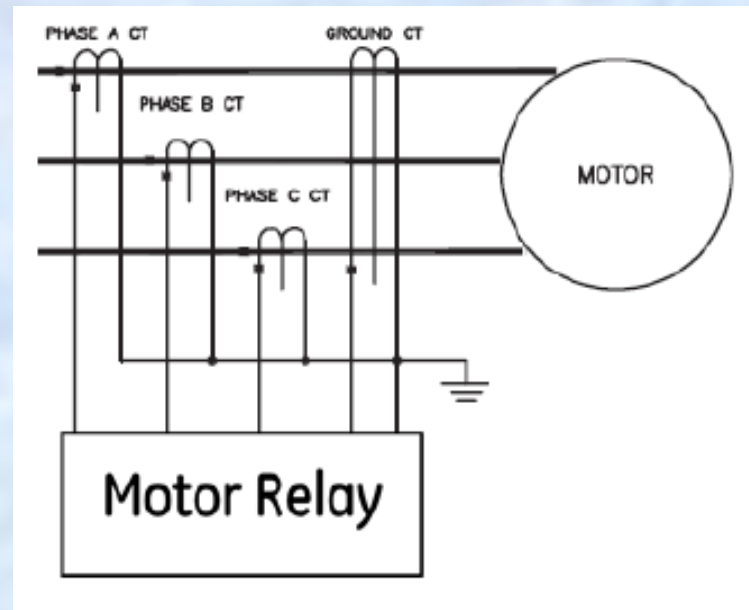
- A ground fault is a fault that creates a path for current to flow from one of the phases directly to the neutral through the earth bypassing the load
- When its phase conductor's insulation is damaged for example due to voltage stress, moisture or internal fault occurs between the conductor and ground



Zero Sequence CT Connection


5- Differential Protection


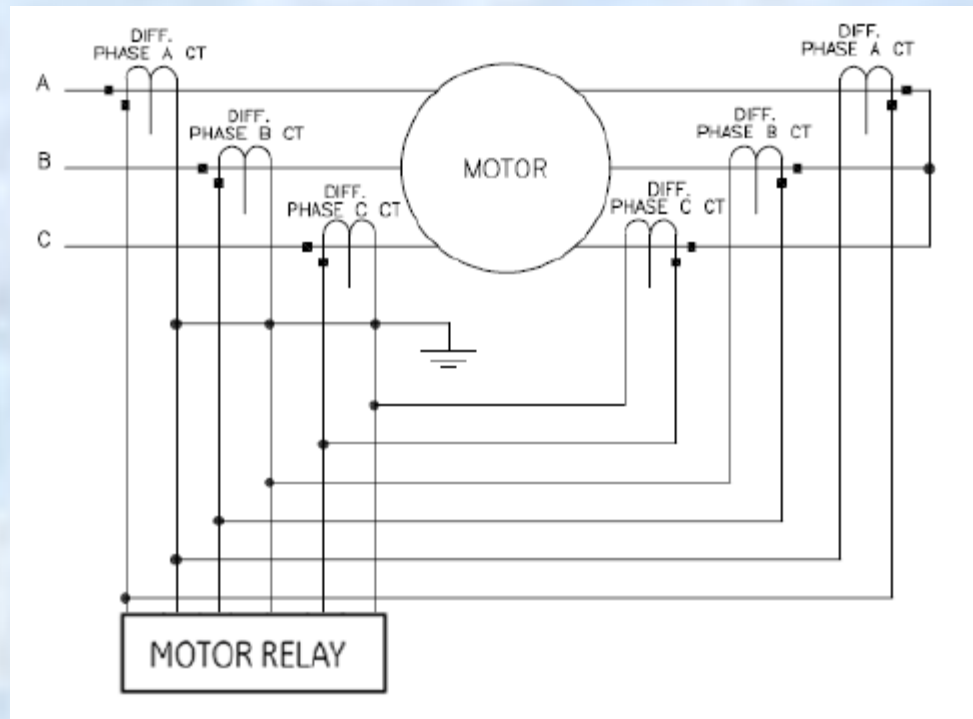
➤ Differential protection may be considered the first line of protection for internal phase-to-phase or phase-to-ground faults. In the event of such faults, the quick response of the differential element may limit the damage that may have otherwise occurred to the motor.




Summation method with six CTs

6- Phase sequence relay

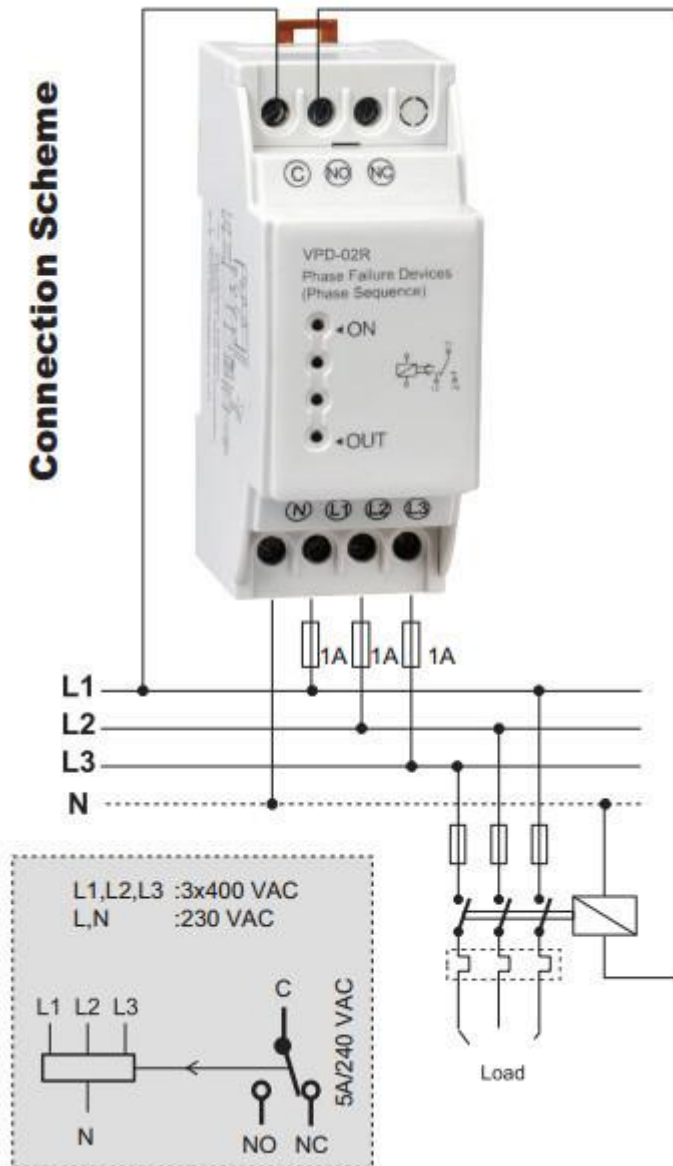

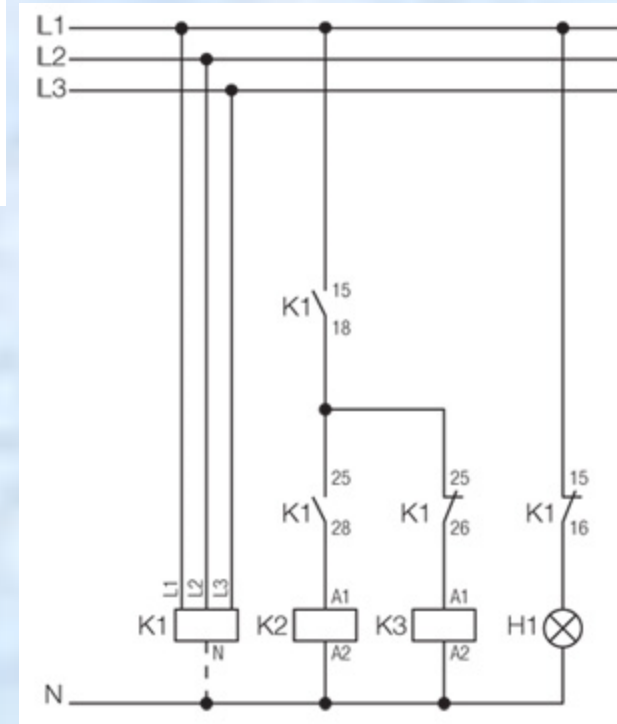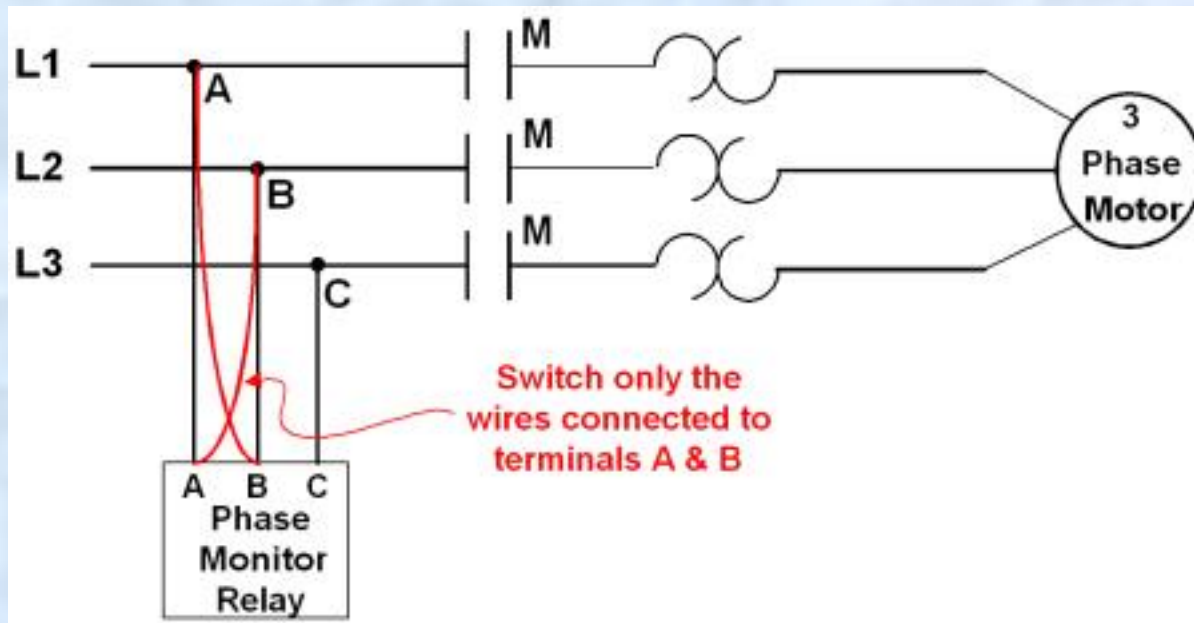

7- Unbalance relay

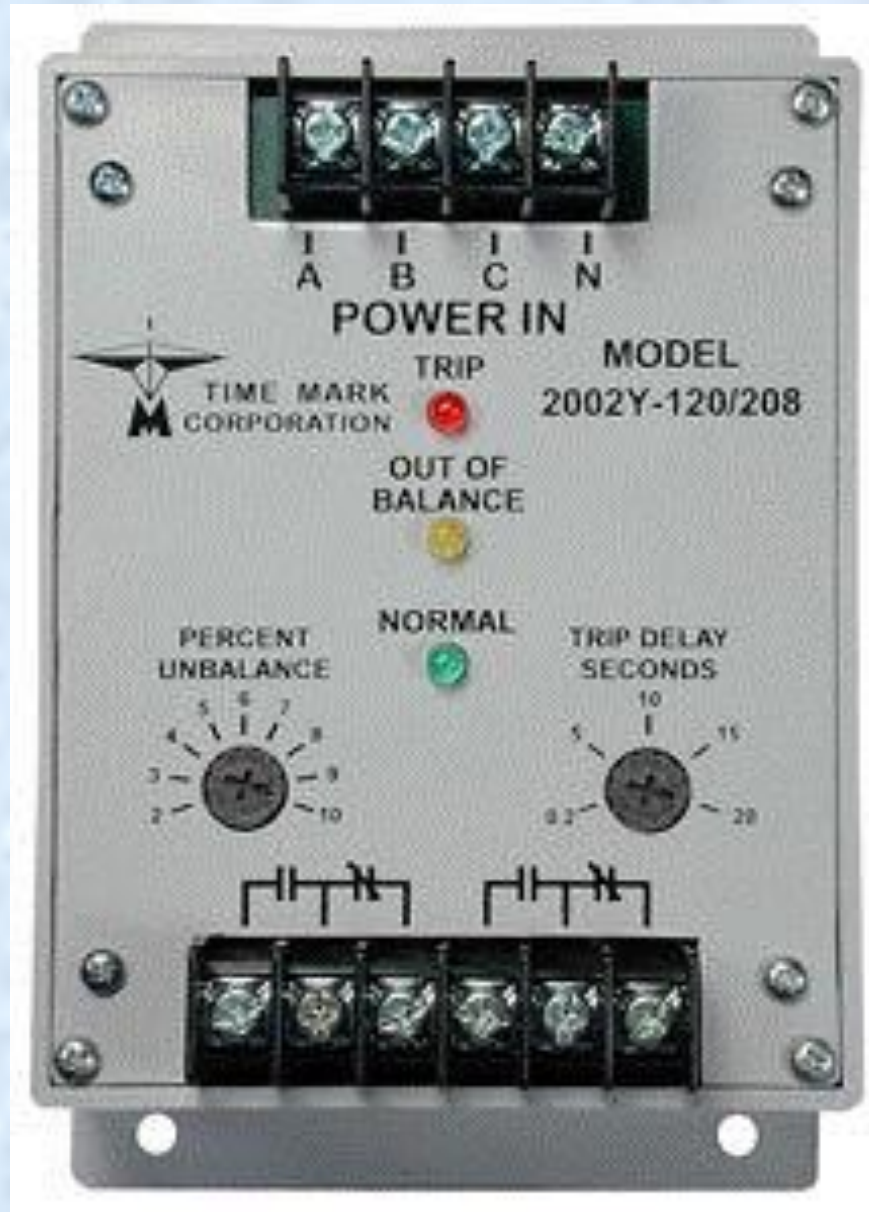



EXAM

